

Article A : Introduction A-1 to A-22

Syllabus : Introduction to Electrical engineering, Concept of emf, Current, Electric Potential, Potential Difference, Resistance, Ohm's Law, Concept of Inductor and Capacitor, Introduction to Electronics engineering.

A.1 IntroductionA-2

A.2 Concept of EMF and CurrentA-2

A.2.1 Concept of EMFA-2

A.2.2 Concept of CurrentA-2

A.3 Electric Potential and Potential DifferenceA-3

A.3.1 Electric PotentialA-3

A.3.2 Potential Difference (P.D.)A-3

A.4 Resistance (R)A-3

A.4.1 Factors Affecting the Resistance ValueA-3

A.4.2 Resistivity or Specific Resistance (ρ)A-3

A.4.3 Conductance (G)A-4

A.4.4 Conductivity (σ)A-4

A.4.5 Resistors in SeriesA-5

A.4.6 Resistors in ParallelA-5

A.5 Ohm's LawA-6

A.6 ElectronicsA-6

A.6.1 Evolution of ElectronicsA-6

A.7 Impact of Electronics on Industry and SocietyA-7

A.8 Types of Electronic ComponentsA-8

A.8.1 Active ComponentsA-8

A.8.2 Passive ComponentsA-9

A.8.3 Comparison of Active and Passive ComponentsA-9

A.9 ResistorA-9

A.9.1 Resistance (R)A-9

A.10 Classification of ResistorsA-9

A.10.1 Linear ResistorsA-10

A.10.2 Nonlinear ResistorsA-10

A.11 General Specifications of ResistorsA-10

A.12 Types of Fixed ResistorsA-11

A.12.1 Carbon Composition ResistorA-11

A.12.2 Wire-wound ResistorsA-11

A.13 Colour Coding of ResistorsA-11

A.13.1 Colour Coding with Four BandsA-12

A.14 Variable ResistorsA-12

A.14.1 Types of Variable ResistorsA-12

A.14.2 A PotentiometerA-12

A.15 CapacitorsA-13

A.15.1 CapacitanceA-13

A.15.2 Classification of CapacitorsA-14

A.16 Capacitors SpecificationsA-14

A.17 Colour Coding of CapacitorsA-14

A.18 Variable CapacitorsA-16

A.18.1 Air Gang CapacitorA-16

A.19 InductorsA-17

A.19.1 Types of Fixed InductorA-17

A.19.2 Applications of Fixed InductorsA-18

A.19.3 Variable InductorsA-18

A.19.4 Application of Variable InductorsA-18

A.20 Electromagnetic RelaysA-18

A.20.1 General Purpose RelayA-18

A.21 SwitchesA-19



| | | | | | |
|--|---|--------------------|-------|--|------|
| A.21.1 | Toggle Switches | A-20 | 1.4.1 | Series Circuits (Resistors in series) | 1-6 |
| A.21.2 | Micro-switches | A-20 | 1.4.2 | Parallel Circuit (Resistors in Parallel) | 1-7 |
| A.22 | Active Devices | A-20 | 1.4.3 | Division of Current Between Parallel Resistors | 1-11 |
| A.22.1 | Diode | A-20 | 1.4.4 | Division of Voltage in the Series Connected Resistors | 1-12 |
| A.22.2 | Transistor | A-21 | 1.4.5 | Relative Potential | 1-12 |
| • | Review Questions..... | A-21 | 1.4.6 | Comparison of Series & Parallel Circuits | 1-13 |
| Unit I | | | | | |
| Chapter 1 : Electric Circuits | | 1-1 to 1-48 | | | |
| Syllabus : Electric Circuits : Classification of electrical networks, Ideal and practical voltage and current sources, Source transformation, Simplification of networks using series and parallel combinations, Star delta transformation, Kirchhoff's laws (loop Current analysis). | | | | | |
| 1.1 | Introduction to Networks / Circuits | 1-2 | 1.5 | Removal of Redundant Branches and Redundant Subcircuit | 1-14 |
| 1.1.1 | Network | 1-2 | 1.6 | Source Transformation | 1-18 |
| 1.1.2 | Circuit Element | 1-2 | 1.6.1 | Transformation of Voltage Source to Current Source | 1-18 |
| 1.1.3 | Open Circuit | 1-2 | 1.6.2 | Transformation of Current Source to Voltage Source | 1-19 |
| 1.1.4 | Short Circuit | 1-2 | 1.6.3 | Voltage Sources in Series | 1-20 |
| 1.1.5 | Branch | 1-2 | 1.6.4 | Current Sources in Parallel | 1-21 |
| 1.1.6 | Mesh or Loop | 1-2 | 1.7 | Star-Delta and Delta-Star Transformation | 1-22 |
| 1.1.7 | Node or Junction | 1-2 | 1.7.1 | The Star Network | 1-22 |
| 1.2 | Classification of Electric Networks | 1-2 | 1.7.2 | The Delta Network | 1-23 |
| 1.2.1 | Active or Passive Network | 1-3 | 1.7.3 | Delta-Star Transformation | 1-23 |
| 1.2.2 | Bilateral or Unilateral Network | 1-3 | 1.7.4 | Star to Delta Conversion | 1-26 |
| 1.2.3 | Distributed or Lumped Network | 1-3 | 1.8 | Kirchhoff's Laws | 1-31 |
| 1.2.4 | Linear or Nonlinear Network | 1-3 | 1.8.1 | Kirchhoff's Current Law (KCL) | 1-31 |
| 1.3 | Energy Sources | 1-4 | 1.8.2 | Node Analysis | 1-33 |
| 1.3.1 | Independent Voltage Sources | 1-4 | 1.8.3 | Solved Examples on KCL | 1-34 |
| 1.3.2 | Current Sources | 1-5 | 1.9 | Mesh or Loop and Sign Convention | 1-35 |
| 1.4 | Circuit Simplification Techniques | 1-6 | 1.9.1 | Kirchhoff's Voltage Law (or Mesh or Loop Law) | 1-36 |



| | | | |
|-------|--|--------|---|
| 1.9.2 | Procedure to be Followed to Solve an Example using Kirchoff's Laws1-37 | 2.3.3 | The Right Hand Gripping Rule (or Right Hand Thumb Rule)2-4 |
| 1.9.3 | Cramer's Rule for Solving the Simultaneous Equations1-37 | 2.3.4 | The Corkscrew Rule2-5 |
| 1.9.4 | Solved Examples on KVL and KCL1-39 | 2.4 | Magnetic Field due to Solenoid2-5 |
| 1.9.5 | Mesh Analysis or Maxwell's Loop Current Method1-41 | 2.4.1 | Right Hand Thumb Rule2-5 |
| • | Review Questions..... 1-47 | 2.4.2 | Corkscrew Rule2-6 |
| | Unit I | 2.5 | Toroid2-6 |
| | | 2.6 | Force on a Current Carrying Conductor in a Magnetic Field2-6 |
| | | 2.6.1 | Magnitude of the Force2-7 |
| | | 2.6.2 | Direction of the Force Exerted on the Conductor (Fleming's Left Hand Rule)2-8 |
| | | 2.7 | Permeability2-8 |
| | | 2.7.1 | Absolute Permeability (μ) 2-8 |
| | | 2.7.2 | Permeability of Free Space or Vacuum (μ_0) 2-9 |
| | | 2.7.3 | Relative Permeability (μ_r) 2-9 |
| | | 2.8 | MMF, Reluctance and Permeance2-9 |
| | | 2.8.1 | Magneto motive Force (MMF)2-9 |
| | | 2.8.2 | Reluctance (S)2-10 |
| | | 2.8.3 | Permeance2-10 |
| | | 2.9 | Magnetic Circuit2-10 |
| | | 2.9.1 | Expressions for Various Quantities2-11 |
| | | 2.9.2 | Comparisons of Magnetic and Electrical Circuits2-11 |
| | | 2.10 | Composite Magnetic Circuits2-12 |
| | | 2.10.1 | Series Magnetic Circuit.....2-12 |
| | | 2.10.2 | A Series Magnetic Circuit with Air Gap ..2-13 |
| | | • | Review Questions2-16 |

Chapter 2 : Magnetic Circuits 2-1 to 2-16

Syllabus : Magnetic Circuit : Flux, Flux density, Reluctance, MMF, Permeability and Field strength, Their units and Relationships, Comparison of electric and magnetic circuit, Series magnetic circuit.

| | |
|-------|---|
| 2.1 | Introduction 2-2 |
| 2.1.1 | Magnet 2-2 |
| 2.2 | Law's and Definitions 2-2 |
| 2.2.1 | Pole Strength 2-2 |
| 2.2.2 | Laws of Magnetism 2-2 |
| 2.2.3 | Magnetic Field 2-2 |
| 2.2.4 | Magnetic Lines of Force 2-3 |
| 2.2.5 | Magnetic Flux ϕ 2-3 |
| 2.2.6 | Magnetic Flux Density (B) 2-3 |
| 2.2.7 | Magnetic Field Strength (H) 2-3 |
| 2.2.8 | Electromagnets 2-3 |
| 2.3 | Magnetic Effects of Electric Current 2-3 |
| 2.3.1 | Dot and Cross Conventions 2-4 |
| 2.3.2 | Rules to Decide Direction of Magnetic Field 2-4 |

Unit II

Chapter 3 : Single Phase AC Circuits 3-1 to 3-52

Syllabus : Single Phase AC Circuits : Elementary idea about power generation, Transmission and distribution, Generation of single-phase sinusoidal A.C voltages, AC quantities, Single phase ac circuit analysis (R, L, C, R-L-C series) on the basis of impedance, Admittance, Concept of active, Reactive, Apparent power and power factor etc.

| | |
|--|--|
| <p>3.1 Elementary Idea About Power Generation 3-2</p> <p>3.2 Introduction to Single Phase AC circuits..... 3-3</p> <p> 3.2.1 Definition of an AC Quantity 3-3</p> <p>3.3 Various Types of AC Waveforms 3-3</p> <p> 3.3.1 Waveform 3-3</p> <p> 3.3.2 Types of AC Waveforms 3-3</p> <p> 3.3.3 Sinusoidal AC Quantities 3-3</p> <p>3.4 Generation of Single Phase AC Waveform 3-4</p> <p> 3.4.1 Elementary Alternator 3-4</p> <p>3.5 Definitions 3-5</p> <p> 3.5.1 Waveform 3-5</p> <p> 3.5.2 Instantaneous Value 3-5</p> <p> 3.5.3 Cycle 3-6</p> <p> 3.5.4 Time Period or Periodic Time (T) 3-6</p> <p> 3.5.5 Frequency 3-6</p> <p> 3.5.6 Amplitude 3-7</p> <p> 3.5.7 Angular Velocity (ω) 3-7</p> <p>3.6 Peak and Peak to Peak Voltage 3-7</p> <p>3.7 Effective or R.M.S. Value 3-7</p> <p> 3.7.1 Analytical Method to Obtain the RMS Value 3-8</p> <p> 3.7.2 Graphical Evaluation of RMS Value 3-9</p> | <p>3.8 Average Value3-9</p> <p> 3.8.1 Methods to Calculate the Average Value3-9</p> <p> 3.8.2 Analytical Method3-9</p> <p> 3.8.3 Graphical Evaluation of Average Value 3-10</p> <p>3.9 Form Factor 3-10</p> <p>3.10 Crest Factor or Peak Factor (K_p) 3-11</p> <p>3.11 Solved Examples 3-11</p> <p>3.12 Phasor Representation of an Alternative Quantity 3-13</p> <p>3.13 Phase of an Alternating Quantity 3-13</p> <p> 3.13.1 Phase Angle 3-13</p> <p> 3.13.2 Phase Difference 3-13</p> <p> 3.13.3 Leading and Lagging Phase Difference .. 3-14</p> <p> 3.13.4 In Phase and Out of Phase 3-14</p> <p>3.14 Mathematical Representation of Phasor 3-18</p> <p> 3.14.1 Polar Representation 3-18</p> <p> 3.14.2 Rectangular Representation 3-18</p> <p> 3.14.3 Polar to Rectangular Conversion 3-18</p> <p> 3.14.4 Rectangular to Polar Conversion 3-18</p> <p>3.15 Addition and Subtraction of Phasors 3-19</p> <p> 3.15.1 Multiplication and Division of Phasors ... 3-19</p> <p>3.16 Single Phase AC Circuits 3-19</p> <p> 3.16.1 Reactance and Impedance 3-20</p> <p> 3.16.2 Reactance 3-20</p> <p> 3.16.3 Inductive Reactance (X_L) 3-20</p> <p> 3.16.4 Capacitive Reactance (X_C) 3-20</p> <p> 3.16.5 Impedance (Z) 3-20</p> |
|--|--|



| | | | | | |
|--------|---|------|--------|--|------|
| 3.17 | AC Circuit Containing a Pure Resistance | 3-20 | 3.21.5 | Causes of Low Power Factor | 3-29 |
| 3.17.1 | Analysis of the Purely Resistive AC Circuit | 3-21 | 3.21.6 | Power Factor | 3-29 |
| 3.17.2 | Voltage and Current Waveforms and Equations | 3-21 | 3.21.7 | Power Triangle | 3-30 |
| 3.17.3 | Phasor Diagram | 3-21 | 3.22 | AC Circuits With Series Elements | 3-30 |
| 3.17.4 | Power in Purely Resistive AC Circuits | 3-21 | 3.23 | The Series R-L Circuit | 3-30 |
| 3.17.5 | Average Power | 3-21 | 3.23.1 | Phasor Diagram | 3-31 |
| 3.17.6 | Impedance of the Purely Resistive Circuit | 3-22 | 3.23.2 | Impedance of L-R Series Circuit | 3-31 |
| 3.18 | AC Circuit Consisting of a Pure Inductance | 3-22 | 3.23.3 | Impedance Triangle | 3-31 |
| 3.18.1 | Equations for Current i and Voltage v | 3-22 | 3.23.4 | Voltage and Current Waveforms | 3-31 |
| 3.18.2 | Waveforms and Phasor Diagram | 3-23 | 3.23.5 | Power in Series L-R Circuit | 3-32 |
| 3.18.3 | Power in a Purely Inductive Circuit | 3-23 | 3.23.6 | Power Triangle for L-R series Circuit | 3-33 |
| 3.18.4 | Impedance of a Purely Inductive Circuit | 3-24 | 3.23.7 | Various Powers in RL Circuit | 3-33 |
| 3.19 | AC Circuit Consisting of a Pure Capacitance..... | 3-25 | 3.23.8 | Power Factor | 3-33 |
| 3.19.1 | Equations for Voltage and Current | 3-25 | 3.24 | The Series R-C Circuit | 3-35 |
| 3.19.2 | Current and Voltage Waveforms and Phasor Diagram | 3-26 | 3.24.1 | Phasor Diagram | 3-35 |
| 3.19.3 | Power in Purely a Capacitive AC Circuit | 3-26 | 3.24.2 | Impedance of RC Series Circuit | 3-35 |
| 3.19.4 | Impedance of a Purely Capacitive Circuit | 3-27 | 3.24.3 | Impedance Triangle (Series R-C circuit) | 3-36 |
| 3.20 | Concept of Impedance Triangle | 3-27 | 3.24.4 | Voltage and Current Waveforms | 3-36 |
| 3.21 | Important Terms Related to Power | 3-28 | 3.24.5 | Power in Series R-C Circuit | 3-36 |
| 3.21.1 | Apparent Power (S) | 3-28 | 3.24.6 | Power Triangle for R-C Series Circuit | 3-37 |
| 3.21.2 | Real Power or True Power or Active Power (P) | 3-28 | 3.24.7 | Various Powers and Power Factor | 3-37 |
| 3.21.3 | Reactive Power or Imaginary Power (Q) | 3-28 | 3.25 | An R-L-C Series Circuit | 3-38 |
| 3.21.4 | Importance (Significance) of Power Factor | 3-29 | 3.25.1 | Importance of the Values of Reactances | 3-38 |
| | | | 3.25.2 | Phasor Diagrams | 3-38 |
| | | | 3.25.3 | Impedance of Series LCR Circuit | 3-40 |
| | | | 3.25.4 | Impedance Triangle for an LCR Circuit ... | 3-40 |
| | | | 3.25.5 | Power Supplied to the R.L.C. Circuit..... | 3-40 |



| | | | | | |
|---|--|-------------|-------|---|------|
| 3.25.6 | Power Triangle | 3-41 | 4.1.1 | Three Phase Supply Waveforms | 4-2 |
| 3.25.7 | Various Powers and Power Factors of RLC Series Circuit | 3-41 | 4.2 | Advantages of Three Phase Systems | 4-2 |
| 3.26 | Resonance | 3-45 | 4.3 | Concept of Three Phase Supply | 4-3 |
| 3.26.1 | Resonance in Series RLC Circuit | 3-45 | 4.3.1 | Symmetrical or Balanced System | 4-4 |
| 3.26.2 | Resonant Frequency (f_r) | 3-45 | 4.3.2 | Phase Sequence | 4-4 |
| 3.26.3 | Phasor Diagram at Resonance | 3-46 | 4.4 | Three Phase Supply Connections | 4-4 |
| 3.26.4 | Impedance at Resonance | 3-46 | 4.4.1 | Star Connection (Wye Connection) | 4-4 |
| 3.26.5 | Current at Resonance | 3-46 | 4.4.2 | Delta Connection | 4-5 |
| 3.26.6 | Phase Angle of Series Resonant Circuit | 3-47 | 4.5 | Types of Loads | 4-5 |
| 3.26.7 | Voltage and Current | 3-47 | 4.5.1 | Balanced or Unbalanced Load | 4-5 |
| 3.26.8 | Variation of Power Factor | 3-47 | 4.6 | A Three Phase Balanced Star Load | 4-6 |
| 3.26.9 | The Q-Factor (Quality Factor) of a Series Resonant Circuit | 3-47 | 4.6.1 | Line Voltages and Phase Voltages for Star Connected Supply | 4-6 |
| 3.26.10 | Bandwidth of a Series Resonant Circuit | 3-48 | 4.6.2 | Phase and Line Voltage for a Star Load ... | 4-7 |
| 3.26.11 | Magnification in Series Resonant Circuit | 3-49 | 4.6.3 | Relation between Phase and Line Currents | 4-7 |
| 3.26.12 | Characteristics of Series Resonant Circuit | 3-49 | 4.6.4 | Relation between Phase and Line Voltages | 4-8 |
| | Review Questions..... | 3-51 | 4.6.5 | The Complete Phasor Diagram | 4-9 |
| Unit II | | | 4.6.6 | Power Relations | 4-10 |
| Chapter 4 : Three phase AC Circuits 4-1 to 4-22 | | | 4.6.7 | Power Triangle | 4-10 |
| Syllabus : Three phase AC Circuits : Introduction to 3 phase supply and its necessity, Balanced three phase system, Relation between line and phase quantities (with phasor diagram), Power in three phase circuits for star and Delta connection. | | | | | |
| 4.1 | Introduction to Polyphase AC Circuits | 4-2 | 4.6.8 | Power Factor | 4-10 |
| | | | 4.6.9 | Solved Examples on Star Load | 4-10 |
| | | | 4.7 | Three Phase Balanced Delta Load | 4-13 |
| | | | 4.7.1 | Line Voltages and Phase Voltages for Delta Connected Supply | 4-13 |
| | | | 4.7.2 | Phase and Line Voltages in Delta Connected Load | 4-14 |
| | | | 4.7.3 | Line Current and Phase Current for Delta Connection | 4-14 |
| | | | 4.7.4 | The Complete Phasor Diagram for Delta Load | 4-15 |
| | | | 4.7.5 | Power Relations | 4-16 |



| | | |
|-------|---|-------------|
| 4.7.6 | Power Triangle | 4-16 |
| 4.7.7 | Power Factor | 4-16 |
| 4.7.8 | Comparison of Star and Delta Connections | 4-17 |
| 4.7.9 | Solved Examples on Delta Load | 4-17 |
| • | Review Questions..... | 4-21 |

| |
|-----------------|
| Unit III |
|-----------------|

Chapter 5 : DC Machines**5-1 to 5-22**

Syllabus : DC Machines : Construction, Working principle of D.C. Generator, Emf equation of D.C. generator (derivation not expected), Working principle of D.C. motor, Types of D.C. motor, Back emf (Numerical), Industrial applications.

| | | |
|--------|--|------|
| 5.1 | Introduction | 5-2 |
| 5.2 | Types of DC Machines | 5-2 |
| 5.2.1 | Windings in a DC Machine | 5-2 |
| 5.3 | Construction of a DC Machine | 5-2 |
| 5.3.1 | Important Parts of a DC Generator | 5-3 |
| 5.3.2 | Yoke | 5-3 |
| 5.3.3 | Poles, Pole Shoe and Pole Core | 5-3 |
| 5.3.4 | Field Winding ($F_1 - F_2$) | 5-4 |
| 5.3.5 | Armature Core | 5-4 |
| 5.3.6 | Armature Winding | 5-4 |
| 5.3.7 | Commutator | 5-5 |
| 5.3.8 | Brushes | 5-5 |
| 5.4 | Types of Armature Windings | 5-6 |
| 5.5 | Generating Action | 5-6 |
| 5.5.1 | Principle of Operation of a DC Generator | 5-6 |
| 5.6 | Practical DC Generator | 5-7 |
| 5.7 | E.M.F. Equation of a DC Generator | 5-7 |
| 5.8 | DC Motor | 5-9 |
| 5.8.1 | Construction of a DC Motor | 5-9 |
| 5.8.2 | Principle of Operation of a DC Motor | 5-9 |
| 5.8.3 | Direction of Rotation of the Motor | 5-9 |
| 5.8.4 | Torque | 5-9 |
| 5.8.5 | Back EMF | 5-10 |
| 5.9 | Voltage Equation of a DC Motor | 5-10 |
| 5.9.1 | Role of Back Emf | 5-10 |
| 5.9.2 | Power Equation of a DC Motor | 5-11 |
| 5.9.3 | Torque Equation of a DC Motor | 5-12 |
| 5.9.4 | Effect of Loading on the DC Motor Operation | 5-12 |
| 5.10 | Types of DC Motors | 5-13 |
| 5.10.1 | Separately Excited DC Motor | 5-13 |
| 5.10.2 | DC Shunt Motor | 5-14 |
| 5.10.3 | DC Series Motor | 5-15 |
| 5.11 | DC Compound Motors | 5-15 |
| 5.11.1 | Long Shunt Compound Motor | 5-16 |
| 5.11.2 | Short Shunt Compound DC Motor | 5-16 |
| 5.11.3 | Cumulative Compound DC Motors | 5-17 |
| 5.11.4 | Differential Compound DC Motors | 5-17 |
| 5.12 | Torque and Speed Equations | 5-17 |
| 5.12.1 | Torque Equations | 5-17 |
| 5.12.2 | Speed Equations | 5-18 |
| 5.12.3 | Never Start a Series Motor on No Load | 5-18 |
| 5.13 | Industrial Applications | 5-21 |
| 5.13.1 | Shunt Motor Applications | 5-21 |
| 5.13.2 | Series Motor Applications | 5-21 |
| 5.13.3 | Cumulative Compound Motor Applications | 5-21 |

5.13.4 Differential Compound Motors Applications5-22

- **Review Questions..... 5-22**

Unit III

Chapter 6 : Single Phase Transformers 6-1 to 6-24

Syllabus : AC Machines : Single Phase Transformers : Construction, Operating principle, Emf equation, Voltage and current ratios. Losses, Efficiency and regulation, Concept of ideal transformer, Auto-transformer.

6.1 Introduction 6-2

6.2 Construction of a Transformer 6-2

6.2.1 Laminated Steel Core 6-2

6.2.2 Different Cross-sections for Transformer Limbs 6-3

6.2.3 Windings of a Transformer 6-3

6.2.4 Transformer Tank 6-4

6.2.5 Conservator 6-4

6.2.6 Breather 6-4

6.2.7 Buchholz Relay 6-4

6.2.8 Explosion Vent 6-4

6.3 Principle of Operation 6-5

6.4 Transformer Types 6-5

6.4.1 Core Type Transformer 6-5

6.4.2 Shell Type Transformer 6-6

6.4.3 Berry Type Transformers 6-7

6.5 EMF Equation of a Transformer 6-7

6.5.1 Expressions for the Induced Voltages 6-7

6.6 Voltage and Current Ratios 6-8

6.6.1 Voltage Ratios of the Transformer with Load6-8

6.6.2 Voltage Ratios for the Transformer without Load6-8

6.6.3 Transformation Ratio (K)6-9

6.6.4 Turns Ratio of the Transformer6-9

6.6.5 Types of Transformers based on the Value of K6-9

6.6.6 Current Ratios6-9

6.7 Rating of Transformer 6-10

6.8 Losses in a Transformer 6-12

6.8.1 Copper Loss (P_{cu}) 6-12

6.8.2 Iron Loss (P_i) 6-13

6.9 Efficiency and Regulation 6-13

6.9.1 Efficiency (η) 6-13

6.9.2 Voltage Regulation 6-15

6.10 An Ideal Transformer 6-18

6.11 Transformer Testing 6-19

6.11.1 Direct Loading Test 6-19

6.11.2 Efficiency Measurement 6-19

6.11.3 Regulation Measurement 6-20

6.11.4 Advantages of a Two Winding Transformer 6-20

6.11.5 Disadvantages 6-20

6.11.6 Applications of Two Winding Transformer 6-20

6.12 Autotransformer 6-21

6.12.1 Advantages of Autotransformer 6-22

6.12.2 Disadvantages of an Autotransformer ... 6-22

6.12.3 Applications of an Autotransformer 6-22

6.12.4 Dimmerstat6-23

6.12.5 Comparison of Two Winding and Autotransformer6-23

• **Review Questions..... 6-23**

Unit IV

Chapter 7 : Diodes 7-1 to 7-26

Syllabus : Diode : Ordinary diode, LED, Photodiode and Zener diode : Construction, Symbol, Working, Characteristics, Applications etc.

7.1 Semiconductors 7-2

7.1.1 Types of Semiconductors 7-2

7.1.2 Conduction in Intrinsic Semiconductors .. 7-3

7.2 Extrinsic Semiconductors 7-3

7.2.1 n-type Semiconductors 7-4

7.2.2 p-type Semiconductors 7-5

7.3 Diffusion 7-6

7.4 Formation of P-N Junction Diode 7-6

7.4.1 Formation of the Depletion Region 7-7

7.4.2 Barrier Potential or Junction Potential (V_j) 7-7

7.5 A p-n Junction Diode 7-8

7.6 Operation of a p-n Junction Diode 7-8

7.7 The Volt Ampere (V-I) Characteristics of a Diode 7-10

7.7.1 V-I Characteristics of an Ideal Diode 7-11

7.7.2 V-I Characteristics of Silicon and Germanium Diodes 7-11

7.7.3 Mathematical Expression of the Diode Current 7-12

7.8 Diode as a Switch 7-12

7.9 Applications of p-n Junction Diode 7-13

7.9.1 Diode Testing 7-13

7.10 Zener Diode 7-14

7.10.1 V-I Characteristics of a Zener Diode 7-15

7.11 Breakdown Mechanisms in Zener Diode 7-15

7.11.1 Zener Breakdown 7-15

7.11.2 Avalanche Breakdown in Zener Diodes 7-16

7.11.3 Comparison of Breakdown Mechanisms 7-16

7.11.4 Comparison of Zener Diode and p-n Junction Diode 7-17

7.11.5 Applications of Zener Diode 7-17

7.11.6 The Zener Voltage Regulator 7-17

7.12 Light Emitting Diodes (LED) 7-21

7.12.1 Construction of LED 7-21

7.12.2 Principle of LED Operation 7-22

7.12.3 LED Voltage and Current 7-22

7.12.4 Output Characteristics of LED 7-22

7.12.5 Applications of LED 7-22

7.12.6 Seven Segment LED Display 7-23

7.12.7 Comparison of PN Junction Diode and LED 7-23

7.13 Photodiode 7-23

7.13.1 Construction and Operation 7-24

7.13.2 Photodiode Characteristics 7-24

7.13.3 Applications of Photodiode 7-25

7.13.4 Comparison of Diodes 7-25

• **Review Questions 7-26**

Unit IV

Chapter 8 : Transistor 8-1 to 8-18

Syllabus : Transistor : Construction, Types, Operation, Transistor configuration (CE, CB and CC) : Characteristics.

8.1 Introduction 8-2

 8.1.1 Bipolar Transistor Symbols and Types 8-2

8.2 Construction of a BJT 8-2

 8.2.1 An Unbiased Transistor 8-3

8.3 Transistor Biasing in the Active Region 8-3

8.4 Transistor Operation in the Forward Active Region 8-4

 8.4.1 Operation of npn Transistor 8-4

 8.4.2 Operation of PNP Transistor 8-5

8.5 Transistor Configurations 8-5

8.6 Common Base (CB) Configuration 8-6

 8.6.1 Current Relations in CB Configuration 8-6

 8.6.2 Current Gain (α or α_{dc}) 8-6

 8.6.3 Characteristics of a Transistor in Common Base Configuration 8-7

 8.6.4 Input Characteristics 8-7

 8.6.5 Output Characteristics of Transistor in CB Configuration 8-8

 8.6.6 Features of CB Configuration 8-9

8.7 Common Emitter (CE) Configuration 8-9

 8.7.1 Current Gain β of CE Configuration 8-10

 8.7.2 Relation between α_{dc} and β_{dc} 8-10

 8.7.3 Input Characteristics 8-10

 8.7.4 Output Characteristics 8-11

 8.7.5 Features of CE Configuration 8-12

8.8 Common Collector (CC) Configuration 8-13

 8.8.1 Practical Way to Draw CC Configuration 8-14

 8.8.2 Input Characteristics of n-p-n Transistor in CC Configuration 8-15

8.8.3 Output Characteristics of a n-p-n Transistor in CC Configuration 8-15

8.8.4 Features of CC Configuration 8-15

8.9 Comparison of Configurations 8-16

 8.9.1 Why is CE Configuration Most Preferred Configuration ? 8-16

 8.9.2 Transistor Applications 8-16

8.10 Transistor as a Switch 8-16

 8.10.1 Applications of Transistor as a Switch 8-17

• **Review Questions 8-17**

Unit IV

Chapter 9 : Digital Electronics 9-1 to 9-46

Syllabus : Logic Gates : Fundamental, Derived and exclusive logic gates : Symbol, Operation, Truth table, Timing diagram, Concept of universal gates.

Combinational Logic Circuit : Reduction of digital expressions by Boolean algebra and De Morgan's Theorem, Half and full adder.

Sequential Logic Circuit : Flip – Flop (SR, D, JK & T) : Construction, Working, Truth table, Types of triggering, 2 bit synchronous and asynchronous counter : Construction and operation.

9.1 Introduction 9-3

9.2 Signals and Systems 9-3

 9.2.1 Signals 9-3

 9.2.2 System or Circuit 9-3

9.3 Binary Logic and Logic Levels 9-4

 9.3.1 Positive and Negative Logic 9-4

9.4 Binary Addition 9-4

9.5 Rules of Binary Addition 9-4

9.6 Logic Operators 9-5

 9.6.1 NOT Operator (Inversion) 9-5

 9.6.2 AND Operator 9-5

 9.6.3 OR Operator 9-5



| | | | | | |
|--------|---|------|--------|--|------|
| 9.6.4 | Logic Gates | 9-5 | 9.18.1 | To Draw a Logic Circuit from Boolean Equation | 9-19 |
| 9.6.5 | Symbols and Truth Tables of Basic Gates | 9-6 | 9.18.2 | To Write a Boolean Expression for a Logic Circuit | 9-20 |
| 9.6.6 | Classification of Logic Gates | 9-6 | 9.18.3 | To Write the Boolean Expression from the Truth Table | 9-20 |
| 9.7 | NOT Gate or Inverter | 9-7 | 9.19 | Universal Gates | 9-21 |
| 9.7.1 | Operation for Pulsed Input | 9-7 | 9.19.1 | NAND Gate as a Universal Gate | 9-22 |
| 9.7.2 | Standard Package | 9-7 | 9.19.2 | NOR Gate as a Universal Gate | 9-23 |
| 9.8 | AND Gate | 9-7 | 9.19.3 | Solved Examples | 9-25 |
| 9.8.1 | Operation with Pulsed Inputs | 9-8 | 9.20 | Logic Circuits | 9-27 |
| 9.8.2 | Standard Package | 9-8 | 9.20.1 | Comparison of Combinational and Sequential Circuits | 9-28 |
| 9.9 | The OR Gate | 9-8 | 9.21 | Adders | 9-28 |
| 9.9.1 | Timing Diagram (Pulsed Operation) | 9-9 | 9.21.1 | Half Adder | 9-28 |
| 9.9.2 | Standard Package | 9-9 | 9.21.2 | Full Adder | 9-29 |
| 9.10 | The NAND Gate | 9-9 | 9.21.3 | Full Adder using Half Adders | 9-30 |
| 9.10.1 | Timing Diagram and Standard Package | 9-10 | 9.21.4 | Applications of Full Adder | 9-30 |
| 9.11 | The NOR Gate | 9-10 | 9.21.5 | Comparison of Half adder and Full Adder | 9-30 |
| 9.11.1 | Timing Diagram | 9-10 | 9.22 | Clock Signal | 9-31 |
| 9.11.2 | Standard Package | 9-11 | 9.23 | Latches and Flip-flop | 9-31 |
| 9.12 | EX-OR and EX-NOR Gates | 9-11 | 9.23.1 | 1-Bit Memory Cell | 9-31 |
| 9.12.1 | The EX-OR Gate | 9-11 | 9.23.2 | S-R Flip-flop using NAND Gates | 9-32 |
| 9.12.2 | The EX-NOR Gate | 9-12 | 9.23.3 | Triggering Methods | 9-33 |
| 9.12.3 | Examples of IC Gates | 9-13 | 9.24 | Edge Triggered S-R Flip-Flop | 9-34 |
| 9.13 | Boolean (Binary) Algebra | 9-13 | 9.24.1 | Positive Edge Triggered S-R Flip Flop | 9-34 |
| 9.14 | Boolean Laws | 9-14 | 9.24.2 | Negative Edge Triggered S-R Flip Flop .. | 9-35 |
| 9.14.1 | Other Important Rules | 9-15 | 9.25 | Edge Triggered D Flip Flop | 9-35 |
| 9.15 | De-Morgan's Theorems | 9-15 | 9.25.1 | Positive Edge Triggered D Flip Flop | 9-36 |
| 9.16 | Boolean Expression and Boolean Function | 9-16 | 9.25.2 | Negative Edge Triggered D Flip Flop | 9-37 |
| 9.17 | Truth Table Formation from a Given Boolean Equation | 9-16 | 9.26 | Edge Triggered J-K Flip Flop | 9-37 |
| 9.17.1 | Examples on Simplification of Logic Expression | 9-16 | | | |
| 9.18 | Writing Boolean Expression from a Logic Diagram | 9-19 | | | |



| | | | | | |
|--------|--|------|---------------------------------|--|------|
| 9.26.1 | Positive Edge Triggered JK Flip Flop | 9-37 | 9.28.1 | Types of Counters | 9-40 |
| 9.26.2 | Negative Edge Triggered JK flip-flop | 9-39 | 9.28.2 | Classification of Counters | 9-40 |
| 9.27 | Toggle Flip Flop (T Flip Flop) | 9-39 | 9.29 | A 2-Bit Asynchronous Up Counters | 9-41 |
| 9.27.1 | Positive Edge Triggered T-FF | 9-39 | 9.30 | Synchronous Counters | 9-42 |
| 9.27.2 | Negative Edge Triggered T Flip Flop | 9-39 | 9.30.1 | 2-Bit Synchronous up Counter | 9-42 |
| 9.27.3 | Application of T F/F | 9-40 | • Review Questions | 9-43 | |
| 9.27.4 | Applications of Flip Flops | 9-40 | | | |
| 9.28 | Counters | 9-40 | | | |

□□□