

**Unit-I****Chapter 1 : AC Fundamentals 1-1 to 1-30**

Syllabus : Generation of alternating voltage, Phasor representation of sinusoidal quantities, R, L, C circuit elements, its voltage and current response.

1.1	Introduction	1-2
1.2	Classification of Electric Networks	1-2
1.2.1	Active or Passive Networks	1-2
1.2.2	Unilateral or Bilateral Networks	1-2
1.2.3	Linear or Nonlinear Networks	1-2
1.3	Circuit Elements	1-2
1.3.1	Resistor and Resistance	1-2
1.3.2	Conductance G	1-3
1.3.3	Capacitors and Capacitance	1-3
1.3.4	Inductors	1-4
1.4	Generation of Alternating Voltage	1-4
1.4.1	Graphical and Mathematical Representation of Sinusoidal AC Quantities	1-5
1.5	Definitions of Various Terms Associated with Waveforms	1-6
1.5.1	Waveform	1-6
1.5.2	Instantaneous Value	1-6
1.5.3	Cycle	1-7
1.5.4	Time Period or Periodic Time (T)	1-7
1.5.5	Frequency	1-7
1.5.6	Amplitude	1-8
1.5.7	Peak and Peak to Peak Voltage	1-8
1.5.8	Effective or R.M.S. Value	1-9

1.5.9	Average Value	1-9
1.5.10	Form Factor	1-11
1.5.11	Crest Factor or Peak Factor (K_p)	1-11
1.5.12	Solved MSBTE Examples	1-11
1.6	Phasor Representation of an Alternative Quantity	1-15
1.7	Phase of an Alternating Quantity	1-16
1.7.1	Phase Angle	1-16
1.7.2	Phase Difference	1-16
1.7.3	Leading and Lagging Phase Difference	1-16
1.8	Mathematical Representation of Phasor	1-18
1.8.1	Polar Representation	1-18
1.8.2	Rectangular Representation	1-18
1.8.3	Conversion from Polar to Rectangular	1-18
1.8.4	Rectangular to Polar Conversion	1-18
1.8.5	Addition and Subtraction of Phasors (using Rectangular Form)	1-18
1.8.6	Multiplication and Division of Phasors (using Polar Form)	1-18
1.9	Single Phase AC Circuits	1-21
1.9.1	Reactance and Impedance	1-21
1.9.2	Inductive Reactance (X_L)	1-21
1.9.3	Capacitive Reactance (X_C)	1-21
1.9.4	Impedance (Z)	1-21
1.10	Purely Resistive AC Circuit	1-22
1.10.1	Analysis of the Purely Resistive AC Circuit	1-22



<p>1.10.2 Voltage and Current Waveforms and Equations 1-22</p> <p>1.10.3 Phasor Diagram 1-23</p> <p>1.10.4 Impedance of the Purely Resistive Circuit 1-23</p> <p>1.10.5 Average Power (P_{av}) 1-23</p> <p>1.11 Purely Inductive AC Circuit 1-23</p> <ul style="list-style-type: none"> 1.11.1 Equations for Current i and Voltage v .. 1-24 1.11.2 Waveforms and Phasor Diagram 1-25 1.11.3 Power in a Purely Inductive Circuit 1-25 1.11.4 Impedance of a Purely Inductive Circuit 1-25 <p>1.12 Purely Capacitive AC Circuit 1-27</p> <ul style="list-style-type: none"> 1.12.1 Equation for Voltage and Current 1-27 1.12.2 Current and Voltage Waveforms and Phasor Diagram 1-28 1.12.3 Power in Purely a Capacitive AC Circuit 1-28 1.12.4 Impedance of a Purely Capacitive Circuit 1-29 1.12.5 Comparison of Purely Inductive and Purely Capacitive Circuits 1-29 <p>1.13 I-Scheme Questions and Answers 1-30</p> <ul style="list-style-type: none"> • Review Questions 1-30 	<p>Unit-I</p> <p>Chapter 2 : Single Phase AC Series Circuits 2-1 to 2-48</p> <p>Syllabus : R-L, R-C, R-L-C combination of AC series circuit, Impedance, Reactance, Impedance triangle, Power factor, Active power, Reactive power, Apparent power, Power triangle and vector diagram, Resonance, Bandwidth, Quality factor and voltage magnification in series R-L, R-C and R-L-C circuit.</p> <p>2.1 Single Phase AC Circuits..... 2-2</p> <p>2.1.1 Reactance and Impedance 2-2</p> <p>2.1.2 Reactance 2-2</p> <p>2.1.3 Inductive Reactance (X_L) 2-2</p> <p>2.1.4 Capacitive Reactance (X_C) 2-2</p> <p>2.1.5 Impedance (Z) 2-2</p> <p>2.2 Concept of Impedance Triangle 2-2</p> <p>2.3 Important Terms Related to Power 2-3</p> <ul style="list-style-type: none"> 2.3.1 Apparent Power (S) 2-3 2.3.2 Real Power or True Power or Active Power (P) 2-3 2.3.3 Reactive Power or Imaginary Power (Q) 2-3 2.3.4 Different Powers and Their Units 2-4 2.3.5 Power Factor 2-4 2.3.6 Importance (Significance) of Power Factor 2-5 2.3.7 Causes of Low Power Factor 2-5 2.3.8 Power Triangle 2-5 <p>2.4 AC Circuits with Series Elements 2-6</p> <p>2.5 The Series R-L Circuit 2-6</p> <ul style="list-style-type: none"> 2.5.1 Phasor Diagram 2-6 2.5.2 Impedance of L-R Series Circuit 2-7 2.5.3 Impedance Triangle 2-7 2.5.4 Voltage and Current Waveforms 2-7 2.5.5 Average Power in Series L-R Circuit 2-8 2.5.6 Power Triangle for L-R Series Circuit 2-8 2.5.7 Apparent Power (S) 2-8
-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------	-------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------



2.5.8 Real Power or True Power or Active Power (P)	2-8	2.8.1 Resonance in Series RLC Circuit	2-33
2.5.9 Reactive Power or Imaginary Power (Q)	2-9	2.8.2 Resonant Frequency (f_r)	2-33
2.5.10 Power Factor	2-9	2.8.3 Phasor Diagrams of RLC Series Resonant Circuit	2-34
2.5.11 Q-Factor	2-9	2.8.4 Impedance at Resonance	2-35
2.6 The Series R-C Circuit	2-15	2.8.5 Current at Resonance	2-36
2.6.1 Phasor Diagram	2-15	2.8.6 Phase Angle of Series Resonant Circuit	2-36
2.6.2 Impedance of RC Series Circuit	2-16	2.8.7 Voltage and Current	2-36
2.6.3 Impedance Triangle (Series R-C Circuit)	2-16	2.8.8 Variation of Power Factor	2-36
2.6.4 Phase Relationship between Voltage and Current (Series R-C Circuit)	2-16	2.8.9 The Q-Factor (Quality Factor) of a Series Resonant Circuit	2-37
2.6.5 Average Power in Series R-C Circuit	2-17	2.8.10 Bandwidth of a Series Resonant Circuit	2-37
2.6.6 Power Triangle for R-C Series Circuit	2-17	2.8.11 Magnification in Series Resonant Circuit	2-38
2.6.7 Various Powers and Power Factor	2-17	2.8.12 Characteristics of Series Resonant Circuit	2-39
2.6.8 Q-Factor	2-18	2.9 I-Scheme Solved Examples	2-43
2.7 An R-L-C Series Circuit	2-22	2.10 I-Scheme Questions and Answers	2-47
2.7.1 Importance of the Values of Reactances	2-22	• Review Questions.....	2-46
2.7.2 Phasor Diagrams	2-22	Unit-II	
2.7.3 Phasor Diagram for : $X_L > X_C$	2-22	Chapter 3 : Single Phase AC Parallel Circuits	
2.7.4 Phasor Diagram for : $X_L < X_C$	2-23	3-1 to 3-31	
2.7.5 Phasor Diagram for : $X_L = X_C$	2-23		
2.7.6 Impedance of Series LCR Circuit	2-23		
2.7.7 Impedance Triangle for an LCR Circuit	2-24		
2.7.8 Power Supplied to the R.L.C. Circuit	2-24		
2.7.9 Power Triangle	2-24		
2.7.10 Various Powers and Power Factors of RLC Series Circuit	2-24		
2.7.11 Figure of Merit or Q-factor	2-25		
2.8 Resonance	2-32		

Syllabus : R-L, R-C, R-L-C parallel combination of AC circuits, Impedance, Reactance, Phasor diagram, Impedance triangle, R-L, R-C, R-L-C parallel AC circuit, Power factor, Active power, Apparent power, Reactive power, Power triangle, Resonance in parallel R-L, R-C, R-L-C circuit, Bandwidth, Quality factor and Voltage magnification.



3.1	A.C. Parallel Circuit	3-2	3.7.1	Conductance and Susceptance	3-8
3.1.1	Two Impedances in Parallel	3-2	3.7.2	Admittance Triangle	3-8
3.2	Multiplication and Division of Impedances	3-2	3.7.3	Solved Examples on Parallel Circuits	3-9
3.2.1	Multiplication of Impedances	3-3	3.8	Resonance in Parallel RLC Circuit	3-16
3.2.2	Division of Impedances	3-3	3.8.1	Resonant Frequency (f_r)	3-17
3.3	Parallel AC Circuits	3-3	3.8.2	Dynamic Impedance at Resonance (Z_D)	3-17
3.4	Resistance in Parallel with Pure Inductance (R-L Parallel Circuit)	3-3	3.8.3	Current and Voltage	3-18
3.4.1	Phasor Diagram	3-4	3.8.4	Phase Angle of Parallel Resonant Circuit	3-18
3.4.2	Impedance	3-4	3.8.5	Why is the Parallel Circuit Called a Rejector Circuit ?.....	3-19
3.4.3	Voltage and Current Waveforms	3-4	3.8.6	Q-Factor of the Parallel Circuit	3-19
3.4.4	Power Factor	3-4	3.8.7	Effect of Q on Bandwidth	3-19
3.4.5	Active Power (P)	3-4	3.8.8	Magnification in Parallel Resonant Circuit	3-20
3.4.6	Reactive Power (Q)	3-5	3.8.9	Current Through C	3-20
3.4.7	Apparent Power (S)	3-5	3.8.10	Characteristics of Parallel Resonant Circuit	3-20
3.5	Resistance in Parallel with Pure Capacitance	3-5	3.8.11	Comparison of Series and Parallel Resonant Circuits	3-21
3.5.1	Phasor Diagram	3-5	3.9	MSBTE Questions and Answers	3-27
3.5.2	Impedance	3-5	3.10	I-Scheme Solved Examples	3-27
3.5.3	Voltage and Current Waveforms	3-5	3.11	I-Scheme Questions and Answers	3-30
3.5.4	Power Factor	3-6		• Review Questions.....	3-26
3.5.5	Active Power (P)	3-6		Unit-III	
3.5.6	Reactive Power (Q)	3-6			
3.5.7	Apparent Power (S)	3-6			
3.6	Series Combination of R and L in Parallel with Capacitor	3-6			
3.6.1	Phasor Diagram	3-6			
3.6.2	Impedance	3-6			
3.6.3	Power Factor	3-7			
3.7	The Concept of Admittance	3-7	4.1	Introduction to Polyphase AC Circuits	4-2

Chapter 4 : Three Phase Circuits**4-1 to 4-32**

Syllabus : Phasor and complex representation of three phase supply, Phase sequence and polarity. Types of three phase connections, Phase and line quantities in three phase star and delta system, Balanced and unbalanced load. Neutral shift in unbalanced load, Three phase power, Active, Reactive and Apparent power in star and delta system.



4.1.1 Why to use a Polyphase System ?4-2	4.7.1 Line Voltages and Phase Voltages for Delta Connected Supply4-17
4.1.2 How Many Phases ?4-2	4.7.2 Phase and Line Voltages in Delta Connections4-18
4.1.3 Three Phase Supply Waveforms4-2	4.7.3 Line Current and Phase Current for Delta Connection4-18
4.2 Advantages of Polyphase Systems over Single Phase System4-2	4.7.4 The Complete Phasor Diagram for Delta Load4-19
4.2.1 Comparison of Single Phase and Three Phase Systems4-3	4.7.5 Power Relations4-20
4.3 Generation of Three Phase Emf4-3	4.7.6 Power Triangle4-20
4.3.1 Complex and Phasor Representation of the Three Phase Voltages4-4	4.7.7 Power Factor4-21
4.3.2 Concept of Symmetrical or Balanced System 4-5	4.7.8 Comparison of Star and Delta Connections4-21
4.3.3 Concept of Phase Sequence4-5	4.8 Applications of 3 Phase AC Circuits4-29
4.4 Types of Three Phase Supply Connections4-5	4.9 I-Scheme Solved Examples.....4-30
4.4.1 Star Connection (Wye Connection)4-6	4.10 MSBTE Questions and Answers4-31
4.4.2 Delta Connection4-6	4.11 I-Scheme Questions and Answers4-32
4.5 Types of Loads4-6	• Review Questions.....4-30
4.5.1 Balanced or Unbalanced Load4-6	Unit-IV
4.5.2 Comparison of Balanced and Unbalanced Load4-7	Chapter 5 : Principles of DC Circuit Analysis
4.5.3 Neutral Shift in Unbalanced Load4-8	5-1 to 5-37
4.6 Relations between Voltages and Current for a Balanced Star Load4-8	Syllabus : Source transformation, Star/delta and Delta/star transformations, Mesh analysis, Node analysis.
4.6.1 Line Voltages and Phase Voltages4-8	5.1 Basic Definitions.....5-2
4.6.2 Typical Values of Line and Phase Voltages for Star Connected Supply4-8	5.1.1 Network or Circuit5-2
4.6.3 Relation between Phase and Line Current4-9	5.1.2 Concept of Open and Short Circuit5-2
4.6.4 Relation between Phase and Line Voltages4-9	5.1.3 Branch, Mesh and Node5-2
4.6.5 The Complete Phasor Diagram4-10	5.2 Source Transformation5-3
4.6.6 Power Relations4-10	5.2.1 Conversion of Voltage Source to Current Source5-3
4.6.7 Power Triangle4-11	5.2.2 Conversion of Current Source to Voltage Source5-4
4.6.8 Power Factor for Star Load4-11	5.2.3 Voltage Sources in Series5-5
4.6.9 Solved Examples on Star Load4-11	5.2.4 Current Sources in Parallel5-5
4.7 Voltage, Current and Power Relation in a Balanced Delta Load4-17	



5.3 Star-Delta and Delta-Star Transformation5-6	6.3 Superposition Theorem6-3
5.3.1 The Star Network5-6	6.3.1 Statement of the Superposition Theorem6-3
5.3.2 The Delta Network5-6	6.3.2 Steps to be Followed to Apply the Superposition Theorem6-3
5.3.3 Delta-Star Transformation5-7	6.3.3 Applications of the Superposition Theorem6-3
5.3.4 Star to Delta Conversion5-9	6.3.4 Drawbacks of the Superposition Theorem6-3
5.4 Kirchhoff's Laws5-10	6.3.5 Examples on Superposition Theorem6-4
5.4.1 Kirchhoff's Current Law (KCL)5-10	6.4 Thevenin's Theorem.....6-19
5.4.2 Node Based Analysis (Nodal Analysis)5-12	6.4.1 Steps for the Thevenin's Theorem6-21
5.5 Mesh or Loop and Sign Convention5-21	6.4.2 Advantages of Thevenin's Theorem6-21
5.5.1 Kirchhoff's Voltage Law (or Mesh or Loop Law)5-22	6.4.3 Where can't We Apply the Thevenin's Theorem ?.....6-21
5.5.2 Procedure to be Followed to Solve an Example using Kirchhoff's Laws5-22	6.4.4 Applications of the Thevenin's Theorem6-21
5.5.3 Mesh Analysis or Maxwell's Loop Current Method5-24	6.4.5 Drawbacks of the Thevenin's Theorem6-22
5.6 MSBTE Questions and Answers5-32	6.4.6 Solved Examples on Thevenin's Theorem6-22
5.7 I-Scheme Solved Examples5-32	6.5 Norton's Theorem6-33
5.8 I-Scheme Questions and Answers5-36	6.5.1 Statement of Norton's Theorem6-33
• Review Questions5-32	6.5.2 Equivalence between Thevenin's and Norton's Theorems6-34

Unit-V**Chapter 6 : Network Theorems 6-1 to 6-62**

Syllabus : Superposition theorem, Thevenin's theorem, Norton's theorem, Maximum power transfer theorem, Reciprocity theorem, Duality in electric circuits.

6.1 Introduction6-2
6.2 Types of Networks6-2
6.2.1 Active or Passive Networks6-2
6.2.2 Unilateral or Bilateral Networks6-2
6.2.3 Linear or Nonlinear Networks6-2

6.3 Superposition Theorem6-3
6.3.1 Statement of the Superposition Theorem6-3
6.3.2 Steps to be Followed to Apply the Superposition Theorem6-3
6.3.3 Applications of the Superposition Theorem6-3
6.3.4 Drawbacks of the Superposition Theorem6-3
6.3.5 Examples on Superposition Theorem6-4
6.4 Thevenin's Theorem.....6-19
6.4.1 Steps for the Thevenin's Theorem6-21
6.4.2 Advantages of Thevenin's Theorem6-21
6.4.3 Where can't We Apply the Thevenin's Theorem ?.....6-21
6.4.4 Applications of the Thevenin's Theorem6-21
6.4.5 Drawbacks of the Thevenin's Theorem6-22
6.4.6 Solved Examples on Thevenin's Theorem6-22
6.5 Norton's Theorem6-33
6.5.1 Statement of Norton's Theorem6-33
6.5.2 Equivalence between Thevenin's and Norton's Theorems6-34
6.5.3 Applications of the Norton's Theorem6-35
6.6 Maximum Power Transfer Theorem6-46
6.6.1 Statement of Maximum Power Transfer Theorem6-46



6.6.2 Condition for Maximum Power Transfer6-47	6.8 Principle of Duality6-55 6.8.1 Graphical Method of Constructing a Dual Network6-56
6.6.3 Applications of Maximum Power Transfer Theorem6-47	6.9 I-Scheme Solved Examples6-58
6.7 Reciprocity Theorem6-53 6.7.1 Explanation of Reciprocity Theorem6-53 6.7.2 Drawbacks of the Reciprocity Theorem6-55	6.10 I-Scheme Questions and Answers6-61 • Review Questions.....6-58

