

**Unit - I**

**Chapter 1 : Fundamental Concepts of DC Circuits**

**1-1 to 1-36**

**Syllabus** : Electric potential, EMF, Current, Power and Energy. Conductor, Semiconductor and Insulator-properties and Applications. Resistor, Inductor and Capacitor. **Resistor**, Properties and Practical applications, Classification based on ohmic value and material, Effect of temperature on resistance and temperature coefficient of resistance. Conductance, Conductivity, Current density. **Ohm's law** : Applications and limitations. Kirchhoff's voltage law and Kirchhoff's current law. Joule's law of heating, Applications. Power and Energy, Unit conversion from mechanical to electrical and vice-versa, Impact of using electrical source over the other energy sources on the environment.

1.1	Network or Circuit .....	1-2
1.2	EMF and Current .....	1-2
1.2.1	EMF .....	1-2
1.2.2	Electric Current .....	1-2
1.3	Electric Potential .....	1-3
1.3.1	Potential Difference (P.D.) .....	1-3
1.3.2	Difference between EMF and PD .....	1-3
1.4	Power (P) .....	1-4
1.5	Energy (E) .....	1-4
1.6	Classification of Solids .....	1-5
1.6.1	Conductors (or Metals) .....	1-5
1.6.2	Insulators .....	1-5
1.7	Semiconductors .....	1-6
1.7.1	Types of Semiconductors .....	1-7
1.7.2	Comparison of Conductor, Insulator and Semiconductor .....	1-7
1.8	Resistors .....	1-7
1.8.1	Resistance (R) .....	1-8
1.8.2	Factors Affecting the Resistance Value .....	1-8
1.8.3	Resistivity or Specific Resistance ( $\rho$ ) .....	1-8
1.9	Capacitors .....	1-10
1.9.1	Capacitance .....	1-10
1.10	Inductors .....	1-11
1.11	Resistor Specifications (Properties) .....	1-11
1.11.1	Resistor-Practical Applications .....	1-12
1.11.2	Classification Based on Ohmic Value .....	1-12
1.11.3	Effect of Temperature on Resistance .....	1-13

1.11.4	Effect of Temperature on Resistance of Alloys .....	1-13
1.11.5	Effect of Temperature on Resistance of Insulators .....	1-13
1.11.6	Effect of Temperature on Resistance of Semiconductors .....	1-14
1.12	Resistance Temperature Coefficient (R.T.C.) .....	1-14
1.12.1	Expression for Resistance at $t^{\circ}\text{C}$ .....	1-15
1.12.2	Effect of Temperature on R.T.C. .....	1-15
1.12.3	Conductance (G) .....	1-17
1.12.4	Conductivity ( $\sigma$ ) .....	1-17
1.12.5	Current Density .....	1-17
1.13	Ohm's Law .....	1-18
1.13.1	Limitations of ohm's law .....	1-18
1.13.2	Applications of ohm's Law .....	1-18
1.14	Important Definitions .....	1-18
1.14.1	Circuit Element .....	1-18
1.14.2	Open Circuit .....	1-18
1.14.3	Short Circuit .....	1-19
1.14.4	Branch .....	1-19
1.14.5	Mesh or Loop .....	1-19
1.14.6	Node or Junction .....	1-19
1.15	Kirchhoff's Laws .....	1-19
1.15.1	Kirchhoff's Current Law (KCL) .....	1-19
1.16	Mesh or Loop and Sign Convention .....	1-21
1.16.1	Kirchhoff's Voltage Law (KVL) .....	1-22
1.17	Types of Connections .....	1-23
1.17.1	Series Connection of Resistors .....	1-23
1.17.2	Parallel Connection of Resistors .....	1-24
1.18	Joule's Law of Heating .....	1-25
1.18.1	Applications of Joule's Law .....	1-26
1.19	SI Units of Work, Power and Energy .....	1-26
1.19.1	SI Units of Work, Power and Energy for a Mechanical System .....	1-26
1.19.2	SI Units of Work, Power and Energy for Electrical System .....	1-27
1.19.3	Equivalence between Various Units of Energy .....	1-28
1.19.4	Efficiency of a System .....	1-28
1.20	Impact of Using Electrical Source Over the Other Energy Sources on the Environment .....	1-30
1.21	1 Mark or 2 Marks UQs with Answers .....	1-35
	<b>• Review Questions .....</b>	<b>1-31</b>

**Unit - II****Chapter 2 : Network Solution Techniques 2-1 to 2-28**

**Syllabus :** Node, Branch, Loop, Mesh ; Open, Closed and Short circuit. Series and Parallel connections of resistors and equivalent resistance. Source transformation techniques. Mesh analysis, Nodal Analysis. Duality in electrical networks.

2.1	Introduction to Networks / Circuits .....	2-2
2.1.1	Network .....	2-2
2.1.2	Circuit Element .....	2-2
2.1.3	Open Circuit .....	2-2
2.1.4	Short Circuit .....	2-2
2.1.5	Branch .....	2-2
2.1.6	Mesh or Loop .....	2-3
2.1.7	Node or Junction .....	2-3
2.2	Circuit Simplification Techniques .....	2-3
2.2.1	Series Circuits (Resistors in Series) .....	2-3
2.2.2	Parallel Circuit (Resistors in Parallel) .....	2-5
2.2.3	Current Division in Parallel Resistors .....	2-7
2.2.4	Voltage Division in Series Resistors .....	2-8
2.2.5	Comparison between Series and Parallel Circuits .....	2-9
2.3	Voltage and Current Sources .....	2-13
2.3.1	Independent Voltage Sources .....	2-13
2.3.2	Current Sources .....	2-14
2.4	Source Transformation Techniques .....	2-15
2.4.1	Voltage Source to Current Source .....	2-15
2.4.2	Current Source to Voltage Source .....	2-16
2.4.3	Voltage Sources in Series .....	2-17
2.4.4	Current Sources in Parallel .....	2-17
2.5	Nodal Analysis .....	2-19
2.5.1	Procedure for using KVL .....	2-20
2.5.2	Mesh Analysis .....	2-21
2.6	Duality in Electrical Networks .....	2-24
2.6.1	Graphical Method of Constructing a Dual Network .....	2-25
2.7	1 Mark or 2 Marks UQs with Answers .....	2-28
	• <b>Review Questions.....</b>	<b>2-27</b>

**Unit - III****Chapter 3 : Network Theorems 3-1 to 3-30**

**Syllabus : Types of electric circuits :** Active and Passive, Linear and Nonlinear, Unilateral and Bilateral circuit. Superposition theorem, Equivalent circuit. Thevenin's theorem, Equivalent circuit. Norton's theorem, Equivalent circuit. Maximum power transfer theorem. 'T' to 'Pi' network conversion (Star-Delta transformation) and 'Pi' to 'T' network conversion (Delta-Star transformation).

3.1	Introduction .....	3-2
3.2	Classification of Electric Networks .....	3-2
3.2.1	Active or Passive Network .....	3-2
3.2.2	Bilateral or Unilateral Network .....	3-2
3.2.3	Linear or Nonlinear Network .....	3-2
3.3	Superposition Theorem .....	3-3
3.4	Thevenin's Theorem .....	3-8
3.5	Norton's Theorem .....	3-14
3.5.1	Equivalence between Thevenin's and Norton's Theorems .....	3-15
3.6	Maximum Power Transfer Theorem .....	3-17
3.7	Star-Delta and Delta-Star Conversion .....	3-19
3.7.1	The Star (T) Network .....	3-20
3.7.2	The Delta ( $\pi$ ) Network .....	3-20
3.7.3	Delta-Star Conversion .....	3-20
3.7.4	Star to Delta Conversion .....	3-23
3.8	1 Mark or 2 Marks UQs with Answers .....	3-30
	• <b>Review Questions .....</b>	<b>3-27</b>

**Unit - IV****Chapter 4 : Capacitors & Its Applications 4-1 to 4-40**

**Syllabus : Capacitor :** Function, Types, Applications, Capacitance, Capacitive reactance, Factors affecting capacitance. Behaviour of capacitors in DC circuits, Charging and Discharging of capacitor, RC time constant, Energy stored in capacitor. Series and Parallel combination of capacitors. Capacitance of parallel plate capacitor and Spherical capacitor. Batteries, Ratings, Types and Their comparison. Identification of weak battery in series and Parallel combination. Recycling, Disposal of old capacitors and Batteries safely.

4.1	Static Electricity .....	4-2
4.2	Coulomb's Laws .....	4-2
4.3	Electrostatic Field .....	4-2
4.3.1	Electrostatic Flux Lines .....	4-2



4.4	Electric Flux .....	4-2	4.18	Batteries .....	4-22
4.5	Electric Flux Density (D) .....	4-2	4.18.1	Battery Types .....	4-22
4.6	Electric Field Strength or Field Intensity .....	4-2	4.19	Construction of a Lead-Acid Battery .....	4-23
4.7	Permittivity ( $\epsilon$ ) .....	4-3	4.20	Characteristics of Lead Acid Battery .....	4-24
4.7.1	Absolute Permittivity ( $\epsilon$ ) .....	4-3	4.20.1	Cell Efficiency .....	4-25
4.7.2	Permittivity of Free Space ( $\epsilon_0$ ) .....	4-3	4.20.2	Battery Ratings .....	4-25
4.7.3	Relative Permittivity ( $\epsilon_r$ ) .....	4-3	4.21	Maintenance of Lead Acid Battery .....	4-26
4.8	Concept of Capacitor .....	4-3	4.21.1	Testing Procedure for Lead Acid Car Batteries .....	4-26
4.8.1	Types of Capacitors .....	4-4	4.21.2	Precautions to be Taken for Lead Acid Batteries .....	4-26
4.8.2	Capacitance .....	4-4	4.21.3	Battery Aging .....	4-26
4.8.3	Factors Affecting the Capacitance .....	4-4	4.21.4	Applications of Lead - Acid (Storage) Batteries.....	4-26
4.8.4	Classification of Capacitors .....	4-5	4.22	Series and Parallel Connection of Batteries .....	4-27
4.9	Classification of Fixed Capacitors .....	4-5	4.22.1	Series Connection of Batteries .....	4-27
4.9.1	Air capacitors .....	4-5	4.22.2	Parallel Connection of Batteries .....	4-27
4.9.2	Paper Capacitors .....	4-5	4.23	Alkaline Batteries .....	4-28
4.9.3	Mica Capacitors .....	4-6	4.24	Nickel - Iron Cell .....	4-28
4.9.4	Ceramic Capacitors .....	4-6	4.24.1	Action of the Cell .....	4-28
4.9.5	Polycarbonate Capacitors .....	4-7	4.24.2	Nickel - Iron Battery .....	4-28
4.9.6	Aluminium Electrolytic Capacitors .....	4-7	4.24.3	Electrical Characteristics .....	4-28
4.9.7	Glass Capacitors .....	4-7	4.24.4	Capacity of Nickel - Iron Battery .....	4-29
4.9.8	Tantalum Electrolytic Capacitors .....	4-7	4.24.5	A-H and W-H Efficiencies .....	4-29
4.9.9	Tantalum Foil Capacitor .....	4-8	4.24.6	Merits of Nickel - Iron Batteries .....	4-29
4.10	Behaviour of Capacitors in DC Circuits .....	4-8	4.24.7	De-Merits of Nickel - Iron Batteries .....	4-29
4.10.1	Charging of a Capacitor .....	4-8	4.24.8	Maintenance of Nickel - Iron Batteries ...	4-29
4.10.2	Discharging of a Capacitor .....	4-9	4.24.9	Applications of Nickel - Iron Batteries ....	4-29
4.11	Energy Stored in a Capacitor .....	4-11	4.25	Nickel - Cadmium Cell .....	4-29
4.12	Capacitors in Series .....	4-12	4.25.1	Action During Discharging .....	4-30
4.13	Capacitors in Parallel .....	4-13	4.25.2	Action During Charging .....	4-30
4.14	Capacitance of a Parallel Plate Capacitor .....	4-17	4.25.3	Construction of Ni-Cd Battery .....	4-30
4.14.1	Spherical Condensers .....	4-19	4.25.4	Charging Methods .....	4-30
4.15	Recycling of Old Capacitors .....	4-19	4.25.5	Applications of Ni-Cd Batteries .....	4-30
4.16	Batteries and Cells .....	4-20	4.26	Comparison of Various Batteries .....	4-30
4.16.1	Cells .....	4-20	4.27	Identification of a Weak Battery .....	4-31
4.16.2	Battery .....	4-20	4.28	Safe Disposal of Batteries .....	4-31
4.16.3	Primary and Secondary Cells .....	4-20	4.29	1 Mark or 2 Marks UQs with Answers .....	4-40
4.17	The Lead-Acid Cell .....	4-21		<b>• Review Questions .....</b>	<b>4-32</b>
4.17.1	Construction .....	4-21			
4.17.2	Working of a Lead - Acid Cell .....	4-21			

**Unit - V****Chapter 5 : Magnetism & Electromagnetism 5-1 to 5-40**

**Syllabus :** Flux, Flux density (B), Magnetic field intensity (H), M.M.F, Magnetic lines of force, Permeability, Hysteresis loop, Reluctance, Leakage factor, B-H Curve. Comparison of magnetic and Electric circuit. Electromagnetism, Electromagnetic field around a current carrying conductor. Faraday's laws of electromagnetic induction, Fleming's right and left-hand rule, Lenz's Law. Induced EMF, Self (Static and Dynamically induced emf) and Mutually induced emf and Their applications. Self and Mutual inductance, Inductive reactance, Coefficient of self and Mutual inductance. Inductance in series and Parallel.

**Inductors :** Function types, Construction and Applications, Energy stored in an inductor.

5.1	Introduction .....	5-2	5.9	B-H Curve or Magnetization Curve .....	5-9
5.1.1	Magnet .....	5-2	5.9.1	Magnetic Hysteresis and Hysteresis Loop .....	5-10
5.1.2	Electromagnets .....	5-2	5.9.2	Hysteresis Loss .....	5-10
5.2	Definitions Related to Magnetism .....	5-2	5.9.3	Hysteresis Loop for Magnetic and Non-Magnetic Materials .....	5-10
5.2.1	Laws of Magnetism .....	5-2	5.10	Leakage Flux and Fringing .....	5-11
5.2.2	Magnetic Field .....	5-2	5.10.1	Leakage Flux .....	5-11
5.2.3	Magnetic Lines of Force .....	5-2	5.10.2	Magnetic Fringing .....	5-12
5.2.4	Magnetic Flux $\phi$ .....	5-3	5.11	Electromagnetic Induction .....	5-12
5.2.5	Magnetic Flux Density (B) .....	5-3	5.11.1	Faraday's Laws of Electromagnetic Induction .....	5-13
5.2.6	Magnetic Field Strength (H) .....	5-3	5.11.2	Direction of Induced E.M.F. ....	5-13
5.3	Magnetic Effects of Electric Current .....	5-3	5.11.3	Fleming's Right Hand Rule .....	5-13
5.3.1	Dot and Cross Conventions .....	5-3	5.11.4	Lenz's Law .....	5-14
5.3.2	Rules for Direction of Magnetic Field .....	5-4	5.12	Fleming's Left Hand Rule .....	5-15
5.3.3	The Right Hand Gripping Rule (or Right Hand Thumb Rule) .....	5-4	5.13	Nature of the Induced E.M.F. ....	5-15
5.4	Magnetic Field Associated with a Straight Conductor .....	5-4	5.14	Dynamically Induced E.M.F. ....	5-16
5.5	Magnetic Field due to Solenoid .....	5-5	5.14.1	Magnitude of Dynamically Induced E.M.F. ....	5-16
5.5.1	Right Hand Thumb Rule .....	5-5	5.15	Statically Induced E.M.F. ....	5-17
5.6	Permeability .....	5-5	5.15.1	Self Induced E.M.F. ....	5-18
5.6.1	Absolute Permeability ( $\mu$ ) .....	5-5	5.15.2	Self Inductance .....	5-18
5.6.2	Permeability of Free Space or Vacuum ( $\mu_0$ ) .....	5-6	5.15.3	Factors Affecting the Self Inductance ....	5-19
5.6.3	Relative Permeability ( $\mu_r$ ) .....	5-6	5.15.4	Mutually Induced E.M.F. ....	5-19
5.7	MMF, Reluctance and Permeance .....	5-6	5.15.5	Mutual Inductance (M) .....	5-20
5.7.1	Magneto motive Force (MMF) .....	5-6	5.15.6	Expression for Mutual Inductance .....	5-20
5.7.2	Reluctance (S) .....	5-7	5.15.7	Coefficient of Coupling (K) .....	5-20
5.7.3	Permeance .....	5-7	5.15.8	Comparison of Statically and Dynamically Induced E.M.F. ....	5-21
5.8	Magnetic Circuit .....	5-7	5.16	Inductances in Series .....	5-23
5.8.1	Expressions for Various Quantities .....	5-8	5.16.1	Series Aiding or Cumulative Coupling ..	5-23
5.8.2	Comparisons of Magnetic and Electrical Circuits .....	5-8	5.16.2	Series Opposition or Differential Coupling .....	5-24
			5.16.3	Series and Parallel Combinations of Isolated Inductances : Series Connection .....	5-24
			5.17	Inductors .....	5-25
			5.17.1	Types of Inductor .....	5-25
			5.18	Types of Fixed Inductor .....	5-25
			5.18.1	Air-core inductor .....	5-25
			5.18.2	Iron-core Inductor .....	5-26
			5.18.3	Ferrite core Inductor .....	5-26
			5.18.4	Toroidal Inductor .....	5-27
			5.19	Variable Inductors .....	5-27
			5.20	Energy Stored in an Inductor .....	5-28
			5.21	1 Mark or 2 Marks UQs with Answers .....	5-39
				• <b>Review Questions</b> .....	<b>5-29</b>

