

**Chapter 1 : Power Electronics 1-1 to 1-2**

1.1	Introduction to Power Electronics	1-1
1.1.1	Principle of Power Electronics	1-1
1.1.2	Application Areas of Power Electronics ...	1-1
1.2	Power Semiconductor Devices	1-1
1.2.1	Need of High Power Semiconductor Switches	1-2
1.2.2	General Requirements of Power Devices	1-2
1.3	MSBTE Questions and Answers	1-2

Unit - I**Chapter 2 : Thyristor Family Devices 2-1 to 2-41**

Syllabus : SCR : Construction, Operating principle with two transistor analogy, V-I characteristics, Latching current (I_L) and holding current (I_H). Applications of SCR. Thyristor family devices : LASCR, SCS, GTO and TRIAC : Power MOSFET and IGBT : Construction, Operating principle, V-I characteristics and applications.

Triggering devices : UJT, PUT, SUS, SBS and DIAC : Construction, Operating principle, V-I characteristics and applications.

2.1	Introduction to Thyristors Family Devices	2-1
2.1.1	Applications of Thyristors	2-1
2.1.2	Silicon Controlled Rectifier (SCR)	2-1
2.1.3	Important Features of SCR	2-2
2.1.4	Construction of SCR	2-2
2.1.5	I-V Characteristics (Static Characteristics)	2-2
2.1.6	Operation of SCR	2-5
2.1.7	Two Transistor Analogy of SCR	2-5
2.1.8	SCR as a Switch	2-6
2.1.9	Applications of SCR	2-6
2.2	Bidirectional Triode SCRs (TRIACs)	2-6
2.2.1	Construction of a TRIAC	2-6
2.2.2	V-I Characteristics of TRIAC (Static Characteristics)	2-7
2.3	Modes of Operation of TRIAC	2-8
2.3.1	Operating Modes of TRIAC	2-8
2.3.2	Applications of TRIAC	2-10
2.4	Gate Turn Off SCR (GTO)	2-10
2.4.1	Construction of GTO	2-10
2.4.2	Operating Principle	2-11
2.4.3	GTO Turn off Mechanism	2-11

2.4.4	Magnitude of $I_G^{(-)}$ for Reliable Turn Off of GTO	2-12
2.4.5	I-V Characteristics of GTO	2-12
2.4.6	Other Important Characteristics of GTO	2-12
2.4.7	Advantages of GTO over SCR	2-12
2.4.8	Applications of GTO	2-13
2.5	Silicon Controlled Switch (SCS)	2-13
2.6	Light Activated SCR (LASCR)	2-14
2.6.1	Equivalent Circuit of LASCR	2-15
2.6.2	VI Characteristics of LASCR	2-15
2.6.3	Applications of LASCR	2-15
2.6.4	Triggering Devices	2-15
2.7	SUS : Silicon Unilateral Switch	2-16
2.8	SBS : Silicon Bilateral Switch	2-16
2.9	DIAC	2-17
2.9.1	Construction of Diac	2-17
2.9.2	I-V Characteristics of a Diac	2-17
2.9.3	DIAC Applications	2-18
2.10	Unijunction Transistor (UJT)	2-18
2.10.1	Construction	2-18
2.10.2	Equivalent Circuit of UJT	2-19
2.10.3	Intrinsic Standoff Ratio (η)	2-19
2.10.4	Operation of UJT	2-19
2.10.5	V-I Characteristics	2-19
2.11	Programmable Unijunction Transistor (PUT)	2-20
2.11.1	Difference between SUS and PUT	2-21
2.12	Types of MOSFETs	2-21
2.12.1	Depletion Type MOSFET	2-21
2.12.2	Enhancement MOSFET	2-23
2.13	Power MOSFET	2-26
2.14	Structure of a Power MOSFET	2-26
2.14.1	Simplified Structure of Power MOSFET	2-26
2.14.2	Principle of Operation	2-27
2.14.3	I-V Characteristics (Steady State Characteristics)	2-28
2.15	Merits, Demerits and Applications of Power MOSFET	2-29
2.15.1	Merits of a Power MOSFET	2-29
2.15.2	Applications of Power MOSFET	2-29
2.16	Insulated Gate Bipolar Transistor (IGBT)	2-29
2.16.1	Features of IGBT	2-30
2.17	Basic Structure of IGBT	2-30
2.18	I-V Characteristics (Steady State Characteristics)	2-31



2.19	Principle of Operation of IGBT	2-31
2.20	Merits, Demerits and Applications of IGBT	2-32
2.20.1	Merits of IGBT	2-32
2.20.2	Demerits of IGBT	2-32
2.20.3	Applications of IGBT	2-32
2.21	Comparisons.....	2-32
2.21.1	Comparison of SCR and TRIAC	2-32
2.21.2	Comparison of Diac and TRIAC	2-33
2.21.3	Comparison of Power Devices	2-33
2.21.4	Comparison of UJT and PUT.....	2-33
2.21.5	Comparison of SCR and DIAC	2-34
2.21.6	Comparison of GTO and IGBT	2-34
2.21.7	Comparison of UJT and DIAC	2-35
2.21.8	Comparison of SCR, MOSFET and IGBT	2-35
2.22	MSBTE Questions and Answers.....	2-37
2.23	I-Scheme Questions and Answers.....	2-41
	• Review Questions	2-36

Unit - II**Chapter 3 : Turn On Methods of SCR 3-1 to 3-18**

Syllabus : Concept of Turn ON mechanism of SCR : High voltage thermal triggering, Illumination triggering, dv/dt triggering, Gate triggering of SCR, Gate trigger circuits – Resistance triggering circuit, Resistance, Capacitance triggering circuit, SCR triggering methods : UJT, PUT - Relaxation oscillator circuit, Synchronized UJT triggering circuit, Pulse transformer used in triggering circuit and optocoupler (MCT2E).

3.1	Introduction to Turn On Methods	3-1
3.1.1	Firing Angle or Phase Angle (α) and Conduction Angle θ	3-1
3.2	Turn ON Mechanism.....	3-1
3.2.1	Thermal Triggering	3-2
3.2.2	Illumination Triggering	3-2
3.2.3	Forward Voltage Triggering	3-2
3.2.4	dv/dt Triggering.....	3-2
3.2.5	Gate Triggering.....	3-3
3.3	Types of Gate Triggering	3-3
3.3.1	DC Triggering	3-3
3.3.2	Pulsed Triggering of SCR.....	3-4
3.3.3	Requirements of Gate Drive for SCR	3-4
3.4	Gate Triggering Circuits.....	3-5
3.4.1	General Block Diagram of Thyristor Gate Trigger Circuit	3-5
3.4.2	Resistance Triggering Circuit.....	3-5

3.4.3	Half Wave RC (Capacitance) Firing Circuit.....	3-7
3.4.4	Full Wave RC (Capacitance) Firing Circuit.....	3-8
3.4.5	Basic UJT Relaxation Oscillator	3-8
3.4.6	SCR Triggering using UJT	3-9
3.4.7	Pulse Transformers.....	3-10
3.4.8	Synchronized UJT Triggering Circuit.....	3-11
3.4.9	Comparison of Triggering Circuits.....	3-12
3.4.10	SCR Triggering using PUT (PUT Relaxation Oscillator).....	3-13
3.5	Isolation Circuits using Opto Coupler	3-14
3.5.1	Opto Couplers / Isolators	3-14
3.5.2	LED-phototransistor Opto Coupler	3-14
3.5.3	Opto Coupler IC MCT2E	3-15
3.5.4	Opto Coupler Based Triggering.....	3-16
3.6	MSBTE Questions and Answers	3-17
3.7	I-Scheme Questions and Answers	3-18
	• Review Questions	3-16

Unit - II**Chapter 4 : Turn Off Methods and Protection Circuits of SCR 4-1 to 4-17**

Syllabus : Turn OFF methods - Class A, Series resonant commutation circuit, Class B-Shunt resonant commutation circuit, Class C-Complementary Symmetry commutation circuit. Protection circuits of SCR : Over voltage, over current, Snubber circuit and crowbar.

4.1	Introduction to Turn Off Methods of Thyristors	4-1
4.1.1	Turn Off Process of SCR.....	4-1
4.1.2	Turn Off Characteristics (Dynamic Turn off Characteristics) of SCR	4-1
4.1.3	Turn Off Time (t_q)	4-2
4.2	Commutation.....	4-3
4.3	Commutation Techniques	4-3
4.3.1	Natural Commutation	4-3
4.3.2	Forced Commutation.....	4-4
4.3.3	Conditions for Successful Commutation.....	4-4
4.4	Classification of Forced Commutation Methods	4-4
4.5	Self Commutation by Resonating the Load (Class A).....	4-4
4.5.1	Load in Parallel with Capacitor.....	4-4
4.6	Class B - Self Commutated by an LC Circuit.....	4-6
4.7	Complementary Voltage Commutation (Class C Commutation)	4-8
4.7.1	Operation of the Circuit	4-8



4.8	Class F - Commutation (Line Commutation).....	4-10	5.4	Single Phase Full Wave Controlled Rectifier.....	5-8
4.9	Comparisons.....	4-10	5.4.1	Center Tapped Full Wave Controlled Rectifier (Mid Point M_2 Configuration).....	5-9
4.9.1	Comparison between Natural and Forced Commutation.....	4-10	5.4.2	Operation with Resistive Load.....	5-9
4.9.2	Comparison between Voltage Commutation and Current Commutation.....	4-10	5.4.3	Operation with Highly Inductive Load... ..	5-11
4.10	Overcurrent Protection using Fuses	4-11	5.5	Two Quadrant Operation of Full Wave Controlled Rectifier (Rectifier and Inverter Modes).....	5-14
4.11	Overvoltage Protection Circuits	4-12	5.6	Full Wave Controlled Rectifier With Freewheeling Diode.....	5-16
4.11.1	Crowbar Circuit (Overcurrent / Overvoltage Protection).....	4-12	5.6.1	Advantages of Full Wave Controlled Rectifier.....	5-18
4.12	dv/dt and di/dt Protection Circuits for SCRs.....	4-12	5.6.2	Applications of Controlled Rectifiers.....	5-18
4.12.1	di/dt Protection (Turn on Snubber)	4-12	5.6.3	Comparison of Controlled H.W.R. and Controlled F.W.R.....	5-18
4.12.2	dv/dt Protection (Turn off Snubber)	4-13	5.7	Polyphase Rectifiers.....	5-19
4.12.3	Design of a Snubber Circuit	4-14	5.7.1	Need of Polyphase Rectifiers	5-19
4.13	MSBTE Questions and Answers.....	4-16	5.7.2	Advantages of Polyphase Rectifiers.....	5-19
4.14	I-Scheme Questions and Answers.....	4-17	5.7.3	3-Phase Transformers	5-19
	• Review Questions	4-15	5.7.4	Delta-Star Connection.....	5-19

Unit - III

Chapter 5 : Phase Controlled Rectifiers 5-1 to 5-29

Syllabus : Phase control parameters : Firing angle (α) and conduction angle (ϕ), Single phase half wave controlled rectifier : Circuit diagram, Working and waveforms with R and RL load, Effect of freewheeling diode with RL load, Single phase center tapped full wave controlled rectifier : Circuit diagram, Working and waveforms with R and RL load, Effect of freewheeling diode with RL load, Basic three phase half wave controlled rectifier.

5.1	Introduction to Phase Controlled Rectifiers.....	5-1	5.7.6	How to Draw the Phase and Line Voltages ?	5-21
5.1.1	Principle of Phase Angle Control	5-1	5.7.7	How to Draw the Phase Voltages ?.....	5-21
5.2	Classification of Controlled Rectifiers	5-2	5.7.8	How to Draw the Line Voltages ?.....	5-21
5.3	Single Phase Half Wave Controlled Rectifier (HWCR).....	5-2	5.8	Three Phase Half Wave Controlled Rectifier (HWCR) (Three Pulse Converter)	5-22
5.3.1	Circuit Diagram and Operation with Resistive Load.....	5-3	5.8.1	3-Phase HWCR with RL (Inductive) Load	5-22
5.3.2	Waveforms with Resistive Load.....	5-3	5.8.2	Operation of HWCR with Purely Resistive Load.....	5-24
5.3.3	Operation of HWCR with Inductive (RL) Load	5-4	5.8.3	3-Pulse Converters	5-25
5.3.4	Use of Freewheeling Diode in Controlled Rectifiers	5-6	5.8.4	Applications of Polyphase Rectifiers	5-25
5.3.5	Effect of Freewheeling Diode (With RL Load).....	5-6	5.8.5	Comparison of Controlled and Uncontrolled Rectifiers	5-25
5.3.6	Average Output Voltage of HWCR with RL Load.....	5-8	5.9	MSBTE Questions and Answers	5-26
5.3.7	Rectifier Operation (Single Quadrant Operation).....	5-8	5.10	I-Scheme Solved Examples	5-29
5.3.8	Drawbacks of HWCR.....	5-8	5.11	I-Scheme Questions and Answers	5-29
				• Review Questions	5-26

Unit - IV

Chapter 6 : Choppers and Inverters 6-1 to 6-20

Syllabus : Converters and its types, Block diagram and working of step up and step down choppers using power MOSFET, Inverters : Circuit diagram, Working of series, Parallel inverters.

6.1	Converters and its Types	6-1
6.1.1	Classification of Converters.....	6-1
6.1.2	Rectifiers (Uncontrolled).....	6-1



6.1.3	AC to DC Converter (Controlled Rectifiers).....	6-1
6.1.4	DC to AC Converter (Inverter).....	6-2
6.1.5	DC to DC Converter (Chopper).....	6-2
6.1.6	AC Regulators (AC Controller).....	6-3
6.1.7	Static Switches.....	6-3
6.2	Chopper : Basic Concept.....	6-3
6.3	Classification of Choppers.....	6-4
6.4	A Step Down Chopper using MOSFET.....	6-5
6.5	Step Up Chopper.....	6-6
6.5.1	Expression for the Output Voltage.....	6-6
6.6	Applications of a Chopper.....	6-8
6.6.1	Comparison of Step Up and Step Down Choppers.....	6-8
6.7	Introduction to Inverters.....	6-8
6.8	Classification of Inverters.....	6-9
6.8.1	Classification Based on the Nature of Source.....	6-9
6.8.2	Classification Based on the Configuration of the Inverter.....	6-9
6.8.3	Classification Based on the Nature of Output Waveform.....	6-9
6.8.4	Classification Based on Type of Commutation Circuit.....	6-10
6.8.5	Classification Based on the Power Semiconductor Device Used.....	6-10
6.9	Basic Series Inverter (Self Commutated Inverter).....	6-10
6.9.1	Disadvantages.....	6-11
6.9.2	Improved Series Inverter [Type 1].....	6-11
6.9.3	Improved Series Inverter [Type 2].....	6-12
6.9.4	Applications of Series Inverter.....	6-13
6.9.5	Advantages of Series Inverter.....	6-13
6.10	Parallel Inverter (with Purely Resistive Load).....	6-13
6.11	Parallel Inverter (with Inductive Load).....	6-14
6.11.1	Advantages of Parallel Inverter.....	6-16
6.11.2	Disadvantages.....	6-17
6.11.3	Comparison of Series and Parallel Inverters.....	6-17
6.12	Inverter Specifications.....	6-17
6.13	Applications of Inverters.....	6-17

6.14	MSBTE Questions and Answers.....	6-18
6.15	I-Scheme Questions and Answers.....	6-20
	• Review Questions	6-17

Unit - V

Chapter 7 : Industrial Control Circuits 7-1 to 7-17

Syllabus : Light dimmer circuit using DIAC - TRIAC, Battery charger using SCR, Emergency lighting system, Temperature controller using SCR, Block diagram and concept of UPS (On line and off line), Block diagram and concept of SMPS.

7.1	Introduction.....	7-1
7.2	TRIAC Control using Diac (AC Phase Control).....	7-1
7.2.1	Light Dimmer using TRIAC.....	7-2
7.2.2	Fan Regulator using TRIAC.....	7-3
7.3	Simple Battery Charger.....	7-3
7.3.1	Battery Charging Regulator.....	7-4
7.4	Basic Emergency Lighting System.....	7-5
7.5	Temperature Controller Using SCR.....	7-5
7.6	Switch Mode Power Supply (SMPS) Block Diagram.....	7-6
7.6.1	Complete Switched Mode Regulator.....	7-7
7.6.2	Classification of SMPS.....	7-8
7.7	Advantages and Disadvantages of SMPS.....	7-8
7.8	Applications of SMPS.....	7-8
7.9	UPS.....	7-8
7.9.1	Need of UPS.....	7-8
7.9.2	Types of UPS.....	7-9
7.10	On Line UPS (Inverter Preferred) or (Continuous).....	7-9
7.11	Off Line UPS (Line Preferred) or Transfer UPS System.....	7-10
7.12	Applications of UPS.....	7-11
7.13	Comparison.....	7-12
7.13.1	Comparison of UPS Systems.....	7-12
7.13.2	Comparison of Linear and Switching Mode Regulators.....	7-12
7.14	MSBTE Questions and Answers.....	7-13
7.15	I-Scheme Questions and Answers.....	7-15
	Review Questions	7-12

