

**Article A : Semiconductor Theory A-1 to A-5**

Contents : Review of semiconductor theory (No questions to be set in theory paper), Semiconductor (based on band theory), Intrinsic semiconductors : Extrinsic semiconductors, Doping, Dopant, Trivalent and Pentavalent impurities, P-type and N-type semiconductors.

A.1	Introduction	A-1
A.2	Semiconductors	A-1
A.3	Intrinsic and Extrinsic Semiconductor	A-1
A.4	Crystalline Structure of Intrinsic Semiconductors	A-2
A.5	Conduction in Intrinsic Semiconductors	A-2
A.5.1	Effect of Increased Temperature (Thermal Generation of Carriers)	A-2
A.5.2	Electron and Hole Current	A-3
A.6	Extrinsic Semiconductors	A-3
A.6.1	Doping and Dopant	A-3
A.6.2	n-type Semiconductors	A-4
A.6.3	p-type Semiconductors	A-4
•	Review Questions	A-5

Unit - I**Chapter 1 : Semiconductor Diodes 1-1 to 1-29**

Syllabus : Construction, Symbol, Working principle, Specifications, Applications, Forward and reverse biasing and V-I characteristics of following semiconductor diodes PN junction diode, Zener diode. Special diodes : LED, Photodiode, LASER diode and Power diode.

1.1	Introduction to p-n Junction	1-1
1.1.1	Junction Theory	1-1
1.1.2	Formation of the Depletion Region	1-1
1.1.3	Barrier Potential or Junction Potential (V_j)	1-2
1.2	p-n Junction Diode	1-3
1.3	Biasing of a P-N Junction Diode	1-3

1.3.1	Forward Biased of a P-N Junction Diode	1-4
1.3.2	Voltage Drop Across the Forward Biased Diode (V_F)	1-5
1.3.3	Reverse Biased PN Junction Diode	1-5
1.3.4	Breakdown in the Reverse Biased Diode (Breakdown Voltage)	1-6
1.4	The Volt-ampere (V-I) Characteristics of a Diode	1-7
1.4.1	Forward Characteristics of p-n Junction Diode	1-7
1.4.2	Reverse Characteristics of a Diode (Breakdown Voltage)	1-8
1.4.3	Complete V-I Characteristics of a Diode	1-8
1.4.4	Complete V-I Characteristics of Silicon and Germanium Diodes	1-9
1.4.5	Comparison of Silicon and Germanium Diodes	1-9
1.4.6	Mathematical Expression for the Diode Current (V-I Characteristics)	1-9
1.4.7	Effect of Temperature on the V-I Characteristics	1-10
1.4.8	Circuit Diagram for Characteristics	1-10
1.5	Diode Specifications	1-11
1.6	Applications of p-n Junction Diode	1-11
1.7	Zener Diode	1-12
1.7.1	Operating Principle	1-12
1.7.2	Circuit Symbol and Biasing of a Zener Diode	1-12
1.7.3	V-I Characteristics of a Zener Diode	1-12
1.8	Breakdown Mechanisms in Zener Diode	1-13
1.8.1	Zener Breakdown	1-13
1.8.2	Avalanche Breakdown in Zener Diodes	1-14



1.8.3	Comparison of Zener Diode and p-n Junction Diode	1-14
1.9	Zener Diode Specifications	1-15
1.10	Applications of Zener Diode	1-16
1.11	Special Purpose Diodes	1-16
1.12	Light Emitting Diodes (LED)	1-16
1.12.1	Construction of LED	1-16
1.12.2	Principle of LED Operation	1-17
1.12.3	Colour of the Emitted Light	1-17
1.12.4	Advantages of LEDs	1-18
1.12.5	Disadvantages of LEDs	1-18
1.12.6	Applications of LEDs	1-18
1.12.7	Comparison of PN Junction Diode and LED	1-18
1.13	Photodiode	1-18
1.13.1	Construction and Operation	1-19
1.13.2	Photodiode Characteristics	1-19
1.13.3	Applications of Photodiode	1-20
1.13.4	Comparison of LED and Photodiode	1-20
1.14	Laser Diode	1-20
1.14.1	Absorption	1-20
1.14.2	Spontaneous Emission	1-20
1.14.3	Stimulated Emission	1-21
1.14.4	Construction and Operation of a Laser Diode	1-21
1.14.5	Characteristics of LASER Diode	1-22
1.14.6	Applications	1-22
1.15	Power Diodes	1-22
1.15.1	Types of Power Diodes	1-22
1.15.2	Operating Principle of Power Diodes	1-22
1.15.3	V-I Characteristics of Power Diode	1-22
1.16	MSBTE Questions and Answers	1-23

1.17	I-Scheme Questions and Answers	1-28
•	Review Questions	1-23
•	1 and 2 Marks Questions with Answers	1-24

Unit - II**Chapter 2 : Rectifiers and Filters** 2-1 to 2-30

Syllabus : Types of rectifiers : Half wave, Full wave rectifier (bridge and center tapped) : Circuit operation, Input/output waveforms for voltage and current, Parameters of rectifier : Average dc value of current and voltage, Ripple factor, Ripple frequency, PIV of diode, TUF and efficiency of rectifier. Types of filters : Shunt capacitor, Series inductor, LC and π filter.

2.1	A DC Power Supply	2-1
2.1.1	Rectification	2-1
2.1.2	Rectifiers	2-1
2.1.3	Polarities of Transformer Voltages	2-2
2.2	Types of Rectifiers	2-2
2.3	Half Wave Rectifier (HWR)	2-2
2.3.1	Operation of the HWR	2-3
2.3.2	Analysis of Half Wave Rectifier	2-3
2.3.3	DC or Average Load Current (I_{Ldc})	2-3
2.3.4	DC or Average Load Voltage (V_{Ldc})	2-4
2.3.5	AC or RMS Load Current ($I_{L rms}$)	2-4
2.3.6	AC or RMS Value of Load Voltage ($V_{L rms}$)	2-4
2.3.7	Ripple Factor (RF)	2-4
2.3.8	DC Output Power (P_{Ldc})	2-5
2.3.9	AC Input Power	2-5
2.3.10	Rectification Efficiency or Power Conversion Efficiency	2-5
2.3.11	Transformer Utilization Factor (TUF)	2-5
2.3.12	Peak Inverse Voltage (PIV)	2-6
2.3.13	Ripple Frequency	2-6
2.3.14	Disadvantages of Half Wave Rectifier ...	2-6



2.3.15 Advantages of HWR	2-6	2.9.1 Operation of FWR with a Shunt Capacitor Filter	2-18
2.3.16 Applications of HWR	2-6	2.9.2 Ripple Factor and DC Output Voltage ..	2-19
2.4 Examples on Half Wave Rectifier	2-6	2.9.3 Dependence of Ripple Factor on the Value of Load	2-19
2.5 Full Wave Rectifier with Center Tapped Transformer	2-7	2.9.4 Advantages of Capacitor Input Filter	2-19
2.5.1 Operation of FWR	2-8	2.9.5 Disadvantages (Limitations)	2-19
2.5.2 Average Load Current (I_{Ldc})	2-9	2.9.6 HWR with Shunt Capacitor Filter	2-19
2.5.3 Average Load Voltage (V_{Ldc})	2-9	2.9.7 Bridge Rectifier with Shunt Capacitor Filter	2-20
2.5.4 RMS Load Current (I_{Lrms})	2-10	2.10 Series Inductor Filter (Choke Input Filter) or L Filter	2-20
2.5.5 RMS Load Voltage (V_{Lrms})	2-10	2.10.1 Operation of the Circuit and Waveforms	2-21
2.5.6 Ripple Factor (RF)	2-10	2.10.2 Expression for the Ripple Factor	2-21
2.5.7 DC Output Power (P_{Ldc})	2-10	2.10.3 Dependence of Ripple Factor on Load	2-21
2.5.8 AC Input Power (P_{ac})	2-10	2.10.4 Advantages of Series Inductor Filter	2-22
2.5.9 Rectifier Efficiency	2-10	2.10.5 Disadvantages	2-22
2.5.10 Peak Inverse Voltage (PIV)	2-11	2.10.6 Comparison of Shunt Capacitor and Series Inductor Filters	2-22
2.5.11 Ripple Frequency	2-11	2.10.7 HWR with Series Inductor Filter	2-22
2.5.12 Advantages of Full Wave Rectifier	2-11	2.10.8 Bridge Rectifier with Series Inductor Filter	2-22
2.5.13 Disadvantages of Full Wave Rectifier ..	2-11	2.11 LC Filter	2-22
2.5.14 Applications of FWR	2-11	2.11.1 Role of the Bleeder Resistance (R_B)	2-23
2.5.15 Solved Example on FWR	2-11	2.11.2 Expression for the Ripple Factor	2-23
2.6 Full Wave Bridge Rectifier	2-12	2.11.3 Dependence of Ripple Factor on the Load	2-23
2.6.1 Operation of the Bridge Rectifier	2-13	2.11.4 Advantages of LC Filter	2-23
2.6.2 Performance Parameter of a Bridge Rectifier	2-13	2.11.5 Disadvantages of LC Filter	2-23
2.6.3 Advantages of Bridge Rectifier	2-14		
2.6.4 Disadvantages of Bridge Rectifier	2-15		
2.6.5 Applications of Bridge Rectifier	2-15		
2.6.6 Comparison of Rectifying Circuits	2-15		
2.7 Need of Filter Circuits	2-16		
2.8 Types of Filters (Classification of Filters)	2-16		
2.9 Capacitor Input Filter (Shunt Capacitor Filter) or C Filter	2-17		



2.11.6	LC Filter with Half Wave Rectifier	2-23
2.11.7	LC Filter with Bridge Rectifier	2-23
2.11.8	π Type Filter (CLC Filter)	2-23
2.11.9	Comparison of C, L, LC and π Filters ...	2-25
2.12	MSBTE Questions and Answers	2-26
2.13	I-Scheme Solved Examples.....	2-28
2.14	I-Scheme Questions and Answers	2-29
•	Review Questions	2-25
•	1 and 2 Marks Questions with Answers....	2-27

Unit - III**Chapter 3 : Bipolar Junction Transistor 3-1 to 3-20**

Syllabus : Different types of transistors PNP, NPN, Transistor configurations CB, CE, CC, Transistor as a switch.

3.1	Introduction	3-1
3.1.1	Advantages of a Transistor	3-1
3.1.2	Transistor Definition	3-1
3.1.3	Why is it called a “Bipolar” Transistor ?...3-1	
3.1.4	Types and Symbols of Transistors	3-1
3.2	Construction of a BJT	3-2
3.2.1	An Unbiased Transistor	3-2
3.3	Transistor Biasing in the Active Region	3-3
3.4	Operation of NPN Transistor	3-3
3.4.1	Operation of PNP Transistor	3-4
3.5	Transistor Currents	3-5
3.6	Transistor Configurations	3-5
3.7	Common Base (CB) Configuration	3-5
3.7.1	Current Relations in CB Configuration ...3-6	
3.7.2	Features of CB Configuration	3-7
3.8	Common Emitter (CE) Configuration	3-7
3.8.1	Current Relations in CE Configuration ...3-7	

3.8.2	Reverse Leakage Current in CE Configuration (I_{CEO})	3-8
-------	---	-----

3.8.3	Current Gain (β)	3-8
3.8.4	Relation between α_{dc} and β_{dc}	3-8
3.8.5	Input Characteristics	3-9
3.8.6	Output Characteristics	3-9
3.8.7	Features of CE Configuration	3-10

3.9	Common Collector (CC) Configuration	3-11
-----	---	------

3.9.1	Practical Way to Draw Common Collector Configuration	3-12
3.9.2	Features of CC Configuration	3-13

3.10	Comparison of Configurations	3-13
------	------------------------------------	------

3.11	Specifications of a Transistor	3-14
3.12	Transistor Applications	3-14

3.13	Transistor as a Switch	3-14
------	------------------------------	------

3.13.1	Applications of Transistor as a Switch .	3-15
--------	--	------

3.14	MSBTE Questions and Answers	3-15
------	-----------------------------------	------

3.15	I-Scheme Solved Examples	3-18
------	--------------------------------	------

3.16	I-Scheme Questions and Answers	3-19
------	--------------------------------------	------

•	Review Questions	3-15
---	-------------------------------	-------------

•	1 and 2 Marks Questions with Answers....	3-17
---	---	-------------

Unit - IV**Chapter 4 : Regulators and Power Supply 4-1 to 4-20**

Syllabus : Load and line regulation, Basic zener diode voltage regulator, Regulator IC's : IC's 78XX, 79XX and IC 723 as fixed, Variable and dual regulated dc power supply, Construction and operation of DC regulated power supply.

4.1	Introduction to Voltage Regulators	4-1
4.1.1	Unregulated Power Supply	4-1
4.1.2	Need of Regulator	4-1
4.1.3	Voltage Regulation (or Voltage Regulation Factor)	4-1



4.1.4 Factors Affecting the Output Voltage4-1	4.6.6 The Negative -12 V Power Supply using IC 7912 (Applications of 79XX)4-11
4.1.5 Load Regulation4-2	4.7 Dual Polarity Power Supply4-11
4.1.6 Line Regulation or Source Regulation4-2	4.7.1 Applications of 78XX Series4-11
4.2 Types of Voltage Regulators4-3	4.8 IC 723 - The General Purpose Regulator4-12
4.3 Zener Diode as a Voltage Regulator4-3	4.8.1 Pin Diagram of IC 7234-12
4.3.1 Regulating Action with a Varying Input Voltage (Constant I_L)4-4	4.8.2 Functional Block Diagram4-12
4.3.2 Regulating Action with a Varying Load (V_{in} Constant)4-4	4.9 Applications of IC 7234-13
4.3.3 Limitations of Zener Regulators4-5	4.9.1 Basic Low Fixed Voltage Regulator4-14
4.3.4 Merits of Zener Regulator4-5	4.9.2 Basic Fixed High Voltage Regulator ...4-14
4.3.5 Applications of Zener Regulator4-5	4.9.3 Variable Output Voltage Power Supply using IC 7234-15
4.3.6 A Typical Regulated Power Supply using a Zener Diode4-7	4.10 MSBTE Questions and Answers4-16
4.4 Need of Regulated Power Supply4-7	4.11 I-Scheme Questions and Answers4-19
4.4.1 Basic Block Diagram of Regulated Power Supply4-7	<ul style="list-style-type: none"> • Review Questions4-16 • 1 and 2 Marks Questions with Answers.....4-17
4.4.2 Advantages of Regulated Power Supplies4-8	Unit - V
4.4.3 Applications of Regulated Power Supplies4-8	Chapter 5 : Oscillators
4.4.4 Comparison of Voltage Regulators4-8	5-1 to 5-22
4.5 Three Terminal Regulator ICs4-9	Syllabus : Types of feedback : Positive feedback, Negative feedback, Barkhausen's criterion, Oscillators : Circuit diagram and working of LC, RC and crystal oscillators.
4.5.1 Advantages of IC Regulators4-9	
4.6 Three Terminal Fixed Voltage Regulators4-9	
4.6.1 78XX Series4-9	5.1 Concept of Feedback5-1
4.6.2 79XX Series4-9	5.1.1 Types of Feedback5-1
4.6.3 Standard Connections for Positive Fixed Voltage Regulator (78XX)4-10	5.1.2 Comparison of Positive and Negative Feedback5-1
4.6.4 A Positive 12V Power Supply using IC 7812 (Application of 78XX)4-10	5.2 Definition of Oscillators5-1
4.6.5 Negative Voltage Regulators (79XX Series)4-10	5.2.1 Block Diagram of an Oscillator5-2
	5.2.2 Positive Feedback5-2
	5.2.3 Expression for the Gain with Positive Feedback (A_f)5-3
	5.3 Barkhausen Criteria5-3
	5.4 Classification of Oscillators5-4



5.4.1 RC Oscillators	5-4	5.9.2 Application of Colpitt's Oscillator	5-12
5.4.2 LC Oscillators	5-4	5.10 Applications of LC Oscillators	5-14
5.5 RC Phase Shift Oscillator	5-4	5.11 Crystal Oscillators	5-14
5.5.1 Basic R-C Phase Shifting Network	5-4	5.11.1 Equivalent Circuit of a Crystal	5-14
5.5.2 RC Network for the Phase Shift Oscillator	5-5	5.11.2 Types of Crystal Oscillators	5-15
5.5.3 R-C Phase Shift Oscillator using Transistor	5-5	5.11.3 Pierce Crystal Oscillator	5-15
5.5.4 Frequency of Oscillations	5-6	5.11.4 Miller Crystal Oscillator	5-15
5.5.5 Variation in Frequency	5-6	5.11.5 Applications of Crystal Oscillators.....	5-16
5.5.6 Frequency Range	5-6	5.12 Comparisons	5-16
5.5.7 Advantages of Phase Shift Oscillator	5-6	5.12.1 Comparisons of LC and RC Oscillators	5-16
5.5.8 Disadvantages of Phase Shift Oscillator	5-6	5.12.2 Comparison of LC Oscillators	5-16
5.5.9 Applications of RC Oscillators	5-7	5.12.3 Comparison of RC, LC and Crystal Oscillators	5-16
5.6 Wien Bridge Oscillator	5-7	5.13 General Applications of Oscillator	5-16
5.6.1 The Wien Bridge Circuit	5-7	5.14 MSBTE Questions and Answers	5-17
5.6.2 Feedback Factor (β) and Gain (A)	5-7	5.15 I-Scheme Solved Examples	5-21
5.6.3 Wien Bridge Oscillator using Transistors	5-8	5.16 I-Scheme Questions and Answers	5-21
5.6.4 Advantages of Wien Bridge Oscillator	5-8	• Review Questions	5-16
5.6.5 Disadvantages	5-9	• 1 and 2 Marks Questions with Answers	5-19
5.6.6 Comparison of RC Oscillators	5-9	Unit - VI	
5.6.7 Applications of RC Oscillators	5-9	Chapter 6 : Digital Electronics	
5.7 LC Oscillators	5-9	6-1 to 6-29	
5.8 Hartley Oscillator	5-10	<p>Syllabus : Number systems : Binary, Octal, Decimal and Hexadecimal number system. Boolean algebra : De-Morgan's theorems, Logic gates : Logic symbol, Logical expression and truth table of AND, OR, NOT, EX-OR and EX-NOR gates. Universal gates : NAND and NOR. Flipflops : Symbol, Truth table and working of SR, JK, MSJK, T and D flipflops.</p>	
5.8.1 Applications	5-10	<p>6.1 Number Systems</p>	
5.9 Colpitt's Oscillator	5-11	<p> 6.1.1 Important Definitions</p>	
5.9.1 Frequency Stability	5-12	<p> 6.1.2 Various Numbering Systems</p>	



6.2	The Decimal Number System	6-1	6.9.1	Other Systems to Hex	6-8
6.2.1	Characteristics of a Decimal System	6-1	6.9.2	Hex to Other Systems	6-8
6.3	The Binary Number System	6-2	6.10	Boolean (Binary) Algebra	6-10
6.3.1	Binary Numbers from $(0)_{10}$ to $(15)_{10}$	6-2	6.11	Boolean Laws	6-10
6.3.2	Binary Number Formats	6-2	6.11.1	Commutative Law	6-10
6.3.3	Disadvantages of the Binary System	6-2	6.11.2	Associative Law	6-10
6.4	Octal Number System	6-2	6.11.3	Distributive Law	6-10
6.4.1	Applications of Octal System	6-3	6.11.4	AND Laws	6-10
6.5	Hexadecimal Number System	6-3	6.11.5	OR Laws	6-10
6.5.1	Relation between Binary, Decimal, Octal and Hexadecimal Numbers	6-4	6.11.6	INVERSION Law	6-11
6.6	Conversions Related to Decimal System	6-4	6.11.7	De-Morgan's Theorems	6-11
6.6.1	Conversion from any Radix r to Decimal	6-4	6.12	Logic Gates	6-12
6.6.2	Successive Division for Integer Part Conversion	6-5	6.12.1	Classification of Logic Gates	6-12
6.6.3	Successive Multiplication for Fractional Part Conversion	6-5	6.13	NOT Gate or Inverter	6-12
6.6.4	Conversion of Mixed Decimal Number to any Other Radix	6-6	6.14	AND Gate	6-12
6.7	Conversion from Binary to Other Systems	6-7	6.15	The OR Gate	6-13
6.7.1	Conversion from Binary to Decimal	6-7	6.16	The NAND Gate	6-13
6.7.2	Binary to Hex Conversion	6-7	6.17	The NOR Gate	6-14
6.7.3	Conversion from Other Systems to Binary System	6-7	6.18	Special Type of Gates or Derived Gates	6-14
6.8	Conversion from Octal to Other Systems	6-7	6.18.1	The EX-OR Gate	6-14
6.8.1	Octal to Hex Conversion	6-8	6.18.2	The EX-NOR Gate	6-15
6.8.2	Conversion from Other Systems to Octal	6-8	6.18.3	Examples of IC Gates	6-15
6.9	Conversions Related to Hexadecimal System	6-8	6.19	NAND and NOR as Universal Gates	6-16
			6.19.1	NAND Gate as Universal Gate	6-16
			6.19.2	NOR Gate as a Universal Gate	6-17
			6.20	Applications of Digital Electronics	6-19
			6.21	Flip-Flops	6-19



6.21.1 Basic SR Flip-Flop or SR Latch (Using NAND Gates)	6-19	6.22 MSBTE Questions and Answers	6-23
6.21.2 D-flipflop (Latch or Delay Element)	6-21	6.23 I-Scheme Solved Examples	6-26
6.21.3 JK Flip Flop	6-21	6.24 I-Scheme Questions and Answers	6-27
6.21.4 Master Slave JK Flip Flop	6-22	• Review Questions	6-23
6.21.5 Toggle Flip-Flop (T Flip-Flop)	6-22	• 1 and 2 Marks Questions with Answers.....	6-24

