



2.3.3	Reverse Bias	2-6	2.9.4	Infra Red Light Emitting Diode (IR-LED)	2-20
2.3.4	Breakdown in the Reverse Biased Diode (Breakdown Voltage)	2-8	2.9.5	Comparison of Conventional Diode and LED	2-21
2.4	The Volt-ampere (V-I) Characteristics of a Diode ..	2-9	2.10	MSBTE Questions and Answers	2-21
2.4.1	Forward Characteristics of p-n Junction Diode	2-9	2.11	I-Scheme Questions and Answers	2-26
2.4.2	Reverse Characteristics of a Diode (Breakdown Voltage)	2-10	• Review Questions	2-21	
2.4.3	Complete V-I Characteristics of a Diode	2-11	Unit – II		
2.4.4	Complete V-I Characteristics of Silicon and Germanium Diodes	2-11	Chapter 3 : Rectifiers, Filters and Voltage Regulators		
2.4.5	Comparison of Silicon and Germanium Diodes	2-12	3-1 to 3-44		
2.4.6	Mathematical Expression for the Diode Current (V-I Characteristics)	2-12	Syllabus : Rectifiers Half wave, Full wave and Bridge rectifiers, Working principle, Circuit diagram, Performance parameters PIV, Ripple factor, Efficiency, Need of filters, Circuit diagram and working of L, C and π filters. Zener diode as voltage regulator, Working principle and block diagram of a regulated power supply.		
2.4.7	Effect of Temperature on the V-I Characteristics	2-12	3.1	Basic Block Diagram of Regulated Power Supply ..	3-2
2.4.8	Circuit Diagram for Characteristics	2-12	3.1.1	Need of Regulated Power Supply	3-3
2.4.9	Ideal Characteristics	2-13	3.1.2	Advantages of Regulated Power Supplies	3-3
2.4.10	Comparison of Ideal Diode and Real Diode	2-14	3.1.3	Applications of Regulated Power Supplies	3-3
2.5	Applications of p-n Junction Diode	2-14	3.2	Rectifiers	3-3
2.6	Zener Diode	2-14	3.2.1	Rectification	3-3
2.6.1	Operating Principle	2-14	3.2.2	Rectifiers	3-3
2.6.2	Circuit Symbol and Biasing of a Zener Diode	2-14	3.2.3	Polarities of Transformer Voltages	3-4
2.6.3	V-I Characteristics of a Zener Diode	2-15	3.2.4	Types of Rectifiers	3-4
2.6.4	Circuit Diagram for the V-I Characteristics	2-16	3.3	Half Wave Rectifier (HWR)	3-4
2.7	Breakdown Mechanisms in Zener Diode	2-17	3.3.1	Operation of the HWR	3-5
2.7.1	Zener Breakdown	2-17	3.3.2	Analysis of Half Wave Rectifier	3-6
2.7.2	Avalanche Breakdown in Zener Diodes ..	2-17	3.3.3	DC or Average Load Current (I_{Ldc})	3-6
2.7.3	Comparison of Zener Diode and p-n Junction Diode	2-18	3.3.4	DC or Average Load Voltage (V_{Ldc})	3-6
2.8	Applications of Zener Diode	2-18	3.3.5	AC or RMS Load Current ($I_{L rms}$)	3-6
2.9	Light Emitting Diodes (LED)	2-18	3.3.6	AC or RMS Value of Load Voltage ($V_{L rms}$)	3-6
2.9.1	Construction of LED	2-19	3.3.7	Ripple Factor (RF)	3-7
2.9.2	Principle of LED Operation	2-19	3.3.8	DC Output Power (P_{Ldc})	3-7
2.9.3	Applications of LEDs	2-20	3.3.9	AC Input Power	3-7



3.3.10	Rectification Efficiency or Power	3.9.1	Operation of FWR with a Shunt Capacitor Filter
	Conversion Efficiency		3-22
	3-7	3.9.2	Ripple Factor and DC Output Voltage
3.3.11	Transformer Utilization Factor (TUF)		3-23
	3-8	3.9.3	Dependence of Ripple Factor on the Value of Load
3.3.12	Peak Inverse Voltage (PIV)		3-24
	3-8	3.9.4	Advantages of Capacitor Input Filter
3.3.13	Ripple Frequency		3-24
	3-9	3.9.5	Disadvantages (Limitations)
3.3.14	Disadvantages of Half Wave Rectifier		3-24
	3-9	3.9.6	HWR with Shunt Capacitor Filter
3.3.15	Advantages of HWR		3-24
	3-9	3.9.7	Bridge Rectifier with Shunt Capacitor Filter
3.3.16	Applications of HWR		3-24
	3-9	3.10	Series Inductor Filter (Choke Input Filter) or L Filter.
3.4	Examples on Half Wave Rectifier		3-25
	3-9	3.10.1	Operation of the Circuit and Waveforms
3.5	Full Wave Rectifier with Center Tapped Transformer		3-25
	3-10	3.10.2	Expression for the Ripple Factor
3.5.1	Operation of FWR		3-25
	3-11	3.10.3	Dependence of Ripple Factor on Load ...
3.5.2	Average Load Current (I_{Ldc})		3-26
	3-12	3.10.4	Advantages of Series Inductor Filter
3.5.3	Average Load Voltage (V_{Ldc})		3-26
	3-13	3.10.5	Disadvantages
3.5.4	RMS Load Current (I_{Lrms})		3-26
	3-13	3.10.6	Comparison of Shunt Capacitor and Series Inductor Filters
3.5.5	RMS Load Voltage (V_{Lrms})		3-26
	3-13	3.10.7	HWR with Series Inductor Filter
3.5.6	Ripple Factor (RF)		3-27
	3-13	3.10.8	Bridge Rectifier with Series Inductor Filter
3.5.7	DC Output Power (P_{Ldc})		3-27
	3-14	3.11	LC Filter
3.5.8	AC Input Power (P_{ac})		3-27
	3-14	3.11.1	Role of the Bleeder Resistance (R_B)
3.5.9	Rectifier Efficiency		3-27
	3-14	3.11.2	Expression for the Ripple Factor
3.5.10	Peak Inverse Voltage (PIV)		3-28
	3-14	3.11.3	Dependence of Ripple Factor on the Load
3.5.11	Ripple Frequency		3-28
	3-14	3.11.4	Advantages of LC Filter
3.5.12	Advantages of Full Wave Rectifier		3-28
	3-15	3.11.5	Disadvantages of LC Filter
3.5.13	Disadvantages of Full Wave Rectifier		3-28
	3-15	3.11.6	LC Filter with Half Wave Rectifier
3.5.14	Applications of FWR		3-28
	3-15	3.11.7	LC Filter with Bridge Rectifier
3.5.15	Solved Example on FWR		3-28
	3-15	3.11.8	π Type Filter (CLC Filter)
3.6	Full Wave Bridge Rectifier		3-28
	3-15	3.11.9	Comparison of C, L, LC and π Filters
3.6.1	Operation of the Bridge Rectifier		3-30
	3-16	3.12	Introduction to Voltage Regulators
3.6.2	Performance Parameter of a Bridge Rectifier		3-31
	3-17	3.12.1	Unregulated Power Supply
3.6.3	Advantages of Bridge Rectifier		3-31
	3-18	3.12.2	Need of Regulator
3.6.4	Disadvantages of Bridge Rectifier		3-31
	3-18	3.12.3	Voltage Regulation (or Voltage Regulation Factor)
3.6.5	Applications of Bridge Rectifier		3-31
	3-18	3.12.4	Factors Affecting the Output Voltage
3.6.6	Comparison of Rectifying Circuits		3-31
	3-19		
3.7	Need of Filter Circuits		
	3-20		
3.8	Types of Filters (Classification of Filters)		
	3-21		
3.9	Capacitor Input Filter (Shunt Capacitor Filter) or C Filter		
	3-21		

3.12.5	Load Regulation	3-32	4.8.1	Current Relations in CE Configuration	4-10
3.12.6	Line Regulation or Source Regulation	3-32	4.8.2	Reverse Leakage Current in CE Configuration (I_{CEO})	4-10
3.13	Zener Diode as a Voltage Regulator	3-33	4.8.3	Current Gain (β)	4-10
3.13.1	Regulating Action with a Varying Input Voltage (Constant I_L)	3-34	4.8.4	Relation between α_{dc} and β_{dc}	4-11
3.13.2	Regulating Action with a Varying Load (V_{in} Constant)	3-34	4.8.5	Input Characteristics	4-11
3.13.3	Limitations of Zener Regulators	3-35	4.8.6	Output Characteristics	4-12
3.13.4	Merits of Zener Regulator	3-35	4.8.7	Experimental Setup to Plot CE Characteristics	4-13
3.13.5	Applications of Zener Regulator	3-35	4.8.8	Features of CE Configuration	4-14
3.14	MSBTE Questions and Answers	3-39	4.8.9	Typical Junction Voltages	4-14
3.15	I-Scheme Questions and Answers	3-44	4.9	Common Collector (CC) Configuration	4-15
	• Review Questions.....	3-38	4.9.1	Practical Way to Draw Common Collector Configuration	4-15

Unit – III

Chapter 4 : Bipolar Junction Transistor 4-1 to 4-44

Syllabus : Unipolar and Bipolar devices, Symbol, Construction and working principle of NPN transistor, Transistor as switch and amplifier, CE, CB and CC configurations, Regions – Cut-off, Saturation and Active region, Transistor parameters -Alpha, Beta, Input and output resistances and relation between alpha and beta, Transistor biasing - DC load line, Q-point and Fixed bias and voltage divider biasing, RC coupled amplifier.

4.1	Introduction to Bipolar Junction Transistors	4-2	4.10	Comparison of Configurations	4-17
4.1.1	Advantages of a Transistor	4-2	4.11	Solved Examples	4-17
4.1.2	Transistor Definition	4-2	4.12	Specifications of a Transistor	4-19
4.1.3	Why is it called a “Bipolar” Transistor ?	4-2	4.13	Transistor Applications	4-19
4.1.4	Types and Symbols of Transistors	4-2	4.14	Need of Biasing	4-19
4.2	Construction of a BJT	4-3	4.14.1	Requirements of Transistor Biasing	4-20
4.2.1	An Unbiased Transistor	4-3	4.15	Transistor Biasing	4-20
4.3	Transistor Biasing in the Active Region	4-4	4.15.1	DC Load Line	4-20
4.4	Operation of NPN Transistor	4-4	4.15.2	The Quiescent Point (Q Point) or Bias Point or Operating Point	4-21
4.4.1	Operation of PNP Transistor	4-6	4.15.3	Selection of Q Point	4-21
4.5	Transistor Currents	4-7	4.15.4	Factors Affecting the Stability of Q Point	4-22
4.5.1	Circuit Symbols and Conventions	4-7	4.16	Need of Bias Stabilization	4-22
4.6	Transistor Configurations	4-7	4.16.1	Q Point Instability due to Temperature	4-22
4.7	Common Base (CB) Configuration	4-7	4.16.2	Q Point Instability due to Changes in β_{dc}	4-22
4.7.1	Current Relations in CB Configuration	4-8	4.16.3	Q Point Instability due to Variation in Parameters from One Device to Other ...	4-23
4.7.2	Features of CB Configuration	4-9	4.16.4	Stability Factors	4-23
4.8	Common Emitter (CE) Configuration	4-9	4.16.5	Stabilization Techniques (Types of Biasing Circuits)	4-23
			4.16.6	Steps to Obtain the DC Operating Point	4-23

<p>4.17 Fixed Bias Circuit4-24</p> <p> 4.17.1 Stabilization of Q Point4-24</p> <p> 4.17.2 Advantages of Fixed Bias Circuit4-24</p> <p> 4.17.3 Disadvantages of Fixed Bias Circuit4-24</p> <p>4.18 Voltage Divider Bias or Self Bias or Potential Divider Bias4-25</p> <p> 4.18.1 Advantages of Voltage Divider Bias Circuit4-26</p> <p> 4.18.2 Disadvantages of Voltage Divider Bias Circuit4-26</p> <p>4.19 Concept of Amplification and Definition of Amplifier4-26</p> <p>4.20 Block Diagram of an Amplifier4-26</p> <p> 4.20.1 Amplifier Characteristics4-27</p> <p>4.21 Classification Depending on the Type of Coupling4-27</p> <p>4.22 Transistor as an Amplifier4-27</p> <p> 4.22.1 Transistor as a Current Amplifier4-27</p> <p> 4.22.2 Transistor as a Voltage Amplifier4-28</p> <p>4.23 Single Stage RC Coupled CE Amplifier4-28</p> <p> 4.23.1 Circuit Components their Functions and Selection Criteria4-29</p> <p> 4.23.2 Operation of the RC Coupled Amplifier4-30</p> <p>4.24 Transistor as a Switch4-32</p> <p> 4.24.1 Applications of Transistor as a Switch4-33</p> <p>4.25 MSBTE Questions and Answers4-34</p> <p>4.26 I-Scheme Solved Examples4-38</p> <p>4.27 I-Scheme Questions and Answers4-39</p> <p> • Review Questions..... 4-33</p>	<p>5.1 Introduction to Junction Field Effect Transistor (JFET)5-2</p> <p> 5.1.1 Voltage Controlled or Current Controlled ?5-2</p> <p> 5.1.2 Unipolar or Bipolar ?5-2</p> <p> 5.1.3 Advantages of JFET over BJT5-2</p> <p> 5.1.4 Disadvantage of JFET5-3</p> <p> 5.1.5 Classification of Field Effect Transistors5-3</p> <p> 5.1.6 Construction of an n-Channel JFET5-3</p> <p> 5.1.7 Construction of p-channel JFET5-4</p> <p> 5.1.8 Unbiased JFET5-4</p> <p> 5.1.9 Biased JFET (Working of n-channel JFET)5-5</p> <p>5.2 Characteristics of JFET5-6</p> <p> 5.2.1 Drain Characteristics (Output Characteristics)5-6</p> <p> 5.2.2 Pinch off Voltage (V_p)5-8</p> <p> 5.2.3 Transfer Characteristics (Mutual Characteristics)5-8</p> <p>5.3 p-channel JFET5-9</p> <p>5.4 Comparison of JFET and BJT5-10</p> <p>5.5 Parameters of JFET5-10</p> <p> 5.5.1 DC Drain Resistance5-11</p> <p> 5.5.2 Dynamic (AC) Drain Resistance (r_d)5-11</p> <p> 5.5.3 Transconductance or Mutual Conductance (g_m)5-11</p> <p> 5.5.4 Amplification Factor (μ)5-12</p> <p> 5.5.5 Relation between the Parameters5-12</p> <p> 5.5.6 Input Resistance5-12</p> <p> 5.5.7 Applications of JFET5-12</p> <p>5.6 MOSFETs5-13</p> <p>5.7 Depletion Type MOSFET (D MOSFET)5-13</p> <p> 5.7.1 Basic Construction5-13</p> <p> 5.7.2 Working Principle of Depletion MOSFET5-14</p> <p> 5.7.3 p-channel Depletion Type MOSFET5-15</p> <p> 5.7.4 Symbols of n and p-type Depletion MOSFETs.....5-15</p> <p>5.8 Enhancement MOSFET5-15</p>
--	---

Unit – IV

Chapter 5 : Field Effect Transistors 5-1 to 5-24

Syllabus : FET types : JFET and MOSFET, Classification of JFET, Symbol, Construction and working principle of N-channel and P- channel JFET, Drain and transfer characteristics of JFET, JFET parameters : DC and AC drain resistance, Transconductance, Amplification factor, Symbol, Construction and working principle of MOSFET.

5.8.1 n-Channel EMOSFET5-16

5.8.2 Operation of n - channel Enhancement MOSFET5-16

5.8.3 p-channel Enhancement Type MOSFETs5-17

5.8.4 Symbols of Enhancement MOSFET5-17

5.8.5 Advantages of MOSFETs5-17

5.8.6 Disadvantages5-17

5.8.7 Applications of EMOSFET5-18

5.8.8 Applications of DMOSFET5-18

5.9 Comparisons5-18

5.9.1 Comparison of DMOSFET and EMOSFET5-18

5.9.2 Comparison of BJT, JFET and MOSFET5-18

5.10 MSBTE Questions and Answers5-19

5.11 I-Scheme Solved Examples5-23

5.12 I-Scheme Questions and Answers5-23

• **Review Questions..... 5-19**

Unit - V

Chapter 6 : Sensors and Transducers 6-1 to 6-28

Syllabus : Working of sensors and transducers, Selection criteria for transducers, Active and passive transducers, Inductive, Capacitive, Resistive pressure and piezoelectric transducers, Thermocouple and proximity sensors, Photodiode and phototransistor transducer.

6.1 Introduction 6-2

6.1.1 Basic Instrumentation System 6-2

6.1.2 Transducer 6-3

6.1.3 Sensors 6-3

6.2 Classification of Transducers 6-3

6.2.1 Active Transducers 6-3

6.2.2 Passive Transducers 6-3

6.2.3 Primary or Secondary Transducers 6-4

6.3 Characteristics (Parameters) of a Transducer 6-5

6.4 Selection Criteria of Transducer 6-5

6.5 Resistive Transducer 6-6

6.5.1 Potentiometer 6-6

6.5.2 Advantages of Resistance Potentiometers6-7

6.5.3 Disadvantages6-7

6.5.4 Variable Resistance Transducers for Displacement Measurement6-8

6.5.5 Measurement of Angular Displacement6-8

6.5.6 Potentiometric Pressure Transducer6-8

6.6 Strain Gauge Transducer6-8

6.6.1 Types of Strain Gauges6-9

6.6.2 Unbonded Strain Gauge6-9

6.6.3 Bonded Strain Gauges6-9

6.6.4 Foil Gauges6-9

6.6.5 Semiconductor Strain Gauge6-10

6.7 Inductive Transducers6-10

6.7.1 Transducers Working on the Principle of Variation of Self Inductance6-11

6.7.2 Variable Reluctance Inductive Transducer6-11

6.7.3 Transducers Operating on the Principle of Change in Mutual Inductance6-12

6.7.4 Differential Output Transducers6-12

6.7.5 Eddy Current type Inductive Transducers6-13

6.7.6 Pressure Inductive Transducer6-13

6.7.7 Variable Reluctance (Inductive) Transducer for Displacement Measurement6-13

6.7.8 Linear Variable Differential Transformer (LVDT)6-14

6.7.9 Load Cell (Pressure Cell)6-16

6.8 Capacitive Transducers (Pressure)6-16

6.8.1 Capacitive Pressure Transducer6-17

6.8.2 Advantage6-17

6.8.3 Disadvantages6-17

6.8.4 Applications6-17

6.9 Piezoelectric Pressure Transducers6-17

6.10 Thermocouples6-18

6.10.1 Thermocouple Materials6-19

6.10.2 Comparison of Temperature Transducers6-19



6.11	Proximity Sensors	6-20	6.13	Phototransistor	6-23
6.12	Photodiode	6-21	6.13.1	Construction and Biasing	6-23
6.12.1	Construction and Operation	6-21	6.13.2	Advantages of a Phototransistor	6-23
6.12.2	Photodiode Characteristics	6-22	6.13.3	Disadvantages of a Phototransistor	6-24
6.12.3	Advantages of Photodiode	6-22	6.13.4	Applications of Phototransistor	6-24
6.12.4	Disadvantages of Photodiode	6-22	6.14	I-Scheme Questions and Answers	6-25
6.12.5	Applications of Photodiode	6-22		• Review Questions	6-24
6.12.6	Other Applications	6-22		• Appendix-A :	A-1 to A-4

