

# Electric Circuits & Networks

(Code : 22330)

**SECOND YEAR DIPLOMA**

**Maharashtra State Board of Technical Education (MSBTE)**

Semester III – Electronics Engineering, Digital Electronics and Instrumentation  
Engineering Program Group  
(DE/EJ/ET/EN/EX/EQ/IE/IS/IC)

Strictly as per new revised 'I' Scheme w.e.f. academic year 2018-2019

**J. S. Katre**

M.E. (Electronics and Telecommunication)

Formerly, Assistant Professor

Department of Electronics Engineering

Vishwakarma Institute of Technology (V.I.T.), Pune.

Maharashtra, India

 **Tech Knowledge**<sup>TM</sup>  
Publications

MDO9B Price ₹ 205/-



**Electric Circuits & Networks (Code : 22330)**

(Semester III – Electronics Engineering, Digital Electronics & Instrumentation Engineering Program Group  
(DE/EJ/ET/EN/EX/EQ/IE/IS/IC), MSBTE)

J. S. Katre

Copyright © by Author. All rights reserved. No part of this publication may be reproduced, copied, or stored in a retrieval system, distributed or transmitted in any form or by any means, including photocopy, recording, or other electronic or mechanical methods, without the prior written permission of the publisher.

This book is sold subject to the condition that it shall not, by the way of trade or otherwise, be lent, resold, hired out, or otherwise circulated without the publisher's prior written consent in any form of binding or cover other than which it is published and without a similar condition including this condition being imposed on the subsequent purchaser and without limiting the rights under copyright reserved above.

**First Printed in India** : June 2003  
**First Edition** : June 2018 (As per I-Scheme)  
**Second Revised Edition** : June 2019 (TechKnowledge Publications)  
**Third Revised Edition** : June 2022

This edition is for sale in India, Bangladesh, Bhutan, Maldives, Nepal, Pakistan, Sri Lanka and designated countries in South-East Asia. Sale and purchase of this book outside of these countries is unauthorized by the publisher.

**ISBN** : 978-93-89233-09-4

**Published by :**


**TechKnowledge Publications**

**Head Office** : B/5, First floor, Maniratna Complex, Taware Colony, Aranyeshwar Corner,  
Pune - 411 009. Maharashtra State, India  
Ph : 91-20-24221234, 91-20-24225678.  
Email : info@techknowledgebooks.com,  
Website : www.techknowledgebooks.com

[ 22330 ] (FID : MDO9) (Book Code : MDO9B)

(Book Code : MDO9B)

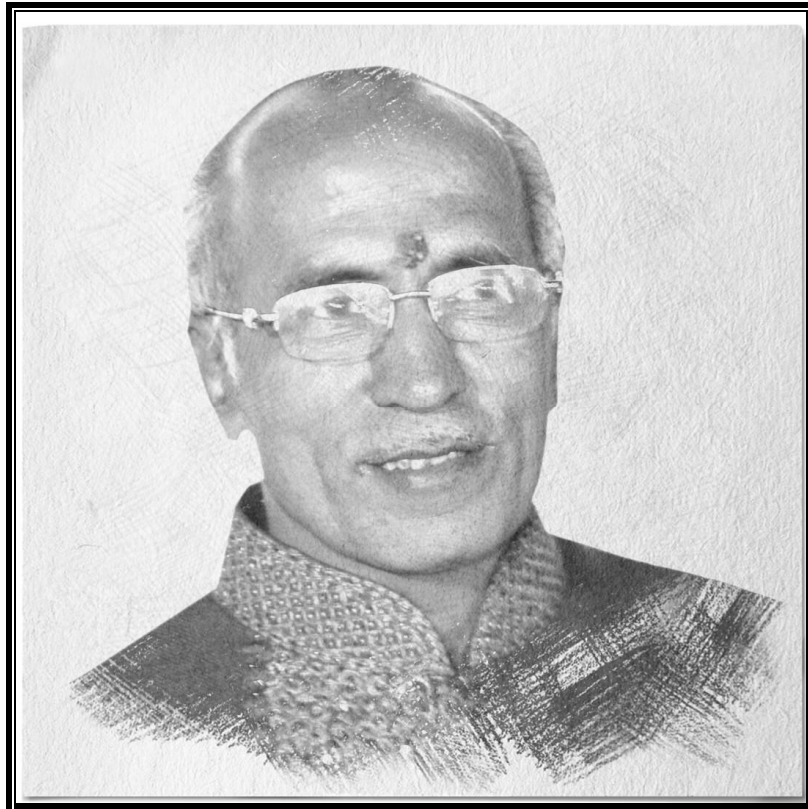*We dedicate this Publication soulfully and wholeheartedly,  
in loving memory of our beloved founder director,  
Late Shri. Pradeepji Lalchandji Lunawat,  
who will always be an inspiration, a positive force and strong support  
behind us.*



*“My work is my prayer to God”*

*- Lt. Shri. Pradeepji L. Lunawat*

*Soulful Tribute and Gratitude for all Your  
Sacrifices, Hardwork and 40 years of Strong Vision...*

## Syllabus...

Unit	Topics and Sub-topics
<b>Unit - I : Single Phase A.C. Circuits</b> <b>Refer chapters 1, 2 and 3</b>	1.1 Series AC circuits : R-L, R-C and R-L-C circuits, Impedance, Reactance, Phasor diagram, Impedance triangle, Power factor, Active (real) power, Apparent power, Reactive power, Power triangle. 1.2 AC series circuit by using complex algebra. 1.3 Parallel AC circuits, Resistance in parallel with pure inductance, Resistance in parallel with capacitance, Series combination of resistance and inductance in parallel with capacitance. 1.4 Concept of Admittance, Conductance and Susceptance. 1.5 Concept of initial and final conditions in switching circuits, Meaning of $t = 0^-$ , $t = 0^+$ and $t = \infty$ , R, L, and C at initial conditions, R, L, and C at final conditions.
<b>Unit - II : Resonance in Series and Parallel Circuits</b> <b>Refer chapter 4</b>	2.1 Series and parallel resonance. 2.2 Impedance and phase angle of a series and parallel resonant circuits. 2.3 Voltage and current in a series and parallel resonant circuit. 2.4 Bandwidth of RLC circuit (Series and parallel resonance). 2.5 Quality factor (Q) and its effect on bandwidth (Series and parallel resonance). 2.6 Magnification in series and parallel resonance circuits.
<b>Unit - III : Principles of Circuit Analysis</b> <b>Refer chapter 5</b>	3.1 Source transformation. 3.2 Star/delta and delta/star transformations. 3.3 Mesh analysis. 3.4 Node analysis.
<b>Unit - IV : Network Theorems</b> <b>Refer chapter 6</b>	4.1 Superposition theorem for both AC voltage and DC source. 4.2 Thevenin's theorem. 4.3 Norton's theorem. 4.4 Maximum power transfer theorem. 4.5 Reciprocity theorem. 4.6 Superposition theorem.

Unit	Topics and Sub-topics
<b>Unit - V : Two Port Networks</b> <b>Refer chapter 7</b>	5.1 Significance of two port network. 5.2 Open circuit (Z) and short circuit (Y) parameters. 5.3 Transmission (ABCD) parameter. 5.4 T and $\pi$ representation of circuits. 5.5 Reciprocal and symmetrical two port network (No derivation).

□□□

**Unit-I**

**Chapter 1 : Single Phase Series AC Circuits 1-1 to 1-38**

**Syllabus :** Series AC circuits : R-L, R-C and R-L-C circuits, Impedance, Reactance, Phasor diagram, Impedance triangle, Power factor, Active (real) power, Apparent power, Reactive power, Power triangle, AC series circuit by using complex algebra.

<p>1.1 Introduction ..... 1-2</p> <p>1.2 Important Basic Concepts ..... 1-2</p> <p>    1.2.1 Phasor Representation of         an Alternative Quantity ..... 1-2</p> <p>    1.2.2 Phase of an Alternating Quantity ..... 1-2</p> <p>    1.2.3 Mathematical Representation         of Phasor ..... 1-4</p> <p>    1.2.4 Addition and Subtraction of         Phasors (Using Rectangular Form) ..... 1-5</p> <p>    1.2.5 Multiplication and Division of         Phasors (Using Polar Form) ..... 1-5</p> <p>1.3 Single Phase AC Circuits ..... 1-6</p> <p>    1.3.1 Reactance and Impedance ..... 1-6</p> <p>    1.3.2 Reactance ..... 1-6</p> <p>    1.3.3 Inductive Reactance (<math>X_L</math>) ..... 1-6</p> <p>    1.3.4 Capacitive Reactance (<math>X_C</math>) ..... 1-6</p> <p>    1.3.5 Impedance (<math>Z</math>) ..... 1-7</p> <p>1.4 Pure Resistance in AC Circuit ..... 1-7</p> <p>    1.4.1 Analysis of the Purely Resistive         AC Circuit ..... 1-7</p>	<p>    1.4.2 Voltage and Current Waveforms and         Equations ..... 1-7</p> <p>    1.4.3 Phasor Diagram ..... 1-8</p> <p>    1.4.4 Impedance of the Purely         Resistive Circuit ..... 1-8</p> <p>    1.4.5 Average Power (<math>P_{av}</math>) ..... 1-8</p> <p>    1.4.6 Energy in Purely Resistive Circuit ..... 1-8</p> <p>1.5 Pure Inductance in AC Circuit ..... 1-8</p> <p>    1.5.1 Equations for Current <math>i</math> and Voltage <math>v</math> .... 1-9</p> <p>    1.5.2 Waveforms and Phasor Diagram ..... 1-9</p> <p>    1.5.3 Power in a Purely Inductive Circuit ..... 1-10</p> <p>    1.5.4 Impedance of a Purely         Inductive Circuit ..... 1-10</p> <p>1.6 Purely Capacitive AC Circuit ..... 1-10</p> <p>    1.6.1 Expressions for Voltage         and Current ..... 1-11</p> <p>    1.6.2 Current and Voltage Waveforms         and Phasor Diagram ..... 1-11</p> <p>    1.6.3 Power in Purely a         Capacitive AC Circuit ..... 1-12</p> <p>    1.6.4 Impedance of a Purely         Capacitive Circuit ..... 1-12</p> <p>1.7 Concept of Impedance and     Impedance Triangle ..... 1-12</p> <p>    1.7.1 Concept of Impedance ..... 1-12</p> <p>    1.7.2 Impedance Triangle ..... 1-12</p>
--	--



1.8	Different Types of Power ..... 1-13	1.10.11	Q-factor ..... 1-18
1.8.1	Apparent Power (S) ..... 1-13	1.11	The Series R-C Circuit ..... 1-24
1.8.2	Real Power or True Power or Active Power (P) ..... 1-13	1.11.1	Phasor (Vector) Diagram ..... 1-25
1.8.3	Reactive Power or Imaginary Power (Q) ..... 1-14	1.11.2	Impedance of RC Series Circuit ..... 1-25
1.8.4	Power Factor ..... 1-14	1.11.3	Impedance Triangle (Series R-C circuit) ..... 1-25
1.8.5	Importance (Significance) of Power Factor ..... 1-15	1.11.4	Waveforms and Expressions of Voltage and Current (Series R-C Circuit) ..... 1-26
1.8.6	Causes and Effects of Low Power Factor ..... 1-15	1.11.5	Average Power in Series R-C Circuit ..... 1-26
1.8.7	Power Triangle ..... 1-16	1.11.6	Power Triangle for R-C Series Circuit ..... 1-26
1.9	AC Circuits with Series Elements ..... 1-16	1.11.7	Various Powers and Power Factor ..... 1-27
1.10	The Series R-L Circuit ..... 1-16	1.11.8	Q Factor ..... 1-27
1.10.1	Phasor Diagram ..... 1-16	1.12	An R-L-C Series Circuit ..... 1-28
1.10.2	Impedance of L-R Series Circuit ..... 1-17	1.12.1	Importance of the Values of Reactances ..... 1-29
1.10.3	Impedance Triangle ..... 1-17	1.12.2	Phasor Diagrams ..... 1-29
1.10.4	Voltage and Current Waveforms ..... 1-17	1.12.3	Phasor Diagram for : $X_L > X_C$ ..... 1-29
1.10.5	Average Power in Series L-R Circuit .... 1-18	1.12.4	Phasor Diagram for : $X_L < X_C$ ..... 1-29
1.10.6	Power Triangle for L-R Series Circuit ... 1-18	1.12.5	Phasor Diagram for : $X_L = X_C$ ..... 1-30
1.10.7	Apparent Power (S) ..... 1-18	1.12.6	Impedance of Series LCR Circuit ..... 1-30
1.10.8	Real Power or True Power or Active Power (P) ..... 1-18	1.12.7	Impedance Triangle for an LCR Circuit ..... 1-30
1.10.9	Reactive Power or Imaginary Power (Q) ..... 1-18		
1.10.10	Power Factor ..... 1-18		

1.12.8 Power Supplied to the R.L.C. Circuit .....1-31

1.12.9 Power Triangle .....1-31

1.12.10 Various Powers and Power Factors of RLC Series Circuit .....1-31

1.12.11 Figure of Merit or Q-factor .....1-32

1.13 I-Scheme Solved Examples.....1-35

1.14 MSBTE Questions and Answers .....1-37

1.15 I-Scheme Questions and Answers .....1-37

- **Review Questions .....1-35**

**Unit-I**

**Chapter 2 : Single Phase AC Parallel Circuits 2-1 to 2-21**

**Syllabus :** Parallel AC circuits, Resistance in parallel with pure inductance, Resistance in parallel with capacitance, Series combination of resistance and inductance in parallel with capacitance, Concept of Admittance, Conductance and Susceptance.

2.1 A.C. Parallel Circuit .....2-2

2.1.1 Two Impedances in Parallel .....2-2

2.2 Multiplication and Division of Impedances .....2-2

2.2.1 Multiplication of Impedances .....2-2

2.2.2 Division of Impedances .....2-3

2.3 Types of Parallel AC Circuits .....2-3

2.4 Resistance in Parallel with Pure Inductance .....2-3

2.4.1 Phasor Diagram .....2-4

2.4.2 Impedance .....2-4

2.4.3 Voltage and Current Waveforms .....2-4

2.4.4 Power Factor .....2-4

2.5 Resistance in Parallel with Pure Capacitance .....2-4

2.5.1 Phasor Diagram .....2-5

2.5.2 Impedance .....2-5

2.5.3 Voltage and Current Waveforms .....2-5

2.5.4 Power Factor .....2-5

2.6 Series Combination of R and L in Parallel with Capacitor .....2-6

2.6.1 Phasor Diagram .....2-6

2.6.2 Impedance .....2-6

2.6.3 Power Factor .....2-6

2.7 The Concept of Admittance .....2-10

2.7.1 Conductance and Susceptance .....2-11

2.7.2 Admittance Triangle .....2-11

2.8 Solved Examples .....2-14

2.9 I-Scheme Solved Examples .....2-20

2.10 I-Scheme Questions and Answers .....2-20

- **Review Questions .....2-19**

**Unit-I**

**Chapter 3 : Initial & Final Conditions of Elements in a Network 3-1 to 3-6**

**Syllabus :** Concept of initial and final conditions in switching circuits, Meaning of  $t = 0^-$ ,  $t = 0^+$  and  $t = \infty$ , R, L, and C at initial conditions, R, L and C at final conditions.

3.1 Concept of Initial and Final Conditions in Switching Circuits .....3-2

3.1.1 Concept of Initial Conditions .....3-2





3.1.2	Final Conditions .....	3-2	4.2.6	Voltage and Current .....	4-5
3.1.3	Meaning of $t = 0^-$ , $t = 0^+$ and $t = \infty$ .....	3-2	4.2.7	Variation of Power Factor .....	4-5
3.2	Initial and Final Conditions in Elements .....	3-3	4.2.8	The Q-Factor (Quality Factor) of a Series Resonant Circuit .....	4-5
3.2.1	Initial Conditions in Resistor .....	3-3	4.2.9	Bandwidth of a Series Resonant Circuit .....	4-6
3.2.2	Initial and Final Conditions in Inductor ...	3-3	4.2.10	Magnification in Series Resonant Circuit .....	4-7
3.2.3	Initial and Final Condition in Capacitor ...	3-4	4.2.11	Characteristics of Series Resonant Circuit .....	4-7
3.2.4	Equivalent Circuits .....	3-5	4.3	Solved Examples on Series Resonance .....	4-8
3.3	I-Scheme Questions and Answers .....	3-6	4.4	Resonance in Parallel RLC Circuit .....	4-11
	• <b>Review Questions</b> .....	<b>3-6</b>	4.4.1	Resonant Frequency ( $f_r$ ) .....	4-12
<b>Unit-II</b>			4.4.2	Dynamic Impedance at Resonance ( $Z_D$ ) .....	4-13
<b>Chapter 4 : Resonance in Series and Parallel Circuits</b>			4.4.3	Current and Voltage .....	4-13
<b>4-1 to 4-21</b>			4.4.4	Phase Angle of Parallel Resonant Circuit .....	4-14
<b>Syllabus</b> : Series and parallel resonance, Impedance and phase angle of a series and parallel resonant circuits, Voltage and current in a series and parallel resonant circuit, Bandwidth of RLC circuit (Series and parallel resonance), Quality factor (Q) and its effect on bandwidth (Series and parallel resonance), Magnification in series and parallel resonance circuits.			4.4.5	Why is the Parallel Circuit Called a Rejector Circuit ? .....	4-14
4.1	Resonance .....	4-2	4.4.6	Q-Factor of the Parallel Circuit .....	4-14
4.2	Resonance in Series RLC Circuit .....	4-2	4.4.7	Effect of Q on Bandwidth .....	4-14
4.2.1	Resonant Frequency ( $f_r$ ) .....	4-2	4.4.8	Magnification in Parallel Resonant Circuit .....	4-15
4.2.2	Phasor Diagrams of RLC Series Resonant Circuit .....	4-3	4.4.9	Current Through C .....	4-15
4.2.3	Impedance at Resonance .....	4-4	4.4.10	Characteristics of Parallel Resonant Circuit .....	4-15
4.2.4	Current at Resonance .....	4-4			
4.2.5	Phase Angle of Series Resonant Circuit .....	4-5			



4.5	Solved Examples on Parallel Resonance .....	4-16
4.6	Comparison of Series and Parallel Resonant Circuits .....	4-19
4.7	I-Scheme Solved Examples.....	4-20
4.8	I-Scheme Questions and Answers .....	4-20
	• <b>Review Questions</b> .....	<b>4-19</b>

### Unit-III

#### Chapter 5 : Principle of DC Circuit Analysis 5-1 to 5-46

**Syllabus :** Source transformation, Star/delta and delta/star transformations, Mesh analysis, Node analysis.

5.1	Introduction to Networks / Circuits .....	5-2
5.1.1	Network .....	5-2
5.1.2	Circuit Element .....	5-2
5.1.3	Concept of Open and Short Circuit .....	5-2
5.1.4	Branch Mesh and Node .....	5-2
5.1.5	Resistors in Series .....	5-3
5.1.6	Voltage Division Formula .....	5-3
5.1.7	Resistors in Parallel .....	5-4
5.1.8	Current Division Formula .....	5-4
5.2	Review of Ohm's Law .....	5-9
5.3	Concept of Ideal and Practical Voltage and Current Sources .....	5-10
5.3.1	Independent Voltage Sources .....	5-10
5.3.2	Current Sources .....	5-11
5.4	Source Transformation .....	5-13

5.4.1	Transformation of Voltage Source to Current Source .....	5-13
5.4.2	Transformation of Current Source to Voltage Source .....	5-13
5.4.3	Voltage Sources in Series .....	5-14
5.4.4	Current Sources in Parallel .....	5-15
5.5	Star-Delta and Delta-Star Transformation .....	5-17
5.5.1	The Star Network .....	5-17
5.5.2	The Delta Network .....	5-17
5.5.3	Delta-Star Transformation .....	5-18
5.5.4	Star to Delta Conversion .....	5-19
5.6	Kirchhoff's Laws .....	5-27
5.6.1	Kirchhoff's Current Law (KCL) .....	5-27
5.6.2	Node Analysis (Nodal Analysis) .....	5-28
5.6.3	Mesh or Loop and Sign Convention .....	5-32
5.6.4	Kirchhoff's Voltage Law (or Mesh or Loop Law) .....	5-33
5.6.5	Procedure to be Followed to Solve an Example using Kirchhoff's Laws .....	5-34
5.6.6	Mesh Analysis or Maxwell's Loop Current Method .....	5-35
5.7	MSBTE Questions and Answers .....	5-40
5.8	I-Scheme Solved Examples .....	5-41
5.9	I-Scheme Questions and Answers .....	5-45
	• <b>Review Questions</b> .....	<b>5-40</b>

**Unit-IV**

**Chapter 6 : Network Theorems 6-1 to 6-45**

**Syllabus :** Superposition theorem for both AC voltage and DC source. Thevenin's theorem, Norton's theorem, Maximum power transfer theorem, Reciprocity theorem, Superposition theorem.

6.1 Introduction ..... 6-2

6.2 Different Types of Networks ..... 6-2

    6.2.1 Active or Passive Networks ..... 6-2

    6.2.2 Unilateral or Bilateral Networks ..... 6-2

    6.2.3 Linear or Non-linear Network..... 6-3

6.3 Superposition Theorem ..... 6-3

    6.3.1 Statement of the Superposition Theorem ..... 6-3

    6.3.2 Steps to be Followed to Apply the Superposition Theorem ..... 6-3

    6.3.3 Examples on Superposition Theorem .... 6-4

    6.3.4 Superposition Theorem for AC Source ... 6-8

    6.3.5 Applications of the Superposition Theorem ..... 6-12

    6.3.6 Drawbacks (Limitations) of the Superposition Theorem ..... 6-12

6.4 Thevenin's Theorem ..... 6-13

    6.4.1 Implications of Thevenin's Theorem ..... 6-15

    6.4.2 Advantages of Thevenin's Theorem ..... 6-15

    6.4.3 Where can't We Apply the Thevenin's Theorem ?..... 6-15

    6.4.4 Applications of the Thevenin's Theorem ..... 6-15

    6.4.5 Drawbacks of the Thevenin's Theorem ..... 6-15

    6.4.6 Solved Examples on Thevenin's Theorem ..... 6-16

6.5 Norton's Theorem ..... 6-19

    6.5.1 Steps to be Followed to Apply the Norton's Theorem ..... 6-20

    6.5.2 Equivalence between Thevenin's and Norton's Theorems ..... 6-20

    6.5.3 Drawbacks of Norton's Theorem ..... 6-21

    6.5.4 Applications of the Norton's Theorem ..... 6-21

    6.5.5 Solved Examples on Norton's Theorem ..... 6-21

6.6 Maximum Power Transfer Theorem ..... 6-29

    6.6.1 Condition for Maximum Power Transfer ..... 6-29

    6.6.2 Stepwise Procedure for Maximum Power Transfer Theorem ..... 6-30

    6.6.3 Applications of Maximum Power Transfer Theorem ..... 6-30

6.7 Reciprocity Theorem ..... 6-34

    6.7.1 Explanation of Reciprocity Theorem ..... 6-34

    6.7.2 Features of the Reciprocity Theorem ..... 6-38

6.7.3 Drawbacks of the Reciprocity Theorem ..... 6-38

6.8 I-Scheme Solved Examples ..... 6-39

6.9 I-Scheme Questions and Answers ..... 6-44

• **Review Questions** ..... **6-38**

**Unit-V**

**Chapter 7 : Two Port Networks 7-1 to 7-15**

**Syllabus :** Significance of two port network, Open circuit (Z) and short circuit (Y) parameters, Transmission (ABCD) parameter, T and  $\pi$  representation of circuits, Reciprocal and symmetrical two port network (No derivation).

7.1 Introduction ..... 7-2

7.2 Open Circuit Impedance Parameters (Z-Parameters) ..... 7-2

7.3 Two Port Admittance Parameters [Short Circuit Admittance (Y) Parameters] ..... 7-5

7.3.1 Solved Examples on Y Parameters ..... 7-7

7.4 Transmission Parameters (ABCD Parameters) ..... 7-8

7.4.1 Condition of Symmetry ..... 7-9

7.4.2 Condition for Reciprocity ..... 7-9

7.4.3 Expression of ABCD Parameters ..... 7-9

7.4.4 Solved Examples on Transmission Parameters ..... 7-9

7.5 T Representation of Circuits ..... 7-10

7.5.1 Characteristic Impedance ( $Z_0$ ) of Symmetrical T-Network ..... 7-10

7.6  $\pi$  Representation of Circuits ..... 7-11

7.6.1 Characteristics Impedance ..... 7-11

7.7 I-Scheme Solvd Examples ..... 7-12

7.8 I-Scheme Questions and Answers ..... 7-13

• **Review Questions** ..... **7-12**

