

**Unit-I****Chapter 1 : Basic Electrical Parameters 1-1 to 1-34**

**Syllabus :** Direct current (DC), Alternating current (AC), Voltage source and current source : Ideal and practical. Electric current, Electric potential, Potential difference (P.D.), Electromotive force (EMF). Electric work, Power and energy, Resistance, Resistivity, Conductivity, Effects of temperature on resistance, Types of resistors and their applications, Heating effect, Magnetic effect, Chemical effect of electric current.

1.1	Introduction to Electricity .....	1-1	1.9.1	Direct Current (D.C.) .....	1-12
1.2	Electrical Quantities .....	1-1	1.9.2	Applications of Direct Current .....	1-12
1.3	Concept of EMF and Current .....	1-1	1.9.3	Alternating Current (A.C.) .....	1-12
1.3.1	Concept of EMF .....	1-1	1.9.4	Advantages of AC Over DC .....	1-13
1.3.2	Concept of Current .....	1-1	1.9.5	Various Types of AC Waveforms .....	1-13
1.4	Concept of Electric Potential and Potential Difference .....	1-2	1.9.6	Applications of Alternating Current .....	1-13
1.4.1	Definition of Electric Potential .....	1-2	1.10	Sources of DC Supply .....	1-13
1.4.2	Potential Difference (P.D.) .....	1-2	1.10.1	Voltage and Current Sources .....	1-13
1.5	Concept of Resistance (R) .....	1-2	1.10.2	Independent Voltage Sources .....	1-13
1.6	Factors Affecting the Resistance Value .....	1-3	1.10.3	Independent Current Sources .....	1-14
1.6.1	Concept of Resistivity .....	1-3	1.11	Source Conversion .....	1-15
1.6.2	Conductance (G) .....	1-3	1.11.1	Conversion of Voltage Source to Current Source .....	1-15
1.6.3	Concept of Conductivity ( $\sigma$ ) .....	1-3	1.11.2	Conversion of Current Source to Voltage Source .....	1-16
1.6.4	Effect of Temperature on Resistance .....	1-4	1.12	Effects of Electric Current .....	1-18
1.6.5	Series Circuit (Resistors in Series) .....	1-5	1.12.1	The Chemical Effect of Electric Current .....	1-19
1.6.6	Parallel Circuit (Resistors in Parallel) .....	1-5	1.12.2	Electromagnets (Magnetic Effects of Electric Current) .....	1-19
1.7	Basic Definitions .....	1-6	1.12.3	Heating Effects of Electric Current .....	1-19
1.7.1	Network or Circuit .....	1-6	1.13	SI Units of Work, Power and Energy .....	1-20
1.7.2	Power .....	1-6	1.14	Concept of Electrical Work, Power and Energy .....	1-20
1.7.3	Electrical Energy .....	1-6	1.14.1	Examples on Work Power Energy .....	1-20
1.7.4	Circuit Element .....	1-6	1.15	Types of Resistors .....	1-24
1.7.5	Branch, Mesh and Node .....	1-6	1.16	Fixed Resistors .....	1-24
1.7.6	Relation between Voltage, Current, Resistance Ohm's Law .....	1-7	1.16.1	Carbon Composition Resistor .....	1-24
1.8	Temperature Coefficient of Resistance (R.T.C.) ...	1-7	1.16.2	Wire-wound Resistors .....	1-25
1.8.1	Expression for the Resistance at $t^{\circ}\text{C}$ .....	1-8	1.16.3	Film Type Resistors .....	1-25
1.8.2	Effect of Temperature on R.T.C. ....	1-8	1.16.4	Carbon Film Resistors .....	1-26
1.8.3	Effect of Temperature on Resistivity ( $\rho$ ) .	1-9	1.16.5	Metal Film Resistors .....	1-26
1.8.4	Temperature Coefficient of Resistivity ....	1-9	1.16.6	General Applications of Fixed Resistors .....	1-27
1.9	Classification of Electric Current .....	1-12	1.17	MSBTE Questions and Answers .....	1-27
			1.18	I-Scheme Solved Examples .....	1-32
			1.19	I-Scheme Questions and Answers .....	1-32
				• <b>Review Questions</b> .....	<b>1-27</b>
				• <b>1 and 2 Marks Questions With Answers</b> ....	<b>1-30</b>

**Unit-II****Chapter 2 : DC Circuits 2-1 to 2-50**

**Syllabus :** Ohm's law, Internal resistance of source, Internal voltage drop, Terminal voltage, Resistances in series, Resistances in parallel, Active, Passive, Linear, Non linear circuits, Unilateral circuits and Bilateral circuits, Passive and active networks, Node, Branch, Loop, Mesh. Kirchhoff's current law, Kirchhoff's voltage law.

2.1	DC Circuits .....	2-1
2.1.1	Ohm's Law .....	2-1
2.1.2	Internal Resistance of Source .....	2-2
2.1.3	Voltage Drop .....	2-2
2.1.4	Terminal Voltage .....	2-2
2.2	Resistors in Series .....	2-2
2.2.1	Expression for the Equivalent Resistance .....	2-3
2.3	Voltage Division Formula .....	2-4
2.4	Resistors in Parallel .....	2-4
2.4.1	Expression for the Equivalent Resistance .....	2-4
2.5	Current Division Formula .....	2-5
2.5.1	Comparison between Series and Parallel Circuits .....	2-6
2.5.2	Solved Examples on Series and Parallel Circuits .....	2-7
2.5.3	Duality between Series and Parallel Circuits .....	2-14
2.6	Definitions of Terms Related to Electrical Circuits .....	2-15
2.6.1	Classification of Electric Networks .....	2-15
2.6.2	Active or Passive Networks .....	2-15
2.6.3	Unilateral or Bilateral Networks .....	2-16
2.6.4	Distributed or Lumped Networks .....	2-16
2.6.5	Linear or Non-linear Network .....	2-16
2.7	Star-Delta and Delta-Star Transformation .....	2-17
2.7.1	The Star Network .....	2-17
2.7.2	The Delta Network .....	2-17
2.7.3	Delta-Star Transformation .....	2-17
2.7.4	Star to Delta Conversion .....	2-18
2.8	Kirchhoff's Laws .....	2-26
2.8.1	Kirchhoff's Current Law (KCL) .....	2-26

2.8.2	Mesh or Loop and Sign Convention .....	2-29
2.8.3	Kirchhoff's Voltage Law (or Mesh or Loop Law) .....	2-30
2.8.4	Procedure to be Followed to Solve an Example using Kirchhoff's Laws .....	2-30
2.9	MSBTE Questions and Answers .....	2-40
2.10	I-Scheme Solved Examples .....	2-47
2.11	I-Scheme Questions and Answers .....	2-49
	• <b>Review Questions</b> .....	<b>2-40</b>
	• <b>1 and 2 Marks Questions With Answers</b> ....	<b>2-45</b>

**Unit-III****Chapter 3 : Capacitors 3-1 to 3-24**

**Syllabus :** Capacitor, Parallel plate capacitor, Various connections of capacitor, Energy stored in capacitor, Charging and discharging of capacitor, Breakdown voltage and dielectric strength, Types of capacitors and applications.

3.1	Introduction .....	3-1
3.2	Laws and Definition .....	3-1
3.2.1	Coulomb's Law .....	3-1
3.2.2	Electric Field .....	3-1
3.2.3	Electrical Flux Lines or Electric Lines of Force .....	3-1
3.2.4	Electric Flux .....	3-1
3.2.5	Electric Flux Density (D) .....	3-1
3.2.6	Electric Field Strength or Field Intensity .....	3-2
3.2.7	Permittivity ( $\epsilon$ ) .....	3-2
3.2.8	Absolute Permittivity ( $\epsilon$ ) .....	3-2
3.2.9	Permittivity of Free Space ( $\epsilon_0$ ) .....	3-2
3.2.10	Relative Permittivity ( $\epsilon_r$ ) .....	3-2
3.3	Concept and Definition of Capacitor .....	3-3
3.3.1	Capacitor and Capacitance .....	3-3
3.3.2	Relation between Charge and Applied Voltage .....	3-3
3.3.3	Capacitance of a Parallel Plate Capacitor (Uniform Di-electric Medium) .....	3-4
3.3.4	Medium Partly Air .....	3-4
3.4	Capacitors in Series .....	3-7
3.4.1	Series Combination of Two Capacitors .....	3-8



3.5	Capacitors in Parallel .....	3-8	4.4.1	The Right Hand Gripping Rule (or Right Hand Thumb Rule) .....	4-4
3.6	Energy Stored by a Capacitor .....	3-12	4.4.2	The Corkscrew Rule .....	4-4
3.7	Charging and Discharging of a Capacitor through a Resistor .....	3-13	4.5	Dot and Cross Convention .....	4-5
	3.7.1 Charging of a Capacitor .....	3-13	4.6	Permeability .....	4-5
	3.7.2 Discharging of a Capacitor .....	3-14	4.6.1	Absolute Permeability ( $\mu$ ) .....	4-5
3.8	Dielectric Strength and Breakdown Voltage .....	3-15	4.6.2	Permeability of Free Space or Vacuum ( $\mu_0$ ) .....	4-5
	3.8.1 Definition of Breakdown Voltage .....	3-16	4.6.3	Relative Permeability ( $\mu_r$ ) .....	4-5
	3.8.2 Definition of Dielectric Strength .....	3-16	4.7	Definitions Concerning Magnetic Circuits .....	4-6
3.9	Types of Capacitors and their Applications .....	3-16	4.7.1	Magnetomotive Force (MMF) .....	4-6
3.10	Electrolytic Capacitors .....	3-17	4.7.2	Reluctance (S) .....	4-6
3.11	MSBTE Questions and Answers .....	3-18	4.7.3	Permeance .....	4-6
3.12	I-Scheme Solved Examples .....	3-22	4.7.4	Reluctivity .....	4-7
3.13	I-Scheme Questions and Answers .....	3-23	4.8	Magnetic Circuit .....	4-8
	• <b>Review Questions</b> .....	<b>3-18</b>	4.8.1	Comparisons of Magnetic and Electrical Circuits .....	4-9
	• <b>1 and 2 Marks Questions With Answers</b> ....	<b>3-20</b>	4.9	Ohm's Law of Magnetic Circuits .....	4-10
<b>Unit-IV</b>			4.10	Kirchhoff's Laws for the Magnetic Circuits .....	4-10
<b>Chapter 4 : Magnetic Circuits</b>			4.10.1	Kirchhoff's Flux Law .....	4-10
<b>4-1 to 4-26</b>			4.10.2	Kirchhoff's MMF Law .....	4-10
<b>Syllabus</b> : Magnetic lines of force, Flux, Flux density, Magnetic flux density, Magneto-motive Force (MMF), Ampere Turns (AT), Reluctance, Permeance, Reluctivity, Electric and magnetic circuits : Series magnetic and parallel magnetic circuit, Magnetization curve (B-H curve), Magnetic hysteresis, Hysteresis loop, Applications.					
4.1	Introduction .....	4-1	4.11	Composite Magnetic Circuits .....	4-10
4.2	Magnet, Magnetism and its Properties .....	4-1	4.11.1	Series Magnetic Circuit .....	4-11
	4.2.1 Concept of Magnet and Electromagnet ..	4-1	4.11.2	A Series Magnetic Circuit with Air Gap .....	4-11
	4.2.2 Important Properties of a Magnet .....	4-1	4.12	Solved Examples .....	4-12
	4.2.3 Applications of Permanent Magnets .....	4-1	4.13	Parallel Magnetic Circuit .....	4-15
	4.2.4 Electromagnets .....	4-1	4.13.1	Expression for the Total MMF (Ampere-Turns) .....	4-15
	4.2.5 Applications of Electromagnets .....	4-2	4.13.2	Expression for the Reluctance of a Parallel Magnetic Circuit .....	4-15
4.3	Law's and Definitions .....	4-2	4.13.3	Parallel Magnetic Circuit with Air Gap .....	4-16
	4.3.1 Pole Strength .....	4-2	4.14	B-H Curve or Magnetization Curve .....	4-16
	4.3.2 Laws of Magnetism .....	4-2	4.14.1	Magnetic Hysteresis and Hysteresis Loop .....	4-17
	4.3.3 Magnetic Field .....	4-2	4.14.2	Hysteresis Loss .....	4-18
	4.3.4 Concept of Magnetic Lines of Force .....	4-2	4.14.3	Magnetization Curves for Magnetic and Non-magnetic Materials .....	4-18
	4.3.5 Magnetic Flux $\phi$ .....	4-3	4.14.4	Factors Affecting the Hysteresis Loss ..	4-19
	4.3.6 Magnetic Flux Density (B) .....	4-3	4.15	MSBTE Questions and Answers .....	4-20
	4.3.7 Magnetic Field Strength (H) .....	4-3	4.16	I-Scheme Solved Examples .....	4-24
4.4	Magnetic Field Associated with a Straight Conductor .....	4-3	4.17	I-Scheme Questions and Answers .....	4-25



- **Review Questions** .....4-19
- **1 and 2 Marks Questions With Answers** ....4-22

**Unit-V**
**Chapter 5 : Electromagnetic Induction**      **5-1 to 5-30**

**Syllabus** : Development of induced emf and current, Faraday's laws of electromagnetic induction, Static and dynamic emf, Lenz's law, Fleming's right hand rule, Self inductance, Co-efficient of self inductance (L), Mutual inductance, Co-efficient of mutual inductance, Self induced emf and mutually induced emf, Coefficient of coupling, Inductances in series, Types of inductors, Their applications and energy stored in magnetic field.

5.1	Relation between Magnetism and Electricity .....	5-1
5.2	Development of Induced Emf and Current .....	5-1
5.3	Electromagnetic Induction .....	5-1
5.4	Faraday's Laws of Electromagnetic Induction .....	5-1
	5.4.1 Faraday's First Law .....	5-1
	5.4.2 Faraday's Second Law .....	5-2
5.5	Direction of Induced E.M.F. ....	5-2
	5.5.1 Fleming's Right Hand Rule .....	5-2
	5.5.2 Lenz's Law .....	5-3
5.6	Nature of the Induced E.M.F. ....	5-3
5.7	Dynamically Induced E.M.F. ....	5-3
	5.7.1 Magnitude of Dynamically Induced E.M.F. ....	5-3
	5.7.2 Direction of Dynamically Induced EMF ...	5-4
5.8	Statically Induced E.M.F. ....	5-5
	5.8.1 Self Induced E.M.F. ....	5-6
	5.8.2 Self Inductance .....	5-6
	5.8.3 Expression for the Coefficient of Self Inductance (L) .....	5-6

5.8.4	Factors Affecting the Inductance of the Coil .....	5-7
5.8.5	Comparison of Statically and Dynamically Induced EMF .....	5-7
5.9	Mutually Induced E.M.F. ....	5-10
	5.9.1 Mutual Inductance (M) .....	5-11
	5.9.2 Alternate Way of Defining the Mutual Inductance .....	5-11
	5.9.3 Expression for Mutual Inductance .....	5-11
	5.9.4 Coefficient of Coupling (K) .....	5-11
	5.9.5 Comparison of Self Induced emf and Mutually Induced emf .....	5-12
5.10	Effective Inductance of the Series Connection (Inductances in Series) .....	5-14
	5.10.1 Series Aiding or Cumulatively Coupling .....	5-14
	5.10.2 Series Opposition or Differential Coupling of Coils .....	5-15
	5.10.3 Series and Parallel Combinations of Isolated Inductances .....	5-15
5.11	Energy Stored in the Magnetic Field .....	5-16
	5.11.1 Expression for the Energy Stored in the Magnetic Field .....	5-17
5.12	Types of Inductors and their Applications .....	5-18
	5.12.1 Iron Core Inductors .....	5-19
	5.12.2 Air Core Inductor .....	5-19
	5.12.3 Ferrites .....	5-19
	5.12.4 Ferrite Core Inductors .....	5-20
	5.12.5 General Applications of Inductors .....	5-20
5.13	MSBTE Questions and Answers .....	5-21
5.14	I-Scheme Solved Examples .....	5-24
5.15	I-Scheme Questions and Answers .....	5-26
	• <b>Review Questions</b> .....	<b>5-20</b>
	• <b>1 and 2 Marks Questions With Answers</b> ....	<b>5-23</b>

