

**Unit-I****Chapter 1 : Power Electronic Devices****1-1 to 1-36**

**Syllabus :** Power electronic devices, Power transistors : Construction, Working principle, V-I characteristics and uses. IGBT : Construction, Working principle, V-I characteristics and uses. Concept of single electron transistor (SET) - Aspects of nano technology.

1.1	Introduction to Power Electronics .....	1-2
1.1.1	Principle of Power Electronics .....	1-2
1.1.2	Application Areas of Power Electronics .....	1-2
1.2	Power Semiconductor Devices .....	1-3
1.2.1	Need of High Power Semiconductor Switches .....	1-3
1.2.2	General Requirements of Power Devices .....	1-3
1.3	Introduction to Power Transistors .....	1-3
1.3.1	Classification of Power Transistors .....	1-3
1.3.2	Need of Power Transistor, MOSFET and IGBT .....	1-4
1.4	Power BJT .....	1-4
1.5	Construction of Power BJT .....	1-5
1.5.1	Power BJT Structure .....	1-5
1.6	I-V Characteristics of the Power Transistor (Static Characteristics) .....	1-6
1.6.1	Operation of Power Transistor .....	1-9
1.6.2	How is Power BJT Different from Small Signal BJT ? .....	1-9
1.6.3	Quasi Saturation in Power Transistors .....	1-9
1.6.4	Hard Saturation .....	1-11
1.7	Various Losses in Power Devices .....	1-11
1.7.1	Static Losses .....	1-11
1.8	Switching (Dynamic) Characteristics of a Power BJT .....	1-12
1.8.1	Model of Power BJT under Transient Conditions .....	1-12
1.8.2	BJT Turn on Characteristics (Dynamic Characteristics) .....	1-13
1.8.3	Turn off Characteristics .....	1-14
1.8.4	Charge Profile during Turn-off .....	1-15
1.9	Second Breakdown in Power Transistors .....	1-16
1.9.1	Interdigitated Structure of Power Transistors .....	1-17
1.10	Merits, Demerits and Applications of a Power BJT .....	1-17



1.11	Power MOSFET .....	1-18
1.11.1	Structure of a Power MOSFET .....	1-19
1.11.2	Simplified Structure of Power MOSFET .....	1-19
1.11.3	Principle of Operation .....	1-20
1.11.4	I-V Characteristics (Steady State Characteristics) .....	1-22
1.12	Merits, Demerits and Applications of Power MOSFET .....	1-23
1.12.1	Merits of a Power MOSFET .....	1-23
1.12.2	Demerits of a Power MOSFET .....	1-23
1.12.3	Applications of Power MOSFET .....	1-23
1.13	Insulated Gate Bipolar Transistor (IGBT) .....	1-24
1.13.1	Features of IGBT .....	1-24
1.14	Basic Structure of IGBT .....	1-24
1.15	I-V Characteristics (Steady State Characteristics) .....	1-25
1.16	Types of IGBTs .....	1-26
1.16.1	Non Punch Through IGBT .....	1-26
1.16.2	Punch Through IGBT .....	1-27
1.17	Principle of Operation of IGBT .....	1-28
1.18	Merits, Demerits and Applications of IGBT .....	1-29
1.18.1	Merits of IGBT .....	1-29
1.18.2	Demerits of IGBT .....	1-29
1.18.3	Applications of IGBT .....	1-29
1.18.4	Advantages of IGBT over BJT .....	1-30
1.18.5	Advantages of IGBT over MOSFET .....	1-30
1.19	Comparison of Power BJT and IGBT .....	1-30
1.20	Aspects of Nanotechnology .....	1-30
1.20.1	Definitions .....	1-31
1.20.2	Properties of Nanoparticles .....	1-31
1.20.3	Applications of Nanoparticles .....	1-31
1.21	Single Electron Transistor (SET) .....	1-31
1.21.1	Single Electron Transistor (SET) .....	1-32
1.21.2	SET Schematic and its Working .....	1-32



1.21.3	Principle of Single Electron Tunneling & Coulomb Blockade .....	1-33
1.21.4	Conditions to Achieve Coulomb Blockade (CB) .....	1-34
1.21.5	I-V Characteristics of SET .....	1-34
1.21.6	Advantages of SET .....	1-34
1.21.7	Disadvantages .....	1-34
1.21.8	Applications of SET .....	1-34
1.22	MSBTE Questions and Answers .....	1-35
1.23	I-Scheme Questions and Answers .....	1-36
•	<b>Review Questions</b> .....	<b>1-34</b>

Unit-II

**Chapter 2 : Thyristor Family Devices****2-1 to 2-57**

**Syllabus :** SCR : Construction, Two transistor analogy, Types, Working and V-I characteristics. SCR mounting and cooling. Types of thyristors : SCR, LASCR, SCS, GTO, UJT, PUT, DIAC and TRIAC. Thyristor family devices : Symbol, Construction, Operating principle and V-I characteristics. Protection circuits : Over-voltage, Over-current, Snubber, Crowbar.

2.1	Introduction to Thyristors Family Devices .....	2-2
2.1.1	Applications of Thyristors .....	2-2
2.1.2	Silicon Controlled Rectifier (SCR) .....	2-3
2.1.3	Important Features of SCR .....	2-3
2.1.4	Construction of SCR .....	2-3
2.1.5	I-V Characteristics (Static Characteristics) .....	2-4
2.1.6	Operation of SCR .....	2-7
2.1.7	Two Transistor Analogy of SCR .....	2-7
2.1.8	SCR as a Switch .....	2-9
2.1.9	Drawbacks of SCR .....	2-9
2.1.10	Advantages of SCR .....	2-9
2.1.11	Applications of SCR .....	2-10
2.1.12	SCR Ratings (Specifications) .....	2-10
2.1.13	Current Ratings .....	2-10
2.1.14	Voltage Ratings .....	2-11
2.1.15	Types of SCR .....	2-12
2.1.16	Phase Control SCRs (Converter Grade SCRs) .....	2-12



2.1.17	Fast Switching SCRs (Inverter Grade SCRs)	2-13
2.1.18	Reverse Conducting Thyristor (RCT)	2-14
2.2	Bidirectional Triode SCRs (Triacs)	2-14
2.2.1	Construction of a Triac	2-14
2.2.2	Characteristics of Triac (Static Characteristics)	2-15
2.2.3	Different States of Triac Operation	2-16
2.3	Modes of Operation	2-17
2.3.1	Operating Modes of Triac	2-17
2.3.2	Advantages of Triac	2-19
2.3.3	Disadvantages of Triac	2-20
2.3.4	Applications of Triac	2-20
2.3.5	Specifications of a Triac	2-20
2.4	Gate Turn Off SCR (GTO)	2-20
2.4.1	Construction of GTO	2-20
2.4.2	Operating Principle	2-21
2.4.3	GTO Turn off Mechanism	2-22
2.4.4	Magnitude of $I_G^{(-)}$ for Reliable Turn Off of GTO	2-22
2.4.5	I-V Characteristics of GTO	2-23
2.4.6	Other Important Characteristics of GTO	2-23
2.4.7	Advantages of GTO over SCR	2-23
2.4.8	Advantages of GTO Over BJT	2-23
2.4.9	Difference between Gating Characteristics of GTO and SCR	2-24
2.4.10	Applications of GTO	2-24
2.5	Ideal Switch Characteristics	2-24
2.5.1	Triggering Devices	2-25
2.6	Silicon Controlled Switch (SCS)	2-25
2.7	Light Activated SCR (LASCR)	2-27
2.7.1	Equivalent Circuit of LASCR	2-28
2.7.2	V-I Characteristics of LASCR	2-28
2.7.3	Advantages of LASCR	2-29
2.7.4	Applications of LASCR	2-29



2.8	DIAC .....	2-29
2.8.1	Construction of Diac .....	2-29
2.8.2	I-V Characteristics of a Diac .....	2-30
2.8.3	DIAC Applications .....	2-31
2.8.4	Disadvantages of DIAC .....	2-31
2.9	Unijunction Transistor (UJT) .....	2-31
2.9.1	Construction .....	2-31
2.9.2	Equivalent Circuit of UJT .....	2-32
2.9.3	Intrinsic Standoff Ratio ( $\eta$ ) .....	2-32
2.9.4	Operation of UJT .....	2-32
2.9.5	UJT Characteristics .....	2-33
2.10	Programmable Unijunction Transistor (PUT) .....	2-33
2.11	Comparisons .....	2-36
2.11.1	Comparison of SCR and Triac .....	2-36
2.11.2	Comparison of Diac and Triac .....	2-36
2.11.3	Comparison of Power Devices .....	2-37
2.11.4	Comparison of UJT and PUT .....	2-37
2.11.5	Comparison of SCR and DIAC .....	2-38
2.11.6	Comparison of GTO and IGBT .....	2-38
2.11.7	Comparison of UJT and DIAC .....	2-39
2.12	Protection Circuits .....	2-40
2.13	Overcurrent Fault Condition .....	2-40
2.14	Overcurrent Protections .....	2-40
2.14.1	Overcurrent Protection using Fuses .....	2-40
2.14.2	Semiconductor Fuses .....	2-41
2.14.3	Crowbar Circuit (Overcurrent / Overvoltage Protection) .....	2-43
2.14.4	Auto Current Limiting .....	2-44
2.15	Supply and Load Side Voltage Transients .....	2-44
2.15.1	Supply Side Voltage Transients .....	2-44
2.15.2	Load Transients .....	2-45
2.16	Protection Against Switching Voltage Transients .....	2-45
2.16.1	Over Voltage Conditions .....	2-45



2.16.2	Selenium Diodes (Protection Against Transient Overvoltage) .....	2-45
2.16.3	Metal Oxide Varistors (MOVs) .....	2-46
2.17	dv/dt and di/dt Protection .....	2-47
2.17.1	di/dt Protection (Turn on Snubber) .....	2-47
2.17.2	dv/dt Protection (Turn off Snubber) .....	2-48
2.18	Different Cooling Methods for Power Devices .....	2-49
2.19	Different Mounting Techniques .....	2-51
2.19.1	Thyristor Mounting Techniques .....	2-51
2.20	MSBTE Questions and Answers .....	2-54
2.21	I-Scheme Questions and Answers .....	2-56
	• <b>Review Questions</b> .....	<b>2-52</b>

<b>Unit-III</b>
-----------------

**Chapter 3 : Turn On Methods of SCR****3-1 to 3-28**

**Syllabus :** SCR Turn on methods : High voltage thermal triggering, Illumination triggering, dv/dt triggering, Gate triggering. Gate trigger circuits : Resistance and Resistance, Capacitance circuits. SCR triggering using UJT, PUT : Relaxation oscillator and synchronized, UJT circuit. Pulse transformer and opto-coupler based triggering.

3.1	Introduction to Turn On Methods .....	3-2
3.1.1	Delay Angle or Firing Angle or Phase Angle ( $\alpha$ ).....	3-2
3.2	Turn ON Methods .....	3-2
3.2.1	By Raising the Temperature (Thermal Triggering) .....	3-3
3.2.2	By Focusing Light (Illumination Triggering) .....	3-3
3.2.3	Forward Voltage Triggering .....	3-3
3.2.4	dv/dt Triggering .....	3-4
3.2.5	Gate Triggering .....	3-5
3.3	Dynamic Characteristics of SCR .....	3-5
3.3.1	Turn On Characteristics of SCR .....	3-6
3.4	Various Losses in Power Devices .....	3-7
3.4.1	Static Losses .....	3-7
3.4.2	Switching Losses (Dynamic Losses) .....	3-8
3.5	SCR Gate Characteristics .....	3-8
3.5.1	Types of Gate Triggering .....	3-9



3.5.2	Pulsed Triggering of SCR .....	3-10
3.5.3	Requirements of Gate Drive for SCR .....	3-11
3.6	Gate Triggering Circuits .....	3-11
3.6.1	General Block Diagram of Thyristor Gate Trigger Circuit .....	3-11
3.6.2	Resistance Trigger Circuit (Simple Resistor Triggering) .....	3-12
3.6.3	Half Wave RC (Capacitance) Firing Circuit .....	3-14
3.6.4	Full Wave RC (Capacitance) Firing Circuit .....	3-15
3.6.5	Basic UJT Relaxation Oscillator .....	3-16
3.6.6	SCR Triggering using UJT .....	3-17
3.6.7	Pulse Transformers .....	3-18
3.6.8	Synchronized UJT Triggering Circuit.....	3-19
3.6.9	Comparison of Triggering Circuits .....	3-22
3.6.10	SCR Triggering using PUT (PUT Relaxation Oscillator) .....	3-22
3.7	Isolation Circuits using Opto Coupler .....	3-25
3.7.1	Opto Couplers / Isolators .....	3-25
3.7.2	LED-phototransistor Opto Coupler .....	3-25
3.7.3	Opto Coupler Based Triggering.....	3-26
3.8	MSBTE Questions and Answers .....	3-28
3.9	I-Scheme Questions and Answers .....	3-28
	• <b>Review Questions</b> .....	<b>3-27</b>

<b>Unit-III</b>
-----------------

**Chapter 4 : Turn Off Methods of SCR****4-1 to 4-23**

**Syllabus** : SCR turn off methods : Class A - Series resonant commutation circuit, Class B - Shunt resonant commutation circuit, Class C - Complementary Symmetry commutation circuit. Class – D - Auxiliary commutation, Class E - External pulse commutation, Class F – Line or natural commutation.

4.1	Introduction to Turn Off Methods of Thyristors .....	4-2
4.1.1	Turn Off Process of SCR .....	4-2
4.1.2	Turn Off Characteristics (Dynamic Turn off Characteristics) of SCR .....	4-2
4.1.3	Turn Off Time ( $t_q$ ) .....	4-3
4.2	Commutation .....	4-4



4.3	Commutation Techniques (SCR Turn off Methods) .....	4-5
4.3.1	Natural Commutation .....	4-5
4.3.2	Forced Commutation .....	4-6
4.3.3	Conditions for Successful Commutation .....	4-6
4.4	Classification of Forced Commutation Methods .....	4-6
4.5	Self Commutation by Resonating the Load (Class A) .....	4-7
4.5.1	Load in Parallel with Capacitor .....	4-7
4.5.2	Load in Series with the SCR .....	4-8
4.5.3	Drawbacks of Self Commutation Technique .....	4-9
4.6	Class B - Self Commutated by an LC Circuit .....	4-9
4.7	Complementary Voltage Commutation (Class C Commutation) .....	4-11
4.7.1	Operation of the Circuit .....	4-12
4.7.2	Value of the Commutating Capacitor C .....	4-14
4.7.3	Modified Complementary Commutated Circuit .....	4-14
4.8	Auxiliary Voltage Commutation (Class D Commutation) .....	4-16
4.8.1	Operation of the Circuit .....	4-17
4.9	Class E - External Pulse Source for Commutation .....	4-19
4.10	Class F - Commutation (Line Commutation) .....	4-20
4.11	Comparisons .....	4-20
4.11.1	Comparison between Natural and Forced Commutation .....	4-20
4.11.2	Comparison between Voltage Commutation and Current Commutation .....	4-20
4.11.3	Comparison of Self and Class D Commutation .....	4-21
4.12	MSBTE Questions and Answers .....	4-22
4.13	I-Scheme Questions and Answers .....	4-22
	• <b>Review Questions</b> .....	<b>4-21</b>

**Unit-IV****Chapter 5 : Phase Controlled Rectifiers****5-1 to 5-55**

**Syllabus** : Phase control : Firing angle, Conduction angle, Single phase half controlled, Full controlled and midpoint controlled rectifier with R, RL load : Circuit diagram, Working, Input-Output waveforms, Equations for DC output and effect of freewheeling diode, Different configurations of bridge controlled rectifiers : Full bridge, half bridge with common anode, Common cathode, SCRs in one arm and diodes in another arm.





5.1	Introduction to Phase Controlled Rectifiers.....	5-2
5.1.1	Principle of Phase Angle Control Firing Angle .....	5-2
5.2	Classification of Controlled Rectifiers .....	5-3
5.3	Single Phase Half Wave Controlled Rectifier (HWCR) .....	5-4
5.3.1	Operation with Resistive Load .....	5-4
5.3.2	Analysis of HWCR with Resistive Load .....	5-5
5.3.3	Operation of HWCR with Inductive (RL) Load .....	5-7
5.3.4	Use of Freewheeling Diode in Controlled Rectifiers .....	5-9
5.3.5	Effect of Freewheeling Diode (With a Level Load) .....	5-9
5.3.6	Average Output Voltage of HWCR with RL Load .....	5-11
5.3.7	Rectifier Operation (Single Quadrant Operation) .....	5-12
5.3.8	Drawbacks of HWCR .....	5-12
5.4	Semiconverter or Half Controlled Bridge Rectifier (Full Wave) .....	5-12
5.4.1	Operation with Highly Inductive (RL) Load (For Symmetrical Configuration) .....	5-13
5.4.2	Variation of Average Load Voltage with $\alpha$ .....	5-16
5.4.3	Single Quadrant Operation .....	5-17
5.4.4	Half Controlled Converter with Freewheeling Diode (RL load) .....	5-17
5.4.5	Operation with the Resistive Load (Symmetrical Configuration) .....	5-21
5.4.6	Asymmetrical Configuration Operation (Half Controlled Converter) .....	5-24
5.4.7	Comparison between Configurations of Semiconverter .....	5-25
5.4.8	Advantages of Semiconverters .....	5-26
5.4.9	Disadvantages of Semiconverters .....	5-26
5.4.10	Application .....	5-27
5.5	Single Phase Full Wave Controlled Rectifier .....	5-27
5.5.1	Mid Point Configuration ( $M_2$ Configuration) .....	5-28
5.5.2	Operation with Resistive Load .....	5-28
5.5.3	Operation with Highly Inductive Load .....	5-30
5.6	Full Converter or Bridge Rectifier [ $B_2$ Connection] .....	5-35
5.6.1	Operation of Full Converter with RL (Inductive) Load .....	5-35
5.6.2	Two Quadrant Operation of Full Converter (Rectifier and Inverter Modes) .....	5-39
5.6.3	Operation of Full Converter with Resistive Load .....	5-41



5.7	Full Converter using Freewheeling Diode .....	5-45
5.7.1	Advantages of Full Converter .....	5-47
5.7.2	Disadvantages of Full Converter .....	5-48
5.7.3	Application .....	5-48
5.7.4	Comparison of Semiconverter and Full Converter .....	5-48
5.7.5	Applications of Controlled Rectifiers .....	5-48
5.7.6	Comparison of Controlled H.W.R. and Controlled F.W.R. ....	5-48
5.7.7	Comparison of Controlled and Uncontrolled Rectifiers .....	5-49
5.8	I-Scheme Solved Examples.....	5-51
5.9	MSBTE Questions and Answers .....	5-51
5.10	I-Scheme Questions and Answers .....	5-54
	• <b>Review Questions</b> .....	<b>5-50</b>

<b>Unit-V</b>
---------------

**Chapter 6 : Industrial Control Circuits****6-1 to 6-25**

<p><b>Syllabus</b> : Applications : Burglar's alarm system, Battery charger using SCR, Emergency light system, Temperature controller using SCR and Illumination control / Fan speed control using TRIAC. SMPS, UPS : Offline and online, SCR based AC and DC circuit breakers.</p>
---

6.1	Introduction.....	6-2
6.2	Burglar's Alarm .....	6-2
6.3	Simple Battery Charger Using SCR .....	6-2
6.3.1	Battery Charging Regulator .....	6-3
6.4	Basic Emergency Lighting System .....	6-4
6.5	Triac Control using Diac (AC Phase Control) .....	6-5
6.5.1	Illumination Control using Triac .....	6-7
6.5.2	Fan Speed Control using Triac .....	6-8
6.6	SCR Based Temperature Controller .....	6-8
6.7	Switch Mode Power Supply (SMPS) Block Diagram .....	6-9
6.7.1	Complete Switched Mode Regulator .....	6-11
6.7.2	Classification of SMPS .....	6-12
6.7.3	Types of Non-isolated Switching Regulators .....	6-12
6.8	Advantages and Disadvantages of SMPS .....	6-12



---

6.9	Applications of SMPS .....	6-13
6.10	UPS .....	6-13
6.10.1	Need of UPS .....	6-13
6.10.2	Types of UPS .....	6-14
6.11	On Line UPS (Inverter Preferred) or (Continuous) .....	6-14
6.12	Off Line UPS (Line Preferred) or Transfer UPS System .....	6-16
6.12.1	Comparison of UPS Systems .....	6-18
6.12.2	Comparison of Linear and Switching Mode Regulators .....	6-18
6.13	Applications of UPS .....	6-19
6.14	Static Switches .....	6-19
6.14.1	Static Switch using Inverse Parallel SCRs .....	6-19
6.14.2	Static Switch using Triac .....	6-20
6.14.3	Static Circuit Breaker .....	6-21
6.14.4	Static DC Circuit Breaker .....	6-22
6.14.5	Static AC Circuit Breaker .....	6-22
6.15	MSBTE Questions and Answers .....	6-24
6.16	I-Scheme Questions and Answers .....	6-24
•	<b>Review Questions</b> .....	<b>6-23</b>

□□□