

Unit – I

Chapter 1 : Magnetic Circuits 1-1 to 1-28

Syllabus : Magnetic flux, Flux density, Magneto motive force, Magnetic field strength, Permeability, Reluctance, Electric and magnetic circuits, Series and parallel magnetic circuits, Faraday’s laws of electromagnetic induction, Fleming’s right hand rule, Lenz’s law, Dynamically and statically induced emf, Self and mutual inductance, B-H curve and hysteresis, Hysteresis loop and hysteresis loss.

1.1	Introduction	1-2
1.1.1	Magnet	1-2
1.1.2	Electromagnets	1-2
1.2	Important Definitions Related to Magnetism	1-2
1.2.1	Magnetic Field	1-2
1.2.2	Magnetic Flux ϕ	1-2
1.2.3	Magnetic Flux Density (B)	1-2
1.2.4	Magnetic Field Strength (H)	1-2
1.3	Permeability	1-3
1.3.1	Absolute Permeability (μ)	1-3
1.3.2	Permeability of Free Space or Vacuum (μ_0)	1-3
1.3.3	Relative Permeability (μ_r)	1-3
1.4	Definitions Concerning Magnetic Circuits	1-4
1.4.1	Magnetomotive Force (MMF)	1-4
1.4.2	Reluctance (S)	1-4
1.4.3	Permeance	1-4
1.5	Magnetic Circuit	1-6
1.5.1	Comparisons of Magnetic and Electrical Circuits	1-6
1.6	Composite Magnetic Circuits	1-7
1.6.1	Series Magnetic Circuit	1-7
1.6.2	A Series Magnetic Circuit with Air Gap	1-8
1.6.3	Solved Examples	1-9
1.7	Parallel Magnetic Circuit	1-11
1.7.1	Expression for the Total MMF (Ampere-Turns)	1-12

1.7.2	Expression for the Reluctance of a Parallel Magnetic Circuit	1-12
1.7.3	Parallel Magnetic Circuit with Air Gap	1-12
1.8	Electromagnetic Induction	1-13
1.8.1	Faraday's Laws of Electromagnetic Induction	1-13
1.8.2	Direction of Induced E.M.F.	1-14
1.9	Nature of the Induced E.M.F.	1-14
1.10	Dynamically Induced E.M.F.	1-15
1.10.1	Magnitude of Dynamically Induced E.M.F.	1-15
1.10.2	Direction of Dynamically Induced EMF ..	1-16
1.11	Statically Induced E.M.F.	1-16
1.11.1	Self Induced E.M.F.	1-16
1.11.2	Self Inductance	1-17
1.11.3	Expression for the Coefficient of Self Inductance (L)	1-17
1.11.4	Mutually Induced E.M.F.	1-17
1.11.5	Mutual Inductance (M)	1-18
1.11.6	Alternate Way of Defining the Mutual Inductance	1-18
1.11.7	Expression for Mutual Inductance	1-18
1.11.8	Coefficient of Coupling (K)	1-18
1.11.9	Comparison of Statically and Dynamically Induced E.M.F.	1-19
1.12	B-H Curve or Magnetization Curve	1-22
1.12.1	Magnetic Hysteresis and Hysteresis Loop	1-23
1.12.2	Hysteresis Loss	1-24
1.12.3	Magnetization Curves for Magnetic and Non-magnetic Materials	1-24
1.12.4	Factors Affecting the Hysteresis Loss	1-25
1.13	MSBTE Questions and Answers	1-26
1.14	I-Scheme Solved Examples	1-28
1.15	I-Scheme Questions and Answers	1-28
	• Review Questions	1-25

Unit – II

Chapter 2 : AC Fundamentals 2-1 to 2-54

Syllabus : AC and DC quantity, Advantages of AC over DC, Single phase AC, Sinusoidal AC wave : Instantaneous value, Cycle, Amplitude, Time period, Frequency, Angular frequency, RMS value, Average value for sinusoidal waveform, Form factor, Peak factor, Vector representation of sinusoidal AC quantity, Phase angle, Phase difference, Concept of lagging and leading by waveforms. Mathematical equations and phasors, Pure resistance, Inductance and capacitance in AC circuit. R-L and R-C series circuits, Impedance and impedance triangle, Power factor and its significance, Power-active, Reactive and apparent, Power triangle.

2.1	Difference between AC and DC	2-2
2.1.1	Comparison of AC and DC	2-2
2.1.2	Advantage of AC Over DC	2-3
2.2	Various Types of AC Waveforms	2-3
2.2.1	Definition of Waveform	2-3
2.2.2	Types of AC Waveforms	2-3
2.2.3	Waveform of Sinusoidal AC	2-3
2.2.4	Graphical and Mathematical Representation of Sinusoidal AC Quantities	2-3
2.3	Generation of Single Phase AC by Elementary Alternator	2-4
2.3.1	Single Turn Alternator (Elementary Alternator)	2-4
2.4	Definitions	2-6
2.4.1	Waveform	2-6
2.4.2	Instantaneous Value	2-6
2.4.3	Cycle	2-6
2.4.4	Time Period or Periodic Time (T)	2-6
2.4.5	Frequency	2-7
2.4.6	Amplitude	2-7
2.4.7	Angular Velocity (ω)	2-8
2.5	Peak and Peak to Peak Voltage	2-8
2.6	Effective or R.M.S. Value	2-8

2.7	Average Value	2-9
2.7.1	Methods to Calculate the Average Value	2-9
2.8	Form Factor	2-10
2.9	Crest Factor or Peak Factor (K_p)	2-10
2.10	Phasor Representation of an Alternative Quantity	2-15
2.11	Phase of an Alternating Quantity	2-16
2.11.1	Phase Angle	2-16
2.11.2	Phase Difference	2-16
2.11.3	Leading and Lagging Phase Difference	2-16
2.12	Mathematical Representation of Phasor	2-19
2.12.1	Polar Representation	2-19
2.12.2	Rectangular Representation	2-19
2.12.3	Conversion from Polar to Rectangular ...	2-19
2.12.4	Rectangular to Polar Conversion	2-19
2.13	Addition and Subtraction of Phasors (Using Rectangular Form)	2-19
2.13.1	Multiplication and Division of Phasors (Using Polar Form)	2-20
2.14	Behavior of Single Phase AC Circuits	2-20
2.14.1	Impedance (Z)	2-20
2.15	AC Circuit Containing Resistance Only	2-21
2.15.1	Analysis of the Purely Resistive AC Circuit	2-21
2.15.2	Voltage and Current Waveforms and Equations	2-21
2.15.3	Phasor Diagram	2-22
2.15.4	Impedance of the Purely Resistive Circuit	2-22
2.15.5	Average Power (P_{av})	2-22
2.15.6	Energy in Purely Resistive Circuit	2-22
2.16	AC Circuit Containing Inductance Only	2-24
2.16.1	Equations for Current i and Voltage V ...	2-24
2.16.2	Waveforms and Phasor Diagram	2-24



2.16.3	Power in a Purely Inductive Circuit2-25	2.21.9	Reactive Power or Imaginary Power (Q)2-36
2.16.4	Impedance of a Purely Inductive Circuit2-25	2.21.10	Power Factor2-36
2.17	AC Circuit Containing Capacitance Only2-26	2.21.11	Q-factor2-36
2.17.1	Equation for Voltage and Current2-26	2.22	The R-C Series Circuit2-40
2.17.2	Current and Voltage Waveforms and Phasor Diagram2-27	2.22.1	Phasor Diagram2-40
2.17.3	Power in Purely a Capacitive AC Circuit2-27	2.22.2	Impedance of RC Series Circuit2-40
2.17.4	Impedance of a Purely Capacitive Circuit2-27	2.22.3	Impedance Triangle (Series R-C circuit)2-41
2.18	Concept of Impedance and Impedance Triangle2-29	2.22.4	Voltage and Current Waveforms2-41
2.18.1	Impedance (Z)2-29	2.22.5	Average Power in Series R-C Circuit2-41
2.18.2	Concept of Impedance Triangle2-29	2.22.6	Power Triangle for R-C Series Circuit2-42
2.19	Types of Power and Power Factor2-30	2.22.7	Various Powers and Power Factor2-42
2.19.1	Apparent Power (S)2-30	2.22.8	Q-Factor2-42
2.19.2	Real Power or True Power or Active Power (P)2-30	2.23	MSBTE Questions and Answers2-45
2.19.3	Reactive Power or Imaginary Power (Q)2-31	2.24	I-Scheme Solved Examples2-52
2.19.4	Power Factor2-31	2.25	I-Scheme Questions and Answers2-54
2.19.5	Causes and Effects of Low Power Factor2-32		• Review Questions.....2-44
2.19.6	Power Triangle2-33	Unit – III	
2.20	AC Circuits with Series Elements2-34	Chapter 3 : Polyphase AC Circuits 3-1 to 3-28	
2.21	The Series R-L Circuit2-34	Syllabus : 3 phase system over 1 phase system, 3-phase emf generation and its waveform, Phase sequence and balanced and unbalanced load, Phase and line current, Phase and line voltage in star connected and delta connected balanced system, Current, Power, Power factor in three phase balanced system, star and delta connections.	
2.21.1	Phasor Diagram2-34	3.1	Introduction to Polyphase AC Circuits3-2
2.21.2	Impedance of L-R Series Circuit2-35	3.1.1	Why to use a Polyphase System ?3-2
2.21.3	Impedance Triangle2-35	3.1.2	How Many Phases ?3-2
2.21.4	Voltage and Current Waveforms2-35	3.1.3	Three Phase Supply Waveforms3-2
2.21.5	Average Power in Series L-R Circuit2-36	3.2	Advantages of Three Phase Systems over Single Phase System3-2
2.21.6	Power Triangle for L-R Series Circuit2-36	3.2.1	Comparison of Single Phase and Three Phase Systems3-3
2.21.7	Apparent Power (S)2-36	3.3	Principle of Three Phase Emf Generation and Its Waveforms3-3
2.21.8	Real Power or True Power or Active Power (P)2-36		



3.3.1	Mathematical Representation of the Three Phase Voltages	3-4	3.10	MSBTE Questions and Answers	3-21
3.3.2	Concept of Symmetrical or Balanced System	3-4	3.11	I-Scheme Solved Examples	3-26
3.3.3	Concept of Phase Sequence	3-4	3.12	I-Scheme Questions and Answers	3-27
3.4	Three Phase Supply Connections	3-5		• Review Questions	3-21
3.4.1	Star Connection (Wye Connection)	3-5	Unit – IV		
3.4.2	Delta Connection	3-5	<hr/>		
3.5	Types of Loads	3-6	Chapter 4 : Transformer 4-1 to 4-28		
3.5.1	Balanced or Unbalanced Load	3-6	Syllabus : Transformer : Working principle, Emf equation, Voltage ratio, Current ratio and Transformation ratio, Losses. Auto transformer - Comparison with two winding transformer, Applications.		
3.6	Relations between Voltages and Current for a Balanced Star Load	3-7	4.1	Introduction	4-2
3.6.1	Line Voltages and Phase Voltages	3-7	4.1.1	Types of Transformer	4-2
3.6.2	Line and Phase Voltages for Star Connection	3-7	4.1.2	Principle of Operation	4-2
3.6.3	Relation between Line and Phase Voltages for Star Connected Supply	3-7	4.2	Construction of a Transformer	4-3
3.6.4	Relation between Phase and Line Current	3-8	4.2.1	Laminated Steel Core	4-4
3.6.5	Equations for Three Phase Power	3-9	4.2.2	Different Cross-Sections for Transformer Limbs	4-4
3.6.6	Power Factor for a Star Load	3-9	4.2.3	Windings of the Transformer	4-4
3.6.7	The Complete Phasor Diagram	3-9	4.2.4	Transformer Tank	4-5
3.7	Voltage, Current and Power Relation in a Balanced Delta Load	3-14	4.3	Transformer Types on the Basis of Construction ...	4-6
3.7.1	Line Voltages and Phase Voltages for Delta Connected Supply	3-14	4.3.1	Core Type Transformer	4-6
3.7.2	Phase and Line Voltages in Delta Connections	3-15	4.3.2	Shell Type Transformer	4-6
3.7.3	Line Current and Phase Current for Delta Connection	3-15	4.4	EMF Equation of a Transformer	4-7
3.7.4	Power Relations	3-16	4.5	Voltage and Current Ratios of a Transformer	4-8
3.7.5	Power Factor	3-16	4.5.1	Voltage Ratios of the Transformer with Load	4-8
3.7.6	The Complete Phasor Diagram	3-16	4.5.2	Voltage Ratios for the Transformer Without Load	4-9
3.8	Different Types of Power and their Relations	3-17	4.5.3	Transformation Ratio (K)	4-9
3.8.1	Power Triangle	3-17	4.5.4	Turns Ratio of the Transformer	4-10
3.8.2	Power Factor	3-17	4.5.5	Types of Transformers Based on the Value of K	4-10
3.9	Comparison of Star and Delta Systems	3-20	4.5.6	Current Ratios	4-10
			4.6	Ratings of Transformer	4-12
			4.7	Losses in a Transformer	4-14
			4.7.1	Copper Loss (P_{cu})	4-15



4.7.2	Iron Loss (P_i)	4-15	5.5.4	Field Winding ($F_1 - F_2$)	5-3
4.7.3	Hysteresis Losses	4-15	5.5.5	Armature Core	5-4
4.7.4	Eddy Current Losses	4-15	5.5.6	Armature Winding	5-4
4.8	Definitions of Efficiency and Regulation	4-16	5.5.7	Commutator	5-4
4.8.1	Efficiency (η)	4-16	5.5.8	Brushes	5-5
4.8.2	Condition for Maximum Efficiency	4-16	5.5.9	Types of Armature Windings	5-5
4.8.3	Load at Maximum Efficiency	4-17	5.5.10	Direction of Rotation of the Motor	5-5
4.8.4	Voltage Regulation of a Transformer	4-17	5.6	Back EMF	5-6
4.9	Applications of Two Winding Transformer	4-18	5.7	Types of DC Motors	5-6
4.10	Autotransformer	4-19	5.8	DC Shunt Motor	5-6
4.10.1	Autotransformer as Step Down Transformer	4-19	5.9	DC Series Motor	5-7
4.10.2	Autotransformer as a Step Up Transformer	4-19	5.9.1	Why Series Motor is Never Started on No Load ?	5-7
4.10.3	Advantages of Autotransformer	4-20	5.10	DC Compound Motors	5-7
4.10.4	Disadvantages of an Autotransformer	4-20	5.10.1	Long Shunt Compound Motor	5-7
4.10.5	Applications of an Autotransformer	4-20	5.10.2	Short Shunt Compound DC Motor	5-8
4.10.6	Comparison of Two Winding and Autotransformer	4-20	5.10.3	Cumulative Compound DC Motors	5-8
4.11	MSBTE Questions and Answers	4-22	5.10.4	Differential Compound DC Motors	5-8
4.12	I-Scheme Solved Examples	4-26	5.11	DC Motor Applications	5-8
4.13	I-Scheme Questions and Answers	4-28	5.11.1	Shunt Motor Applications	5-8
	• Review Questions.....	4-21	5.11.2	Series Motor Applications	5-9

Unit – IV

Chapter 5 : DC Motors **5-1 to 5-10**

Syllabus : DC motor construction - Parts its function and material used, DC motor - Principle of operation, Types of DC motors, Schematic diagram, Applications of dc shunt, Series and compound motors.

5.1	Introduction	5-2
5.2	DC Machines	5-2
5.3	Windings in a DC Machine	5-2
5.4	Principle of Operation of a DC Motor	5-2
5.5	Construction of a DC Machine	5-3
5.5.1	Important Parts of a DC Machine	5-3
5.5.2	Yoke	5-3
5.5.3	Poles, Pole Shoe and Pole Core	5-3

5.5.4	Field Winding ($F_1 - F_2$)	5-3
5.5.5	Armature Core	5-4
5.5.6	Armature Winding	5-4
5.5.7	Commutator	5-4
5.5.8	Brushes	5-5
5.5.9	Types of Armature Windings	5-5
5.5.10	Direction of Rotation of the Motor	5-5
5.6	Back EMF	5-6
5.7	Types of DC Motors	5-6
5.8	DC Shunt Motor	5-6
5.9	DC Series Motor	5-7
5.9.1	Why Series Motor is Never Started on No Load ?	5-7
5.10	DC Compound Motors	5-7
5.10.1	Long Shunt Compound Motor	5-7
5.10.2	Short Shunt Compound DC Motor	5-8
5.10.3	Cumulative Compound DC Motors	5-8
5.10.4	Differential Compound DC Motors	5-8
5.11	DC Motor Applications	5-8
5.11.1	Shunt Motor Applications	5-8
5.11.2	Series Motor Applications	5-9
5.11.3	Cumulative Compound Motor Applications	5-9
5.11.4	Differential Compound Motors Applications	5-9
5.12	I-Scheme Questions and Answers	5-9
	• Review Questions.....	5-9

Unit – V

Chapter 6 : Fractional Horse Power (FHP) Motors

6-1 to 6-18

Syllabus : FHP : Schematic representation, Principle of operation and application of : Split phase induction motor, Capacitor start induction run, Capacitor start capacitor run and permanent capacitor motor, Shaded pole motors. Universal motor : Principle of operation, Reversal of rotation and Applications. Stepper motor : Types, Principle of working and applications.

6.1	Introduction	6-2
-----	--------------------	-----



6.2	Single Phase Induction Motors 6-2	6.9	Classification of Stepper Motors 6-11
6.2.1	Construction of Single Phase Induction Motors 6-2	6.10	Various Types of Stepper Motors 6-11
6.2.2	Double Revolving Field Theory 6-2	6.10.1	Variable Reluctance (V.R.) Motor 6-11
6.2.3	Torque Speed Characteristics of Single Phase Induction Motor 6-3	6.10.2	Permanent Magnet Step Motors 6-12
6.2.4	Split Phasing Principle of Starting 6-3	6.10.3	Hybrid Step Motors 6-13
6.2.5	Types of Single Phase Induction Motors 6-4	6.10.4	Applications of Stepper Motor 6-14
6.3	Resistance Split Phase Induction Motor 6-4	6.10.5	Limitations of Stepper Motor 6-14
6.3.1	Principle of Operation 6-4	6.11	MSBTE Questions and Answers 6-15
6.3.2	Applications of Split Phase Induction Motor 6-5	6.12	I-Scheme Questions and Answers 6-17
6.4	Capacitor Start Induction Motors 6-5		• Review Questions..... 6-14
6.4.1	Capacitor Start Capacitor Run Motor 6-5	Unit – VI	
6.4.2	Applications 6-6	Chapter 7 : Protective Devices and Switchgear	
6.4.3	Comparison between Resistance Split Phase and Capacitor Start Single Phase I.M 6-6	7-1 to 7-18	
6.5	Permanent Capacitor Motor 6-6	Syllabus : Fuse : Operation, Types, Switch fuse unit and Fuse switch unit : Differences, MCB, MCCB and ELCB : Operation and general specifications. Earthing : Importance of earthing, Factors affecting earthing, Methods of reducing earth resistance : I.E. rules relevant to earthing.	
6.5.1	Advantages 6-7	7.1	Accessories of Electrical Installation 7-2
6.5.2	Limitations / Disadvantages 6-7	7.1.1	Fuse 7-2
6.5.3	Applications 6-7	7.2	Fuses 7-2
6.6	Shaded Pole Induction Motors 6-7	7.2.1	Need of Fuses 7-2
6.6.1	Advantages 6-8	7.2.2	Types of Fuses 7-2
6.6.2	Disadvantages 6-8	7.2.3	Fuse Characteristics 7-4
6.6.3	Applications 6-8	7.2.4	Basic Terms Related to Fuse 7-4
6.7	Universal Motor 6-8	7.3	Switch Fuse Unit (SFU) and Fuse Switch Unit (FSU) 7-5
6.7.1	Types of Universal Motors 6-9	7.3.1	Switch Fuse Unit (SFU) 7-5
6.7.2	Uncompensated Universal Motor 6-9	7.3.2	Fuse Switch Unit (FSU) 7-5
6.7.3	Compensated Universal Motor 6-9	7.3.3	Comparison of SFU and FSU 7-6
6.7.4	Advantages of Universal Motors 6-10	7.4	Miniature Circuit Breaker (MCB) 7-6
6.7.5	Disadvantages of Universal Motors 6-10	7.4.1	Comparison of Fuse and MCB 7-7
6.7.6	Applications of Universal Motors 6-10	7.4.2	MCCB (Moulded Case Circuit Breaker) 7-7
6.8	Stepper Motor 6-10	7.4.3	E.L.C.B. (Earth Leakage Circuit Breaker) 7-7
6.8.1	Advantages of Stepper Motors 6-11	7.5	Earthing 7-9



7.5.1	Necessity of Earthing	7-10	7.6.2	Plate Earthing	7-13
7.5.2	Important Points Regarding Earthing of Electrical Installation	7-11	7.6.3	Earthing of Domestic Appliances	7-14
7.5.3	Factors Affecting the Earth Resistance ...	7-11	7.6.4	IE Rules Relevant to Earthing	7-14
7.6	Different Types of Earthing	7-12	7.7	MSBTE Questions and Answers	7-15
7.6.1	Pipe Earthing	7-12	7.8	I-Scheme Questions and Answers	7-17
				• Review Questions	7-14

□□□