

Power Electronic Applications

(Code : 22527)

(Elective)

Maharashtra State Board of Technical Education (MSBTE)

Semester V – Electrical Engineering Group (EE/EP/EU)

Strictly as per new revised 'I' Scheme w.e.f. academic year 2019-2020

J. S. Katre

M.E. (Electronics and Telecommunication)
Formerly, Assistant Professor
Department of Electronics Engineering
Vishwakarma Institute of Technology (V.I.T.), Pune.
Maharashtra, India

 **Tech Knowledge**TM
Publications



Power Electronic Applications (Code : 22527)

Third Year Diploma : Semester V (MSBTE), [Electrical Engineering Group (EE/EP/EU)]

J. S. Katre

Copyright © Author. All rights reserved. No part of this publication may be reproduced, copied, or stored in a retrieval system, distributed or transmitted in any form or by any means, including photocopy, recording, or other electronic or mechanical methods, without the prior written permission of the publisher.

This book is sold subject to the condition that it shall not, by the way of trade or otherwise, be lent, resold, hired out, or otherwise circulated without the publisher's prior written consent in any form of binding or cover other than which it is published and without a similar condition including this condition being imposed on the subsequent purchaser and without limiting the rights under copyright reserved above.

First Printed in India : July 1998

First Edition as per I-Scheme: June 2019 (**TechKnowledge Publications**)

Second Revised Edition : June 2022

This edition is for sale in India, Bangladesh, Bhutan, Maldives, Nepal, Pakistan, Sri Lanka and designated countries in South-East Asia. Sale and purchase of this book outside of these countries is unauthorized by the publisher.

ISBN : 978-93-89299-01-4

Published by :

TechKnowledge Publications

Head Office : B/5, First floor, Maniratna Complex, Taware Colony, Aranyeshwar Corner,

Pune - 411 009. Maharashtra State, India

Ph : 91-20-24221234, 91-20-24225678.


Email : info@techknowledgebooks.com,

Website : www.techknowledgebooks.com

[22527] (FID : MDO69) (Book Code : MDO69B)

(Book Code : MDO69B)

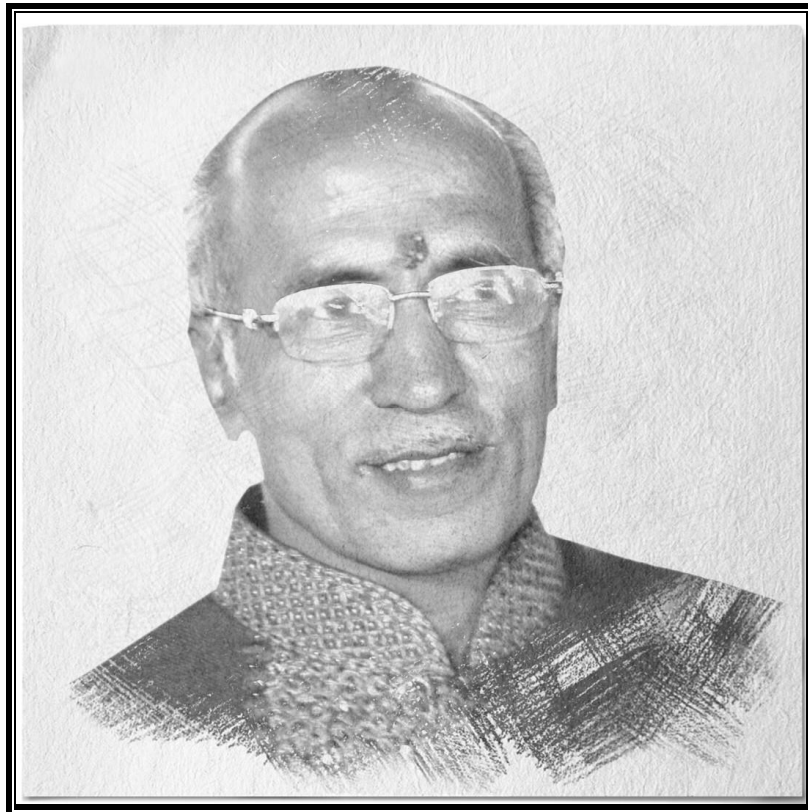*We dedicate this Publication soulfully and wholeheartedly,
in loving memory of our beloved founder director,
Late Shri. Pradeepji Lalchandji Lunawat,
who will always be an inspiration, a positive force and strong support
behind us.*



“My work is my prayer to God”

- Lt. Shri. Pradeepji L. Lunawat

*Soulful Tribute and Gratitude for all Your
Sacrifices, Hardwork and 40 years of Strong Vision...*

Syllabus...

Power Electronic Applications : Sem. V (Electrical Engineering Group (MSBTE))

Unit-I

1. Modern Power Devices :

Power MOSFET and IGBT : Construction, Working, Transfer characteristics, Output characteristics, and application. SCR construction, Working, Transfer characteristics, Output characteristics, and application.

SIT ; Construction, Working, VI characteristics, and application. MCT : Construction, Working, VI characteristics and application. FCT : Construction, Working, VI characteristics, and application. **(Refer Chapter 1)**

Unit-II

2. Chopper Circuits :

DC Choppers : Types, Control strategies of chopper single quadrant, Two quadrant, Four quadrant chopper (Circuit diagram, operation with waveforms), Morgan chopper : Circuit diagram, Operation with waveforms. Jones choppers : Circuit diagram, Operation with waveforms. **(Refer Chapter 2)**

Unit-III

3. Inverter Circuits :

Classification : Voltage-driven and current-driven inverter. Transistor inverter, SCR inverters : Single-phase parallel inverter, Single-phase series inverter, Single phase bridge inverter description with circuits and waveforms. Three-phase bridge inverter description with circuits and waveforms. McMurray half bridge and full bridge inverters description with circuits and waveforms. McMurray-Bedford inverter description with circuits and waveforms and applications. **(Refer Chapter 3)**

Unit-IV

4. Dual Converters and Cyclo-converters :

Dual converters : Principle and types. Circulatory current free mode, Circulatory current mode dual converters, Cyclo-converter : Principle and types. Single phase to single phase and three phase Cyclo-converter : Operation with circuit and waveforms. **(Refer Chapter 4)**

Unit-V

5. Industrial Applications of Power Devices :

Static circuit breaker (DC and AC). High frequency heating : Induction heating and dielectric heating control. Electric welding control. Battery charger control. Battery charger control. AC voltage stabilizer type : Servo, Solid state and relay. Static VAR compensation system. Closed loop speed control method for DC and AC servo motor. Simulation : Chopper, Inverter and Cyclo-converter circuits. **(Refer Chapter 5)**

□□□

**Unit – I****Chapter 1 : Modern Power Devices 1-1 to 1-24**

Syllabus : Power MOSFET and IGBT : Construction, Working, Transfer characteristics, Output characteristics, and application. SCR construction, Working, Transfer characteristics, Output characteristics and application. SIT : Construction, Working, V-I characteristics, and application. MCT : Construction, Working, V-I characteristics, and application. FCT : Construction, Working, V-I characteristics, and application.

1.1	Introduction to Power Electronics	1-2
1.1.1	Principle of Power Electronics	1-2
1.1.2	Application Areas of Power Electronics	1-2
1.2	Power Semiconductor Devices	1-2
1.2.1	General Requirements of Power Devices	1-3
1.3	Introduction to Thyristors Family Devices	1-3
1.3.1	Applications of Thyristors	1-3
1.3.2	Silicon Controlled Rectifier (SCR)	1-4
1.3.3	Important Features of SCR.....	1-4
1.3.4	Construction of SCR.....	1-4
1.3.5	I-V Characteristics (Static/Output Characteristics).....	1-5
1.3.6	Operation of SCR	1-7
1.3.7	Drawbacks of SCR.....	1-7
1.3.8	Advantages of SCR.....	1-8
1.3.9	Applications of SCR.....	1-8
1.4	Power MOSFET	1-8
1.4.1	Structure of a Power MOSFET	1-8
1.4.2	Simplified Structure of Power MOSFET	1-9
1.4.3	Principle of Operation	1-9
1.4.4	I-V Characteristics (Output Characteristics)	1-11
1.4.5	Transfer Characteristics of n-channel Enhancement Type MOSFET	1-12
1.5	Merits, Demerits and Applications of Power MOSFET	1-12

1.5.1	Merits of a Power MOSFET	1-12
1.5.2	Demerits of a Power MOSFET	1-12
1.5.3	Applications of Power MOSFET	1-13
1.6	Insulated Gate Bipolar Transistor (IGBT)	1-13
1.6.1	Features of IGBT	1-13
1.6.2	Basic Structure of IGBT	1-13
1.6.3	I-V Characteristics (Output Characteristics)	1-14
1.6.4	Principle of Operation of IGBT	1-15
1.6.5	Merits, Demerits and Applications of IGBT	1-15
1.7	Static Induction Thyristors (SIT)	1-16
1.8	MOS Controlled Thyristor (MCT)	1-17
1.8.1	Precaution	1-18
1.8.2	Important Features of MCT	1-18
1.8.3	Static (I-V) Characteristics	1-18
1.8.4	Switching Characteristics of MCT	1-18
1.8.5	Ratings of MCT	1-19
1.8.6	SOA of MCT	1-19
1.8.7	Advantages of MCT	1-19
1.8.8	Demerits	1-19
1.8.9	Applications of MCT	1-19
1.9	Field Controlled Thyristor (FCT)	1-20
1.10	Comparison of SCR, MOSFET and IGBT	1-21
1.11	I-Scheme Questions and Answers.....	1-24
	• Review Questions	1-22

Unit – II**Chapter 2 : Chopper Circuits 2-1 to 2-23**

Syllabus : DC choppers : Types, Control strategies of chopper. Single quadrant, Two quadrant, Four quadrant, Chopper (Circuit diagram, Operation with waveforms). Morgan chopper : Circuit diagram, Operation with waveforms. Jones choppers : Circuit diagram, Operation with waveforms.

2.1	Introduction	2-2
2.2	Types of Chopper	2-3
2.3	Control Strategies	2-3



2.3.1	Pulse Width Modulation (PWM) or TRC	2-3	3.2	Classification of Inverters	3-2
2.3.2	Constant Pulse Width Variable Frequency (Frequency Modulation)	2-4	3.2.1	Classification Based on the Nature of Source	3-2
2.3.3	Current Limit Control (CLC)	2-5	3.2.2	Classification Based on the Configuration of the Inverter	3-2
2.3.4	Variable Pulse Width and Frequency	2-5	3.2.3	Classification Based on the Nature of Output Waveform	3-3
2.4	Comparison between Different Control Strategies of a Chopper	2-5	3.2.4	Classification Based on Type of Commutation Circuit	3-3
2.5	Principle of Step Down Chopper	2-6	3.2.5	Classification Based on the Power Semiconductor Device Used	3-3
2.5.1	Average Output Voltage	2-6	3.2.6	Applications of Inverters	3-3
2.6	Single, Two and Four Quadrant Choppers	2-7	3.3	Basic Series Inverter (Self Commutated Inverter)	3-3
2.6.1	Single Quadrant Choppers (Type A and Type B)	2-7	3.3.1	Disadvantages / Limitations	3-5
2.6.2	Two Quadrant Choppers (Type C and Type D)	2-10	3.3.2	Improved Series Inverter [Type 1]	3-6
2.7	Four Quadrant Chopper (Type E Chopper)	2-14	3.3.3	Improved Series Inverter [Type 2]	3-6
2.8	Step Up Chopper	2-14	3.3.4	Applications of Series Inverter	3-8
2.8.1	Expression for the Output Voltage	2-15	3.3.5	Advantages of Series Inverter	3-8
2.8.2	Comparison of Step Up and Step Down Choppers	2-16	3.4	Parallel Inverter (with Purely Resistive Load)	3-8
2.9	Morgan Chopper	2-18	3.5	Parallel Inverter or Centre Tapped Inverter (with Inductive Load)	3-9
2.10	Jone's Chopper	2-19	3.5.1	Advantages of Parallel Inverter	3-11
2.11	Applications of a Chopper	2-21	3.5.2	Disadvantages	3-11
2.11.1	Features of Choppers	2-21	3.5.3	Comparison of Series and Parallel Inverters	3-12
2.12	MSBTE Questions and Answers	2-22	3.6	Half Bridge Inverter	3-12
2.13	I-Scheme Questions and Answers	2-22	3.6.1	Half Bridge Inverter with Inductive Load	3-13
	• Review Questions	2-21	3.6.2	Full Bridge Inverter	3-15

Unit – III

Chapter 3 : Inverter Circuits

3-1 to 3-41

Syllabus : Classification : Voltage-driven and current-driven inverter, Transistor inverter, SCR inverters: Single-phase parallel inverter, Single-phase series inverter, Single-phase bridge inverter description with circuits and waveforms. Three-phase bridge inverter description with circuits and waveforms. McMurry half bridge and full bridge inverters description with circuits and waveforms. McMurry-Bedford inverter description with circuits and waveforms and applications.

3.1	Introduction	3-2
-----	--------------------	-----

3.2.1	Classification Based on the Nature of Source	3-2
3.2.2	Classification Based on the Configuration of the Inverter	3-2
3.2.3	Classification Based on the Nature of Output Waveform	3-3
3.2.4	Classification Based on Type of Commutation Circuit	3-3
3.2.5	Classification Based on the Power Semiconductor Device Used	3-3
3.2.6	Applications of Inverters	3-3
3.3	Basic Series Inverter (Self Commutated Inverter)	3-3
3.3.1	Disadvantages / Limitations	3-5
3.3.2	Improved Series Inverter [Type 1]	3-6
3.3.3	Improved Series Inverter [Type 2]	3-6
3.3.4	Applications of Series Inverter	3-8
3.3.5	Advantages of Series Inverter	3-8
3.4	Parallel Inverter (with Purely Resistive Load)	3-8
3.5	Parallel Inverter or Centre Tapped Inverter (with Inductive Load)	3-9
3.5.1	Advantages of Parallel Inverter	3-11
3.5.2	Disadvantages	3-11
3.5.3	Comparison of Series and Parallel Inverters	3-12
3.6	Half Bridge Inverter	3-12
3.6.1	Half Bridge Inverter with Inductive Load	3-13
3.6.2	Full Bridge Inverter	3-15
3.6.3	Operation with Resistive Load	3-15
3.6.4	Single Phase Thyristorised Bridge Inverter with RL Load	3-16
3.7	McMurry Bedford Commutated Half Bridge Inverter (Complementary Commutation)	3-18
3.7.1	Merits of McMurry Bedford Commutation	3-19
3.7.2	Demerits	3-19
3.8	McMurry Commutation	3-19



3.8.1	Comparison of Half Bridge and Full Bridge Inverters	3-22
3.9	Transistorised Inverters	3-22
3.9.1	Half Bridge Voltage Source Inverter (R Load)	3-22
3.9.2	Half Bridge Inverter with Inductive Load	3-23
3.10	Single Phase Full Bridge Inverter (Square Wave Output)	3-25
3.10.1	Operation with Resistive Load	3-25
3.10.2	Single Phase Bridge Inverter with RL Load	3-26
3.11	Push Pull Inverter (With RL load)	3-27
3.11.1	Operation with Resistive Load	3-28
3.11.2	Operation with Inductive (RL) Load	3-29
3.12	Three Phase Thyristorised Bridge Inverter	3-31
3.12.1	180° Mode of Conduction	3-31
3.12.2	180° Mode with a Star Connected Resistive Load (Thyristorised Inverter)	3-32
3.12.3	120° Mode of Conduction (with Star Connected Resistive Load)	3-37
3.12.4	120° with Y Connected Resistive Load (Thyristorised Inverter)	3-37
3.13	Three Phase Series Inverter	3-40
3.14	MSBTE Questions and Answers	3-40
3.15	I-Scheme Questions and Answers	3-40
	• Review Questions	3-40

Unit - IV**Chapter 4 : Dual Converters and Cycloconverters**

4-1 to 4-18

Syllabus : Dual converters : Principle and types, Circulatory current free mode, Circulatory current mode dual converters, Cyclo-converter : Principle and types, Single phase to single phase and three phase Cyclo-converter : Operation with circuit and waveforms.

4.1	Dual Converters	4-2
4.1.1	Single Phase Dual Converter	4-2
4.1.2	Four Quadrant Operation	4-2

4.1.3	Ideal Dual Converter	4-4
4.1.4	Practical Dual Converters	4-5
4.1.5	Dual Converter with Circulating Current	4-5
4.1.6	Comparison of Circulating and Non-circulating Current Modes	4-5
4.2	Cycloconverters	4-6
4.2.1	Single Phase Cycloconverter	4-6
4.2.2	Centre Tapped Transformer or Mid-point Cycloconverter	4-6
4.2.3	Operation with Inductive Load	4-9
4.3	Bridge Type Single Phase Cycloconverter	4-9
4.3.1	Non-Circulating Current Mode (With R Load)	4-10
4.3.2	Operation with Inductive Load (Noncirculating Current Mode)	4-13
4.3.3	Circulating Current Mode	4-14
4.3.4	Comparison of Circulating and Noncirculating Modes	4-14
4.4	Three Phase Half Wave Cycloconverters	4-14
4.4.1	Three Phase to Single Phase Cycloconverter	4-14
4.4.2	Three Phase to Single Phase Bridge Cycloconverter	4-15
4.4.3	3-Phase to 3-Phase Cycloconverters	4-17
4.5	Advantages of Cycloconverter	4-17
4.6	Disadvantages of Cycloconverter	4-17
4.7	Applications of Cycloconverter	4-17
4.8	I-Scheme Questions and Answers	4-18
	• Review Questions	4-17

Unit - V**Chapter 5 : Industrial Applications of Power Devices**

5-1 to 5-25

Syllabus : Static circuit breaker (DC and AC), High frequency heating : Induction heating and dielectric heating control, Electric Welding Control, Battery charger control, AC voltage stabilizer type : Servo, Solid state and relay. Static VAR compensation system, Closed loop speed control method for DC and AC servomotor, Simulation : Chopper, Inverter and Cyclo - Converter Circuits.



5.1	Introduction	5-2	5.7.6	Other Applications	5-12
5.2	Static Switches	5-2	5.8	Electric Welding Control	5-12
5.2.1	Static Switch using Inverse Parallel SCRs	5-2	5.9	Principle of Resistance Welding	5-13
5.2.2	Static Switch using Triac	5-3	5.10	Basic AC Resistance Welding System	5-14
5.2.3	Static Circuit Breaker	5-3	5.11	Electronic Circuits used in Resistance Welding System	5-14
5.2.4	Static DC Circuit Breaker	5-3	5.12	Line Contactor	5-15
5.2.5	Static AC Circuit Breaker	5-4	5.12.1	SCR Line Contactor	5-15
5.3	Various Methods of Heating	5-4	5.13	Advantages and Disadvantages of Resistance Welding	5-16
5.3.1	Advantages of Electric Heating	5-5	5.13.1	Advantages	5-16
5.4	Radio Frequency (RF) Heating	5-5	5.13.2	Disadvantages	5-16
5.5	Induction Heating	5-6	5.14	Simple Battery Charger	5-16
5.5.1	Principle of Induction Heating	5-6	5.14.1	Battery Charging Regulator	5-17
5.5.2	Block Diagram of Induction Heating	5-7	5.15	AC Voltage Regulator (Stabilizer)	5-18
5.5.3	Power Source used in Induction Heating	5-7	5.15.1	Principle of Operation	5-18
5.5.4	Advantages of Induction Heating	5-7	5.15.2	Regulator Types	5-18
5.5.5	Disadvantages of Induction Heating	5-8	5.16	Relay Type or Tap Changing AC Voltage Stabilizer	5-18
5.5.6	Applications of the Induction Heating	5-8	5.17	Static or Solid State AC Voltage Stabilizer	5-19
5.6	Dielectric Heating :	5-10	5.18	Servo Type AC Voltage Stabilizer	5-20
5.6.1	Principle of Dielectric Heating	5-10	5.19	Comparison of AC Voltage Stabilizers	5-20
5.6.2	Block Diagram of Dielectric Heating	5-10	5.20	Static VAR Compensation System	5-21
5.6.3	Advantages of Dielectric Heating	5-11	5.21	Servomotors	5-21
5.6.4	Disadvantages of Dielectric Heating	5-11	5.21.1	A.C. Servomotor	5-22
5.6.5	Comparison of Induction Heating and Dielectric Heating	5-11	5.21.2	Closed Loop Speed Control of AC Servomotor	5-22
5.7	Applications of Dielectric Heating	5-11	5.22	DC Servomotors	5-23
5.7.1	Preheating of Plastic Performs	5-12	5.22.1	Field Controlled DC Servomotor	5-23
5.7.2	Gluing of Wood	5-12	5.22.2	Armature Controlled DC Servomotor	5-23
5.7.3	Sewing of Plastic Films	5-12	5.22.3	Closed Loop Speed Control of a DC Servomotor	5-24
5.7.4	Food Processing	5-12	5.23	I-Scheme Questions and Answers.....	5-24
5.7.5	Diathermy	5-12		• Review Questions	5-24

